
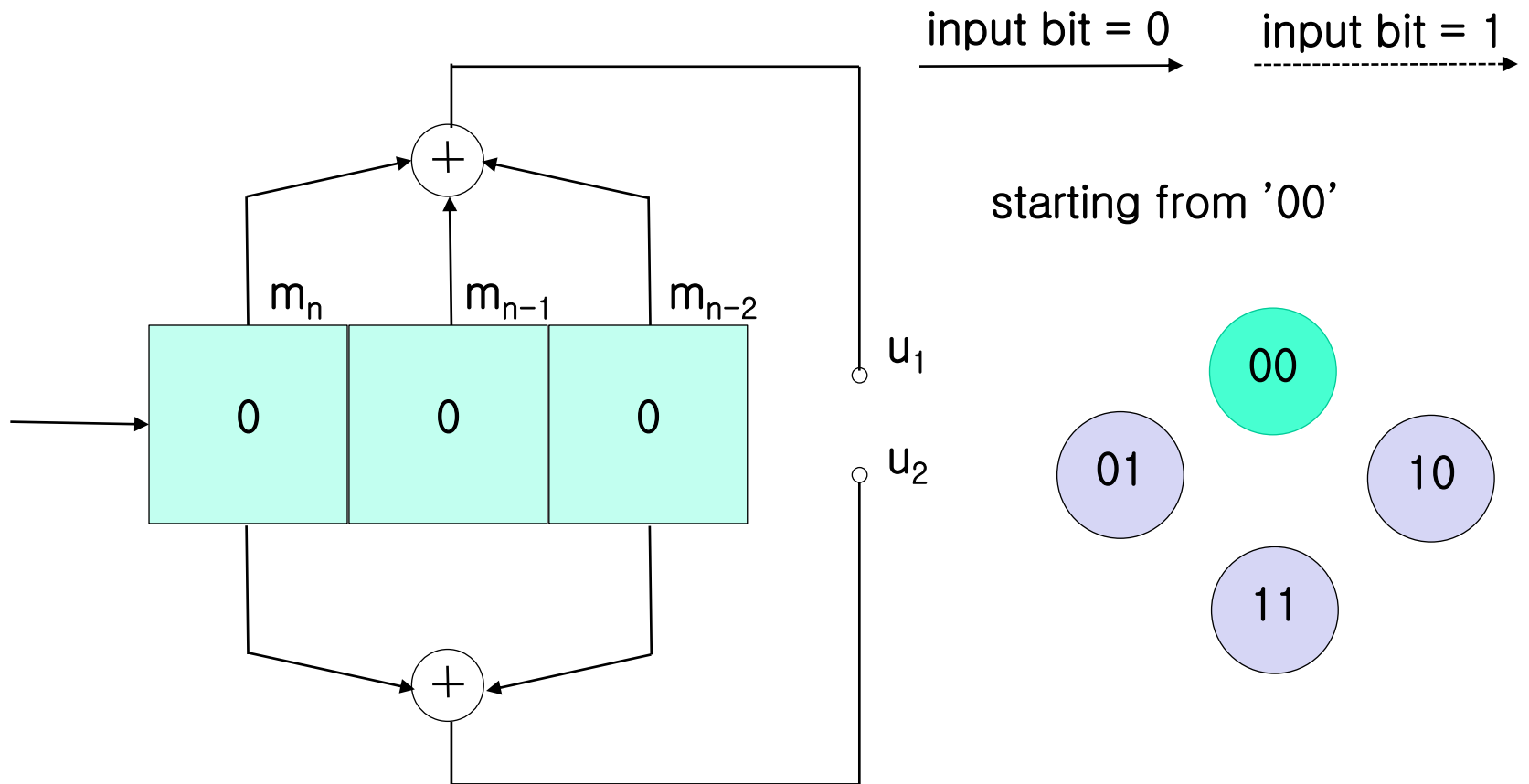



# Convolutional Code


- **State diagram (pp. 2-21),**
- **Trellis diagram (pp.22-69),**
- **Viterbi decoding (pp.70 ~)**


# State diagram

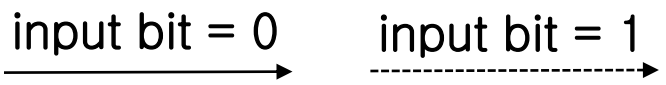




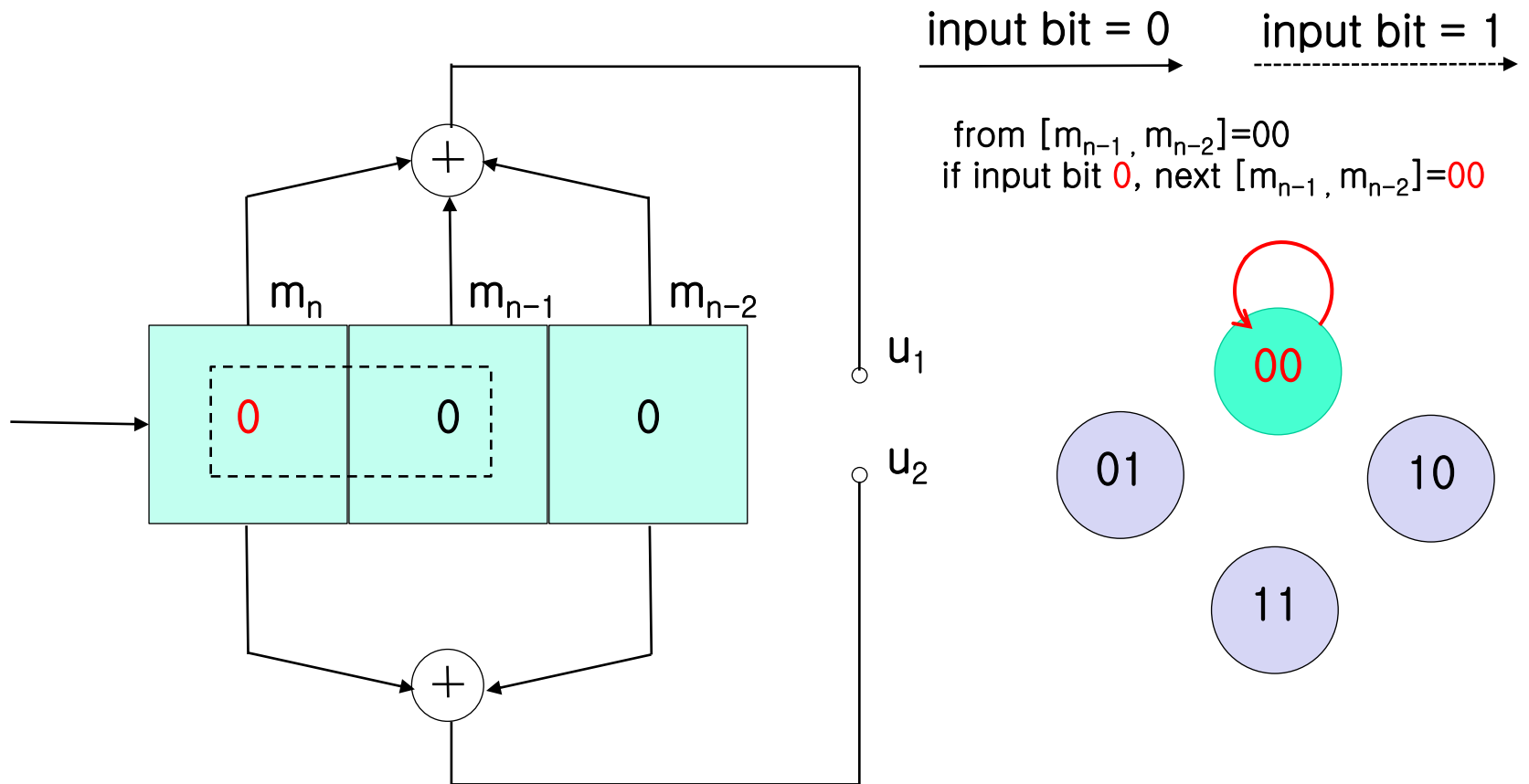


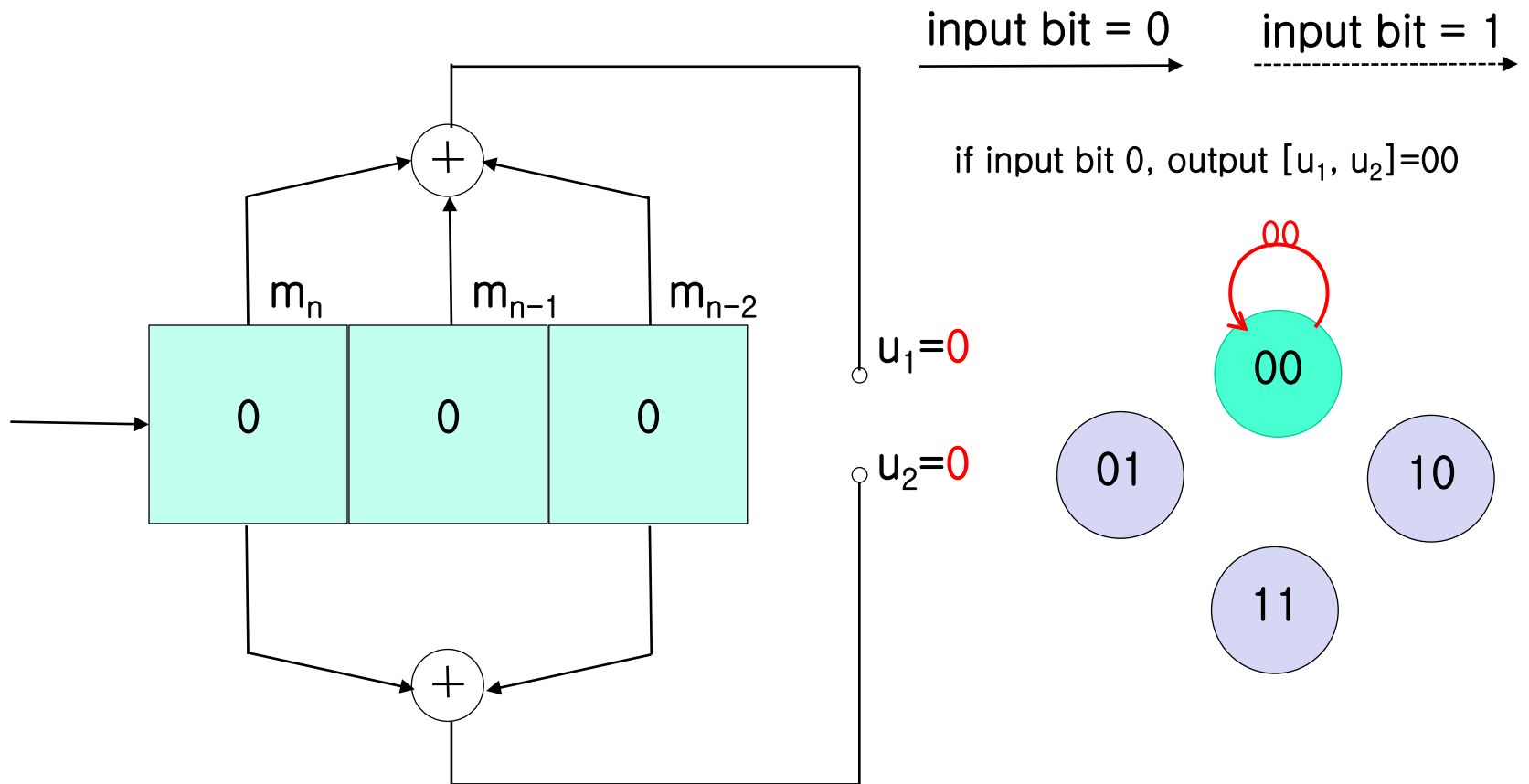

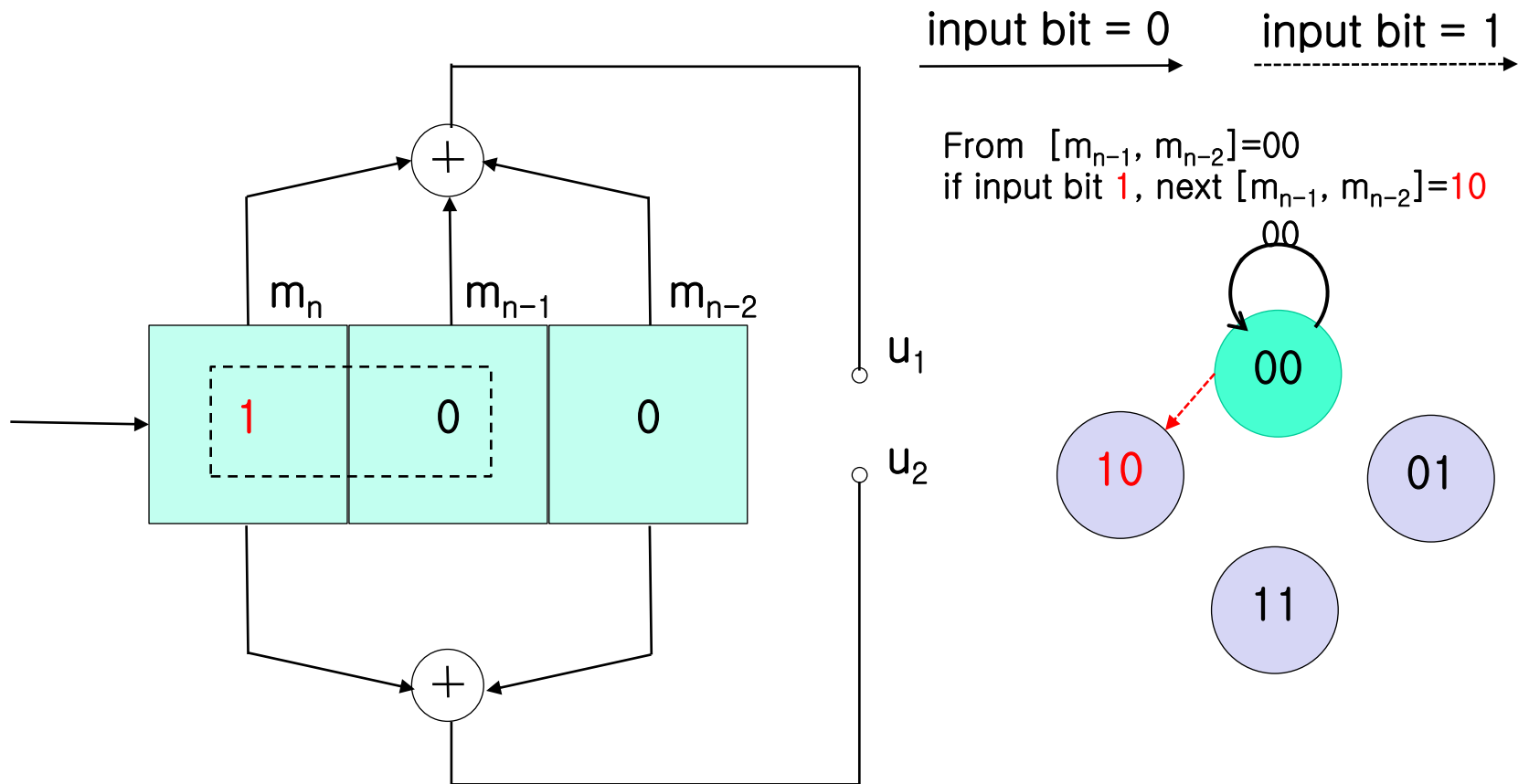

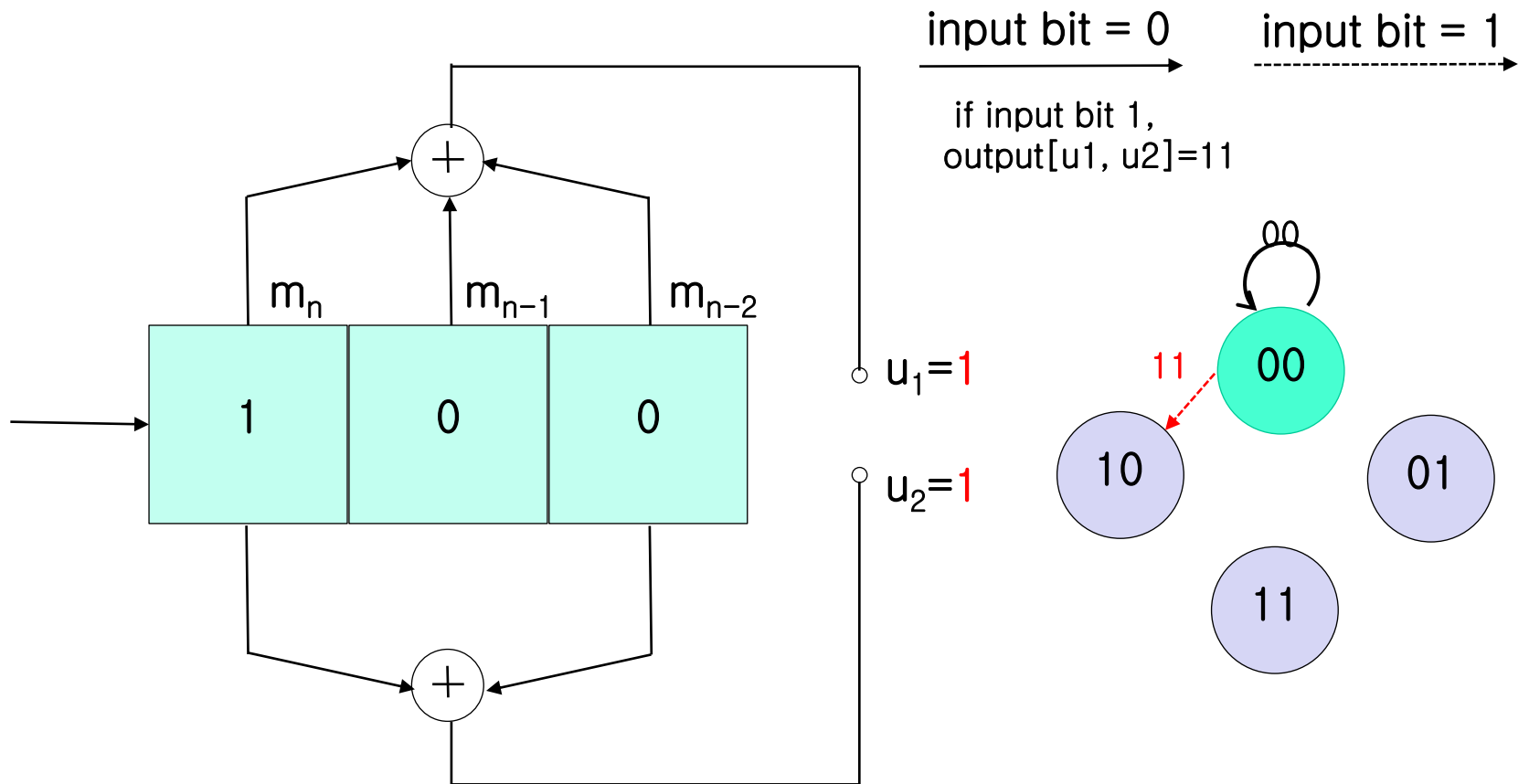




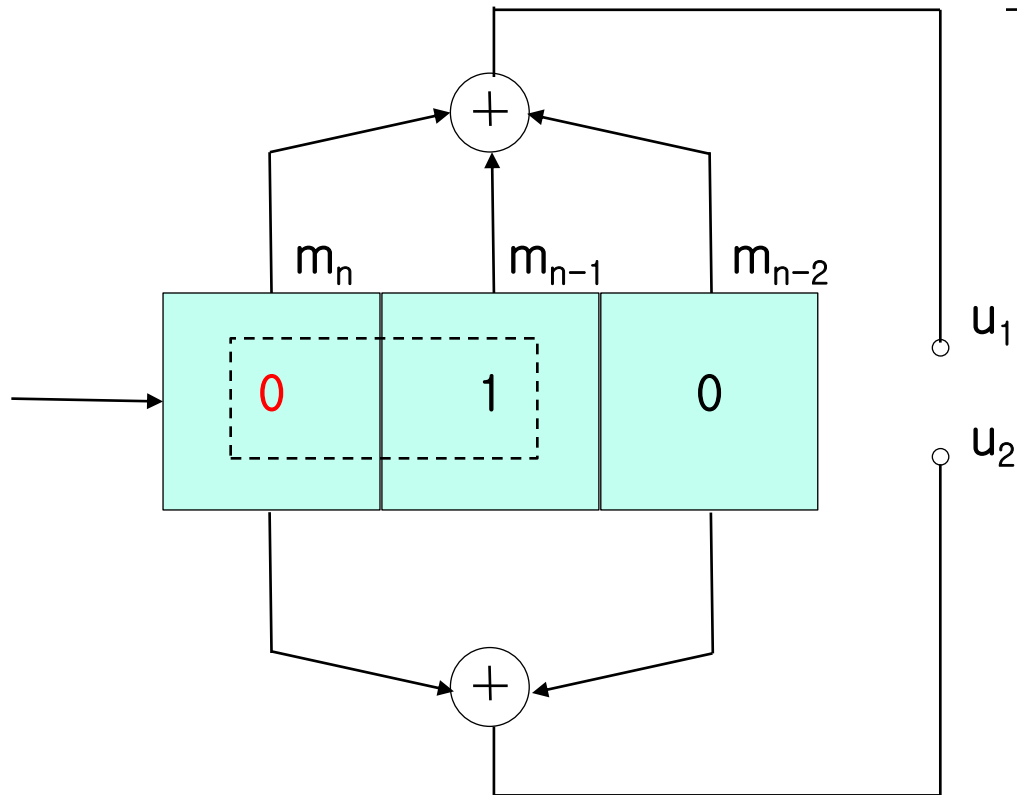


input bit = 0

input bit = 1

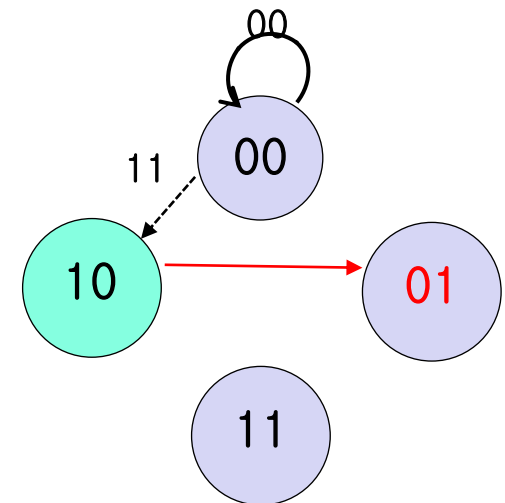From  $[m_{n-1}, m_{n-2}] = [1\ 0]$   
 if input bit **0**, next  $[m_{n-1}, m_{n-2}] = \mathbf{01}$




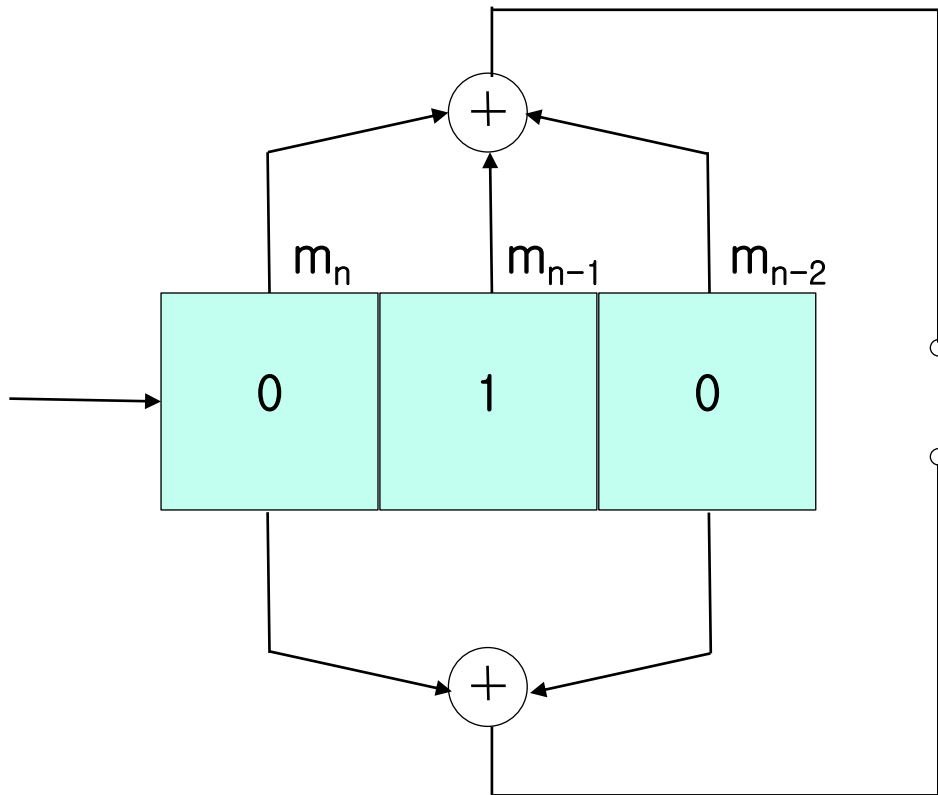


input bit = 0

input bit = 1

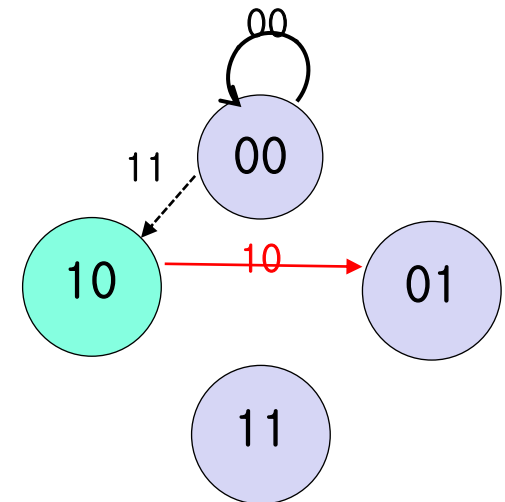if input bit 0, output[ $u_1$ ,  $u_2$ ]=10




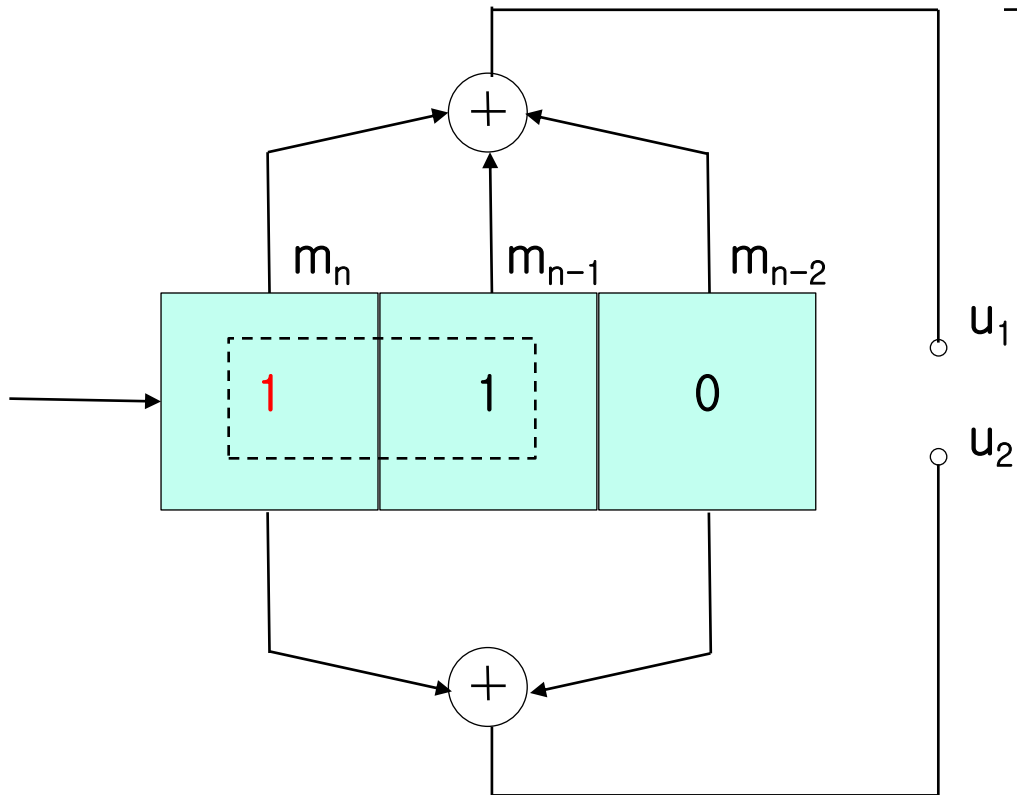



input bit = 0

input bit = 1

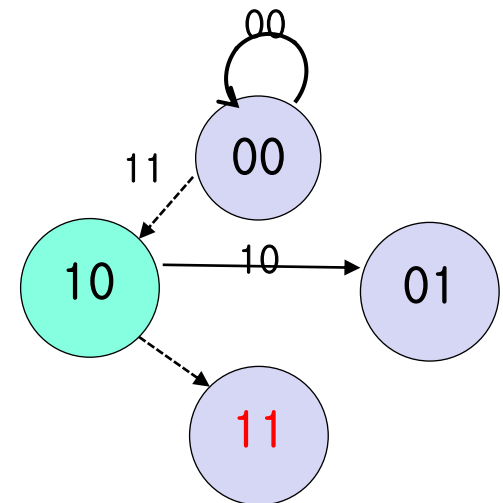From  $[m_{n-1}, m_{n-2}] = [1\ 0]$   
 if input bit 1, next  $[m_{n-1}, m_{n-2}] = \mathbf{11}$



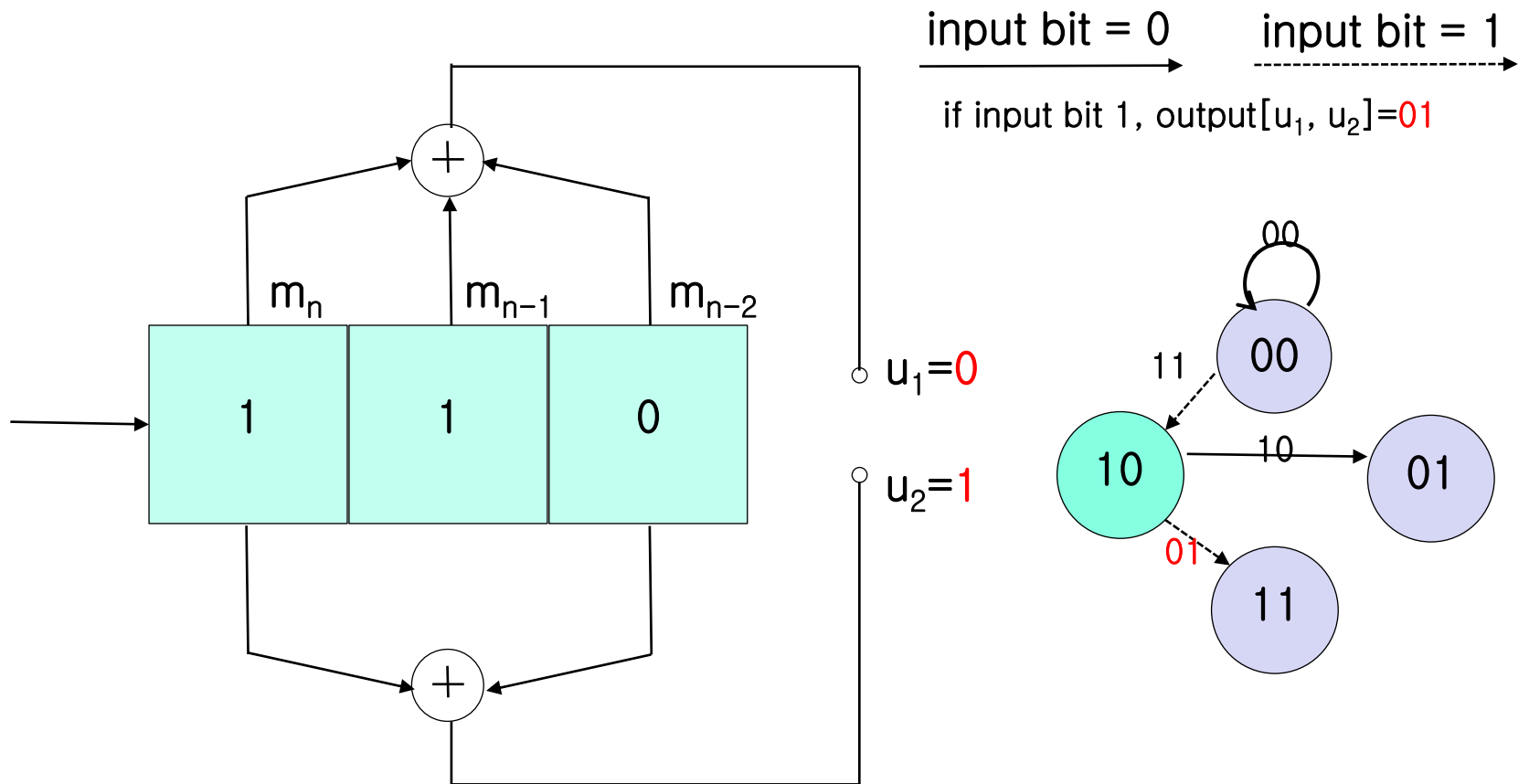


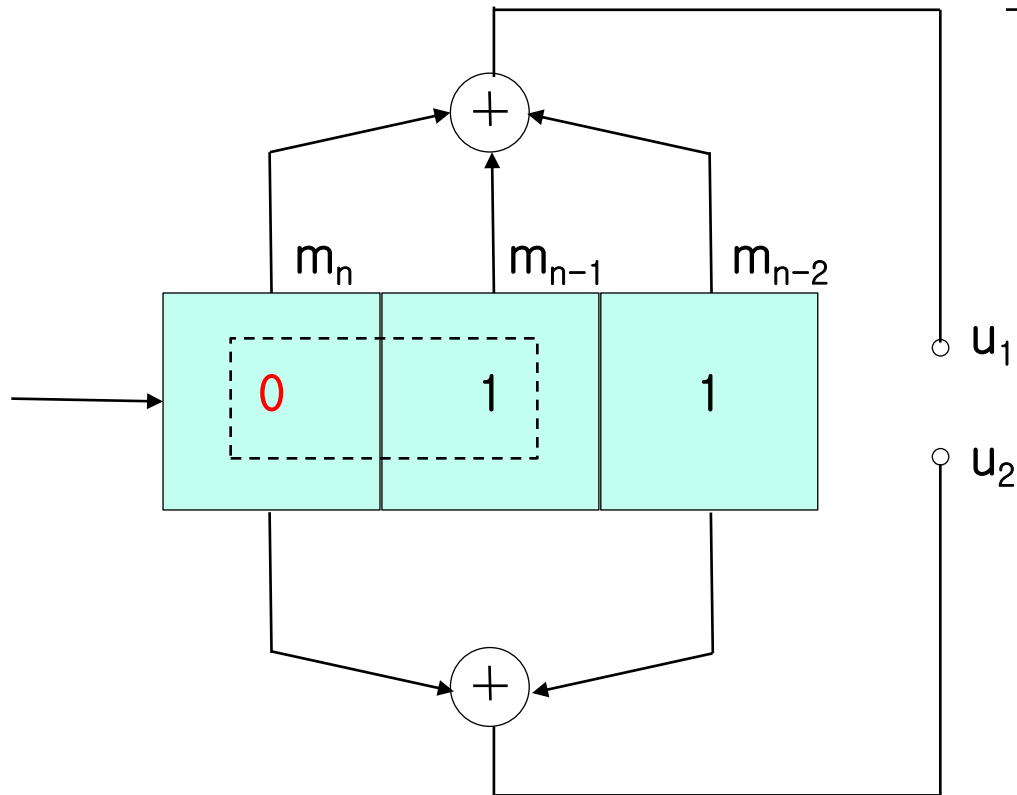


input bit = 0

input bit = 1

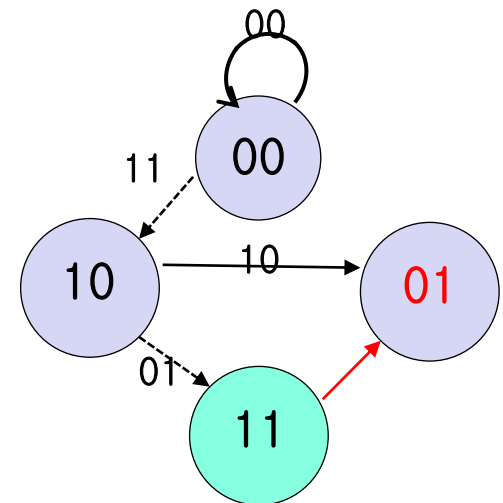From  $[m_{n-1}, m_{n-2}] = [1 \ 1]$   
 if input bit **0**, next  $[m_{n-1}, m_{n-2}] = \mathbf{01}$




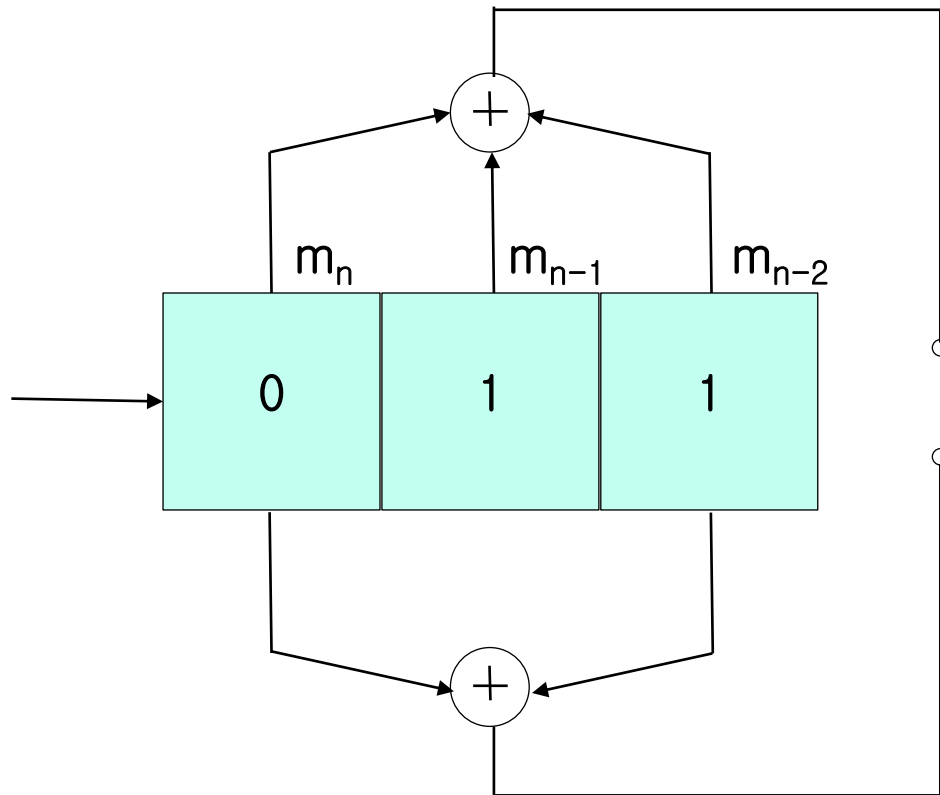


input bit = 0

input bit = 1

if input bit 0,  $[u_1, u_2] = 01$

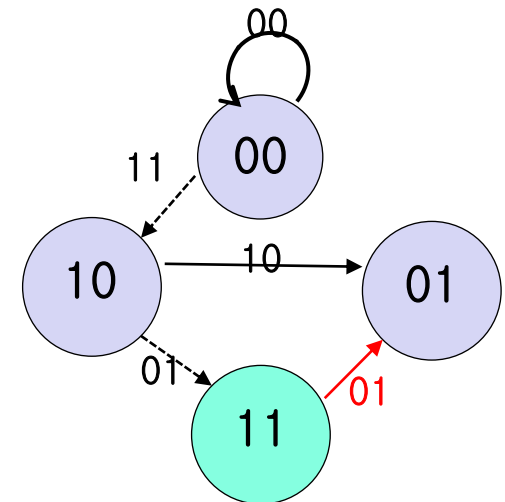


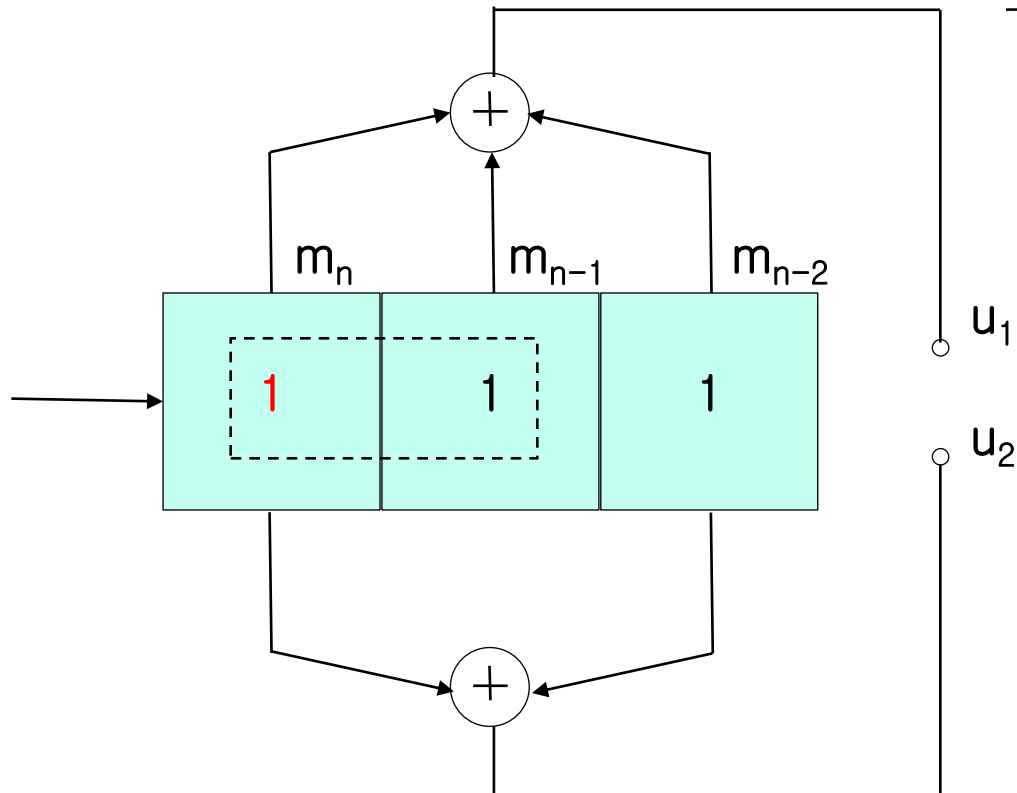


input bit = 0


input bit = 1

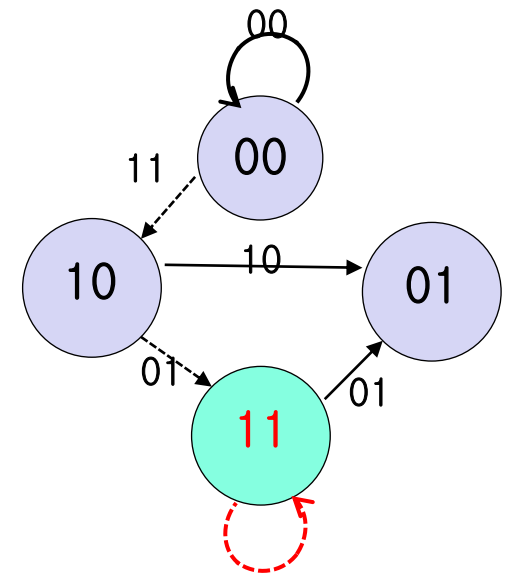From  $[m_{n-1}, m_{n-2}] = [1 \ 1]$   
 if input bit **1**, next  $[m_{n-1}, m_{n-2}] = \mathbf{11}$




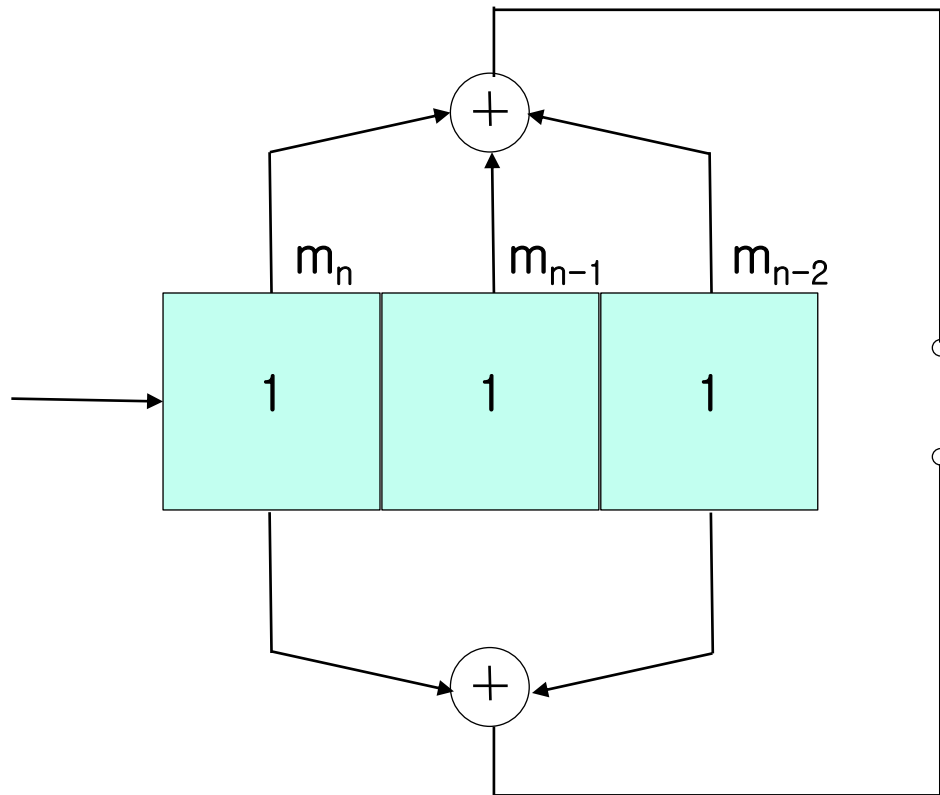

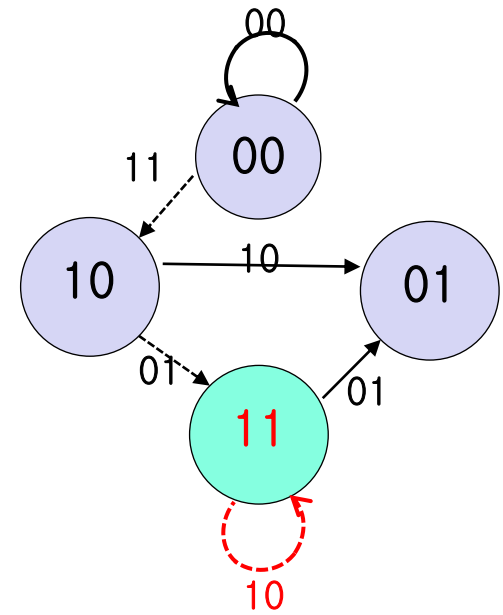$\xrightarrow{\text{input bit} = 0}$ 
 $\xrightarrow{\text{input bit} = 1}$   
 if input bit 1, output  $[u_1, u_2] = 10$






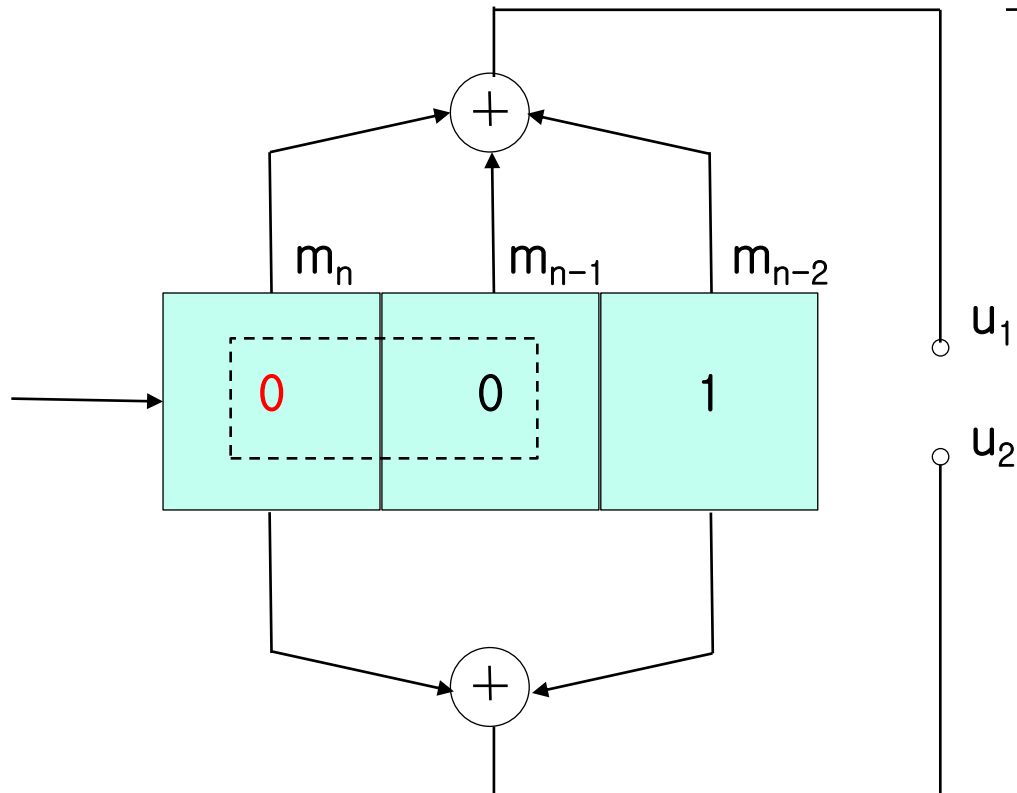


input bit = 0


input bit = 1

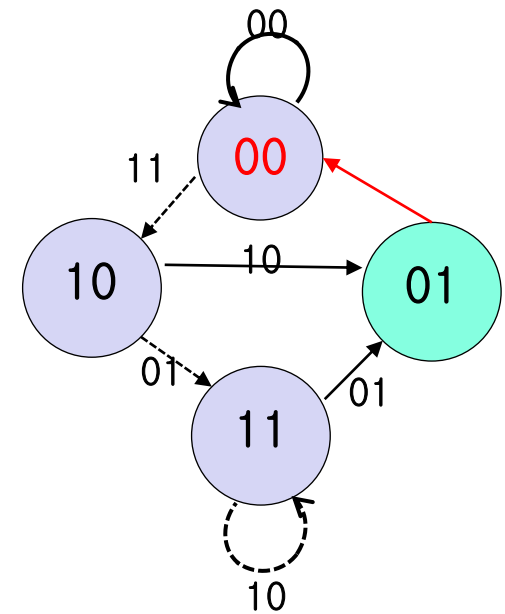
From  $[m_{n-1}, m_{n-2}] = [0 \ 1]$   
 if input bit **0**, next  $[m_{n-1}, m_{n-2}] = \mathbf{00}$



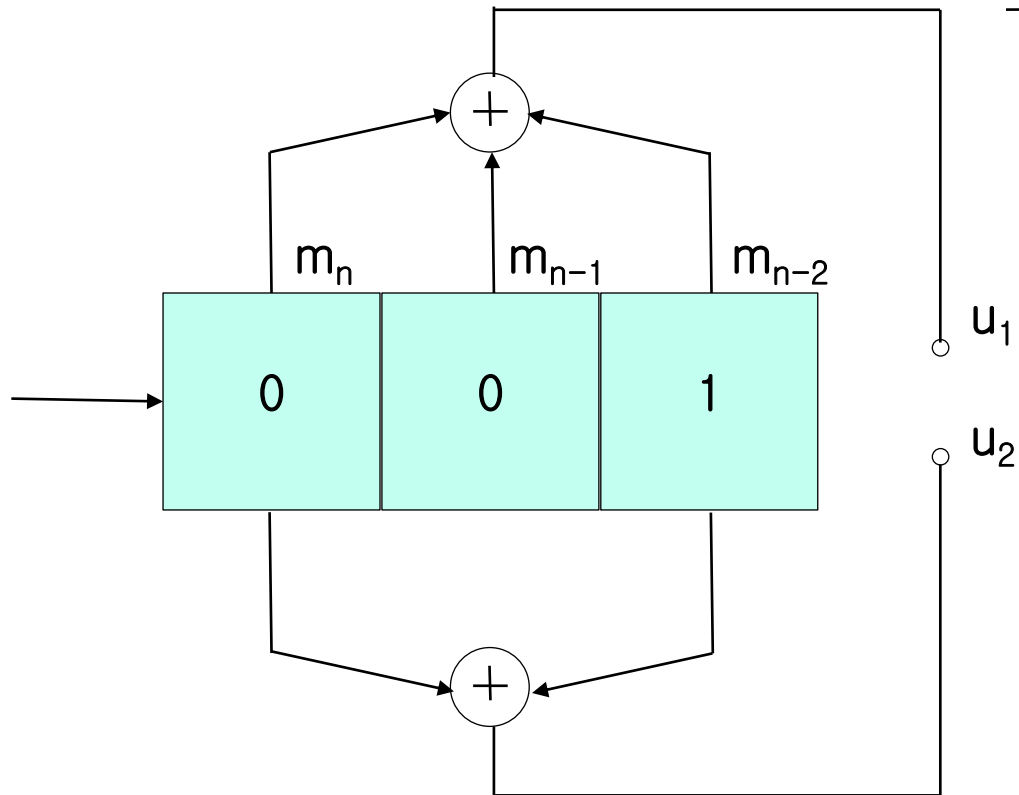

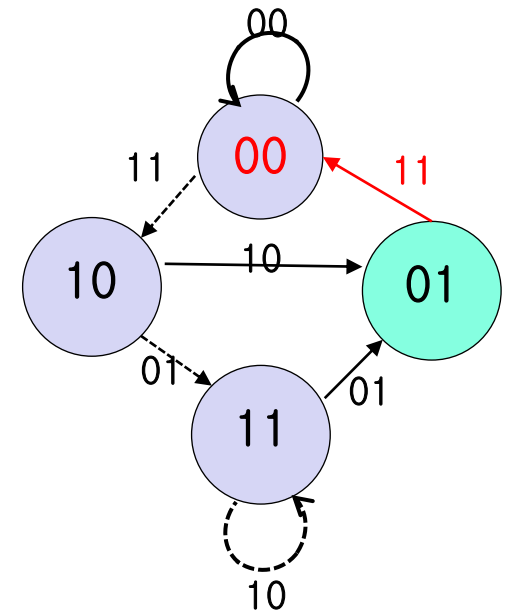input bit = 0      input bit = 1  
 ----->      ----->  
 if input bit 0, output  $[u_1, u_2] = 11$





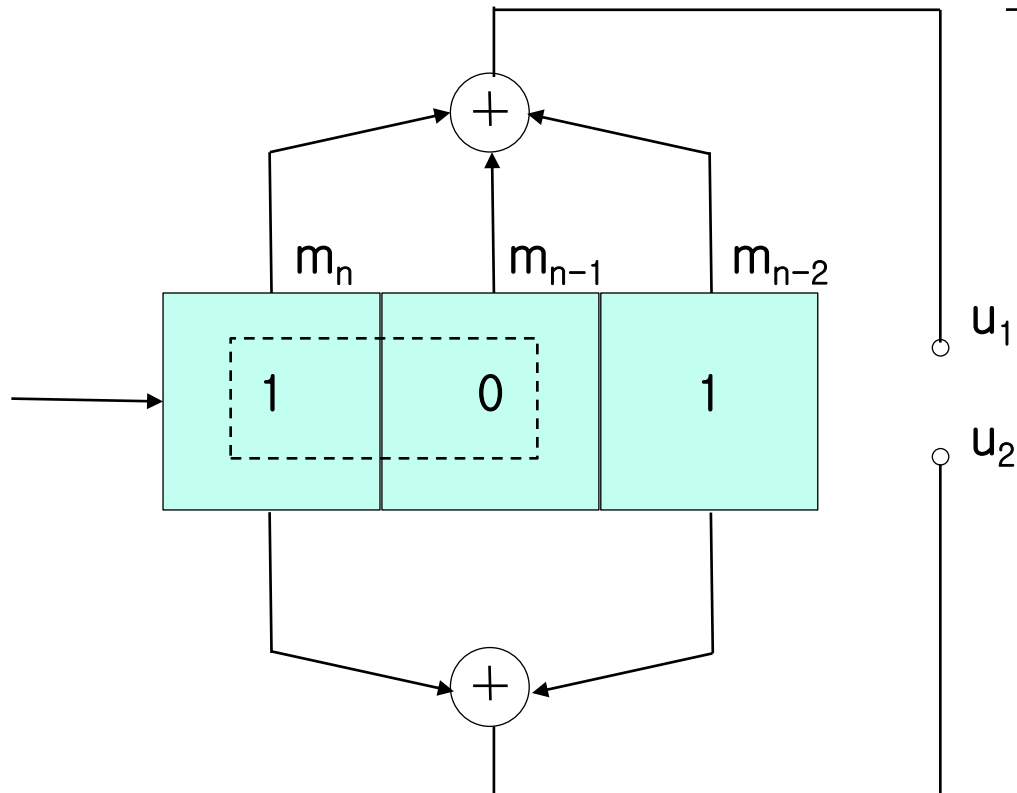



input bit = 0

input bit = 1

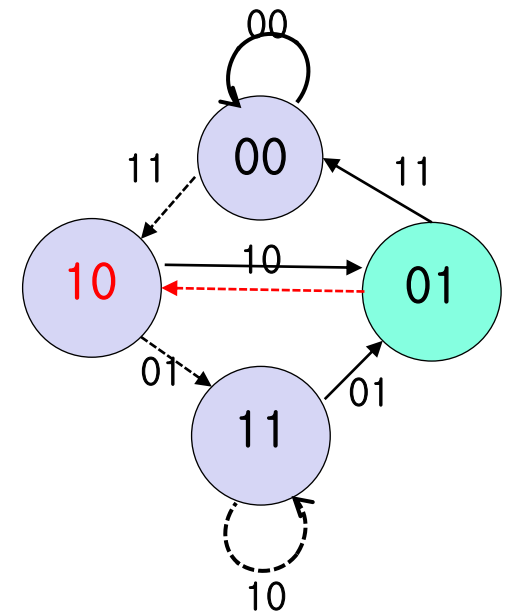
From  $[m_{n-1}, m_{n-2}] = [0 \ 1]$   
 if input bit **1**, next  $[m_{n-1}, m_{n-2}] = \mathbf{10}$



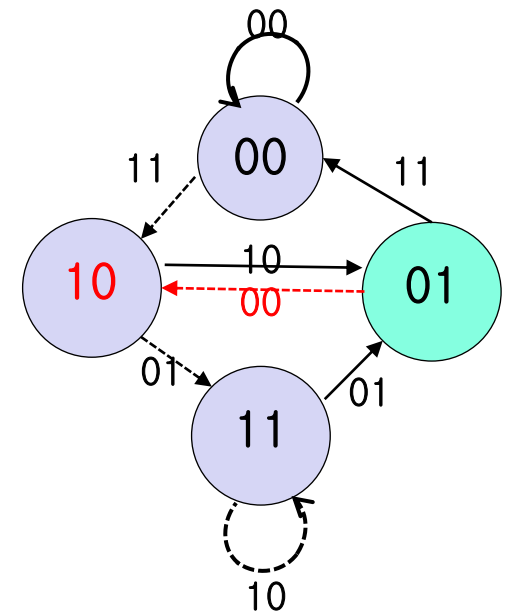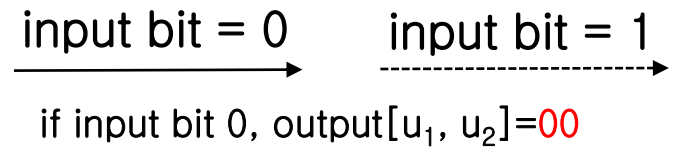

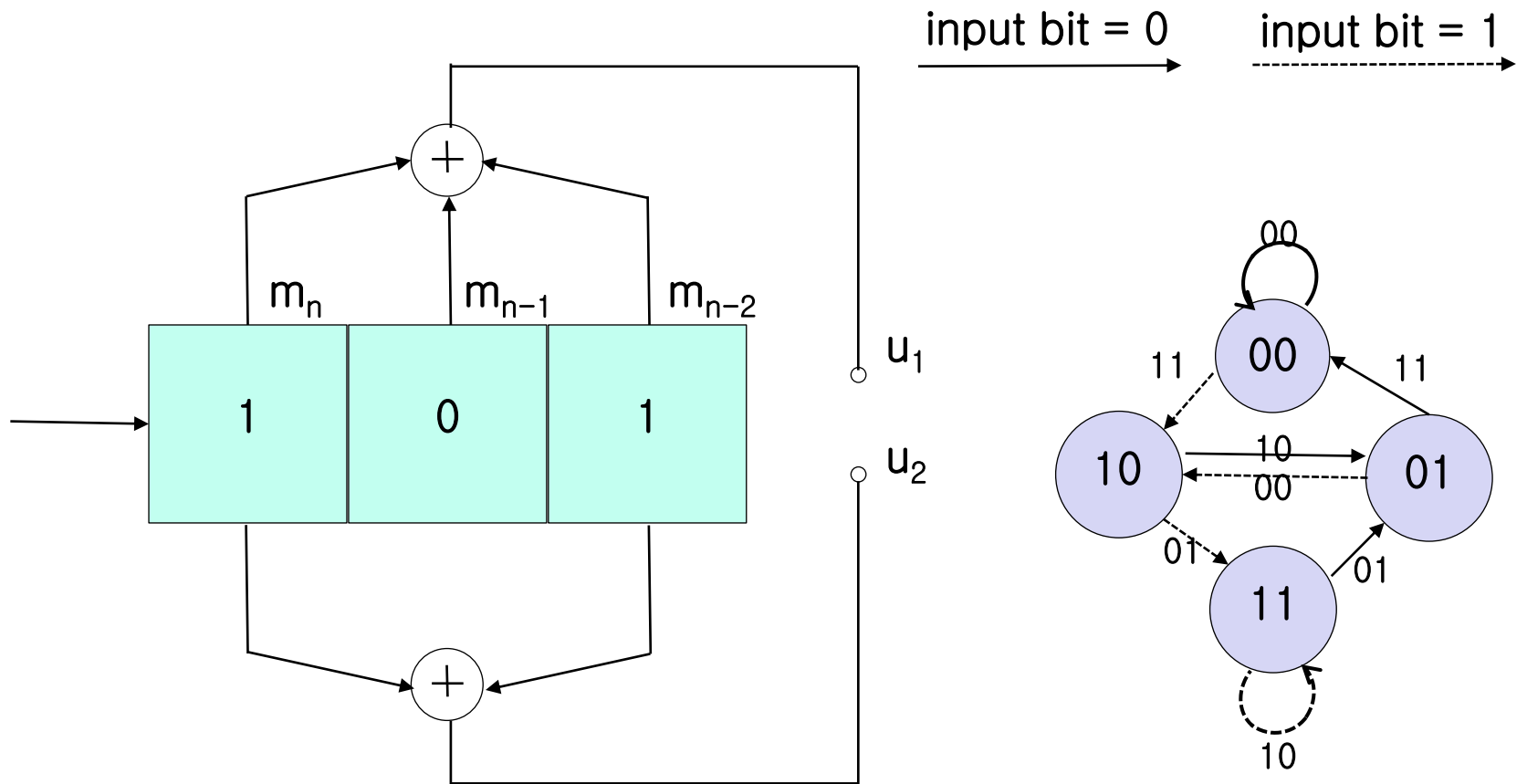

# Trellis diagram


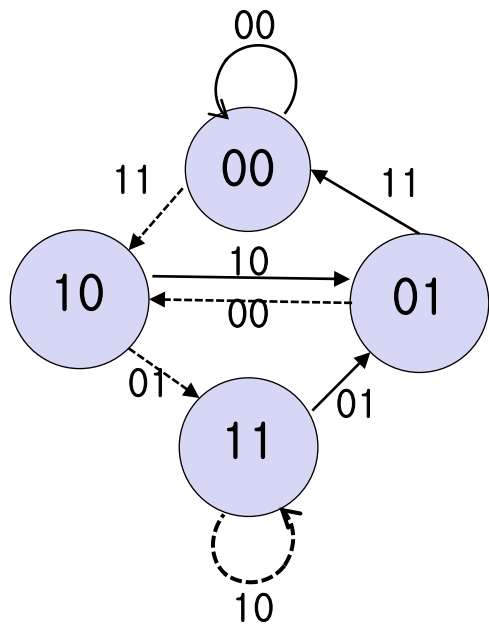


$a = 00$   $t_1$  ●

$b = 10$

$c = 01$

$d = 11$

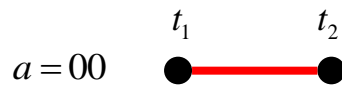
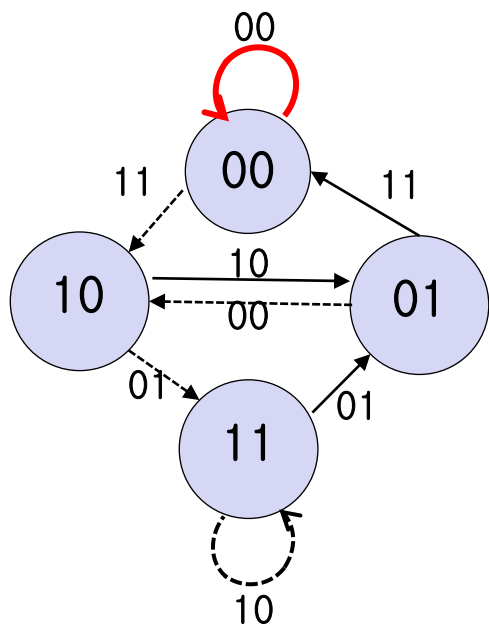


$b = 10$

$c = 01$

$d = 11$





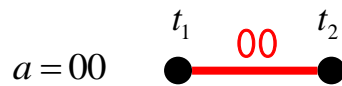
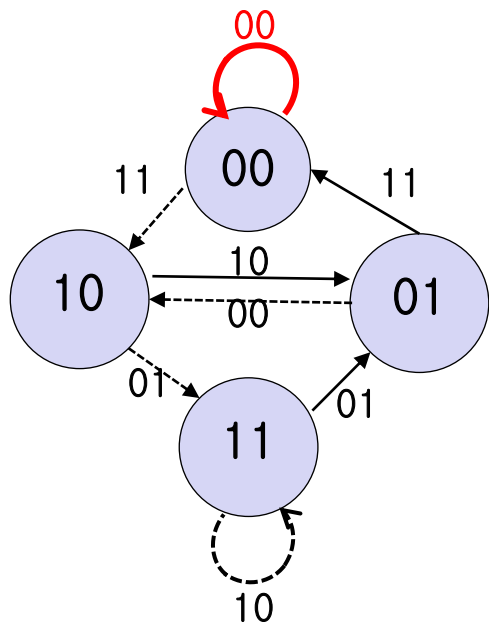




$b = 10$



$c = 01$



$d = 11$

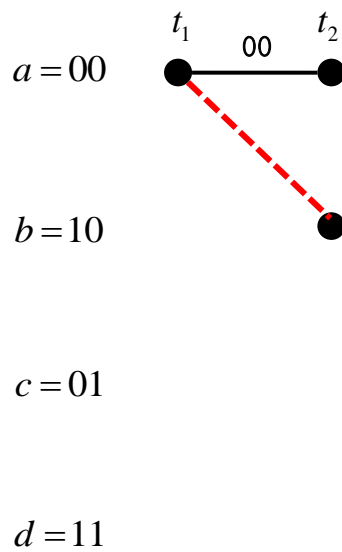
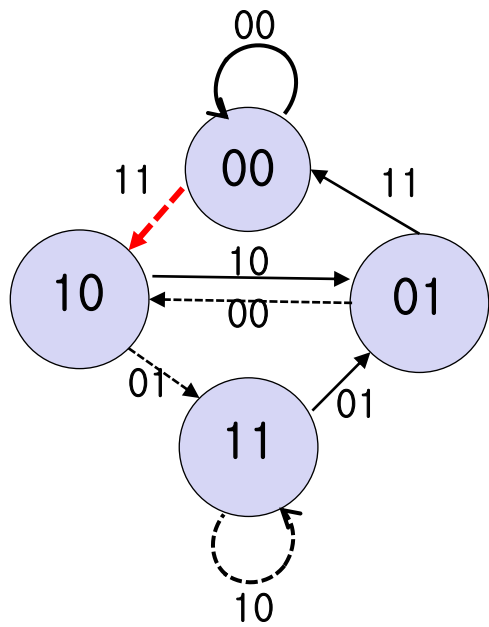


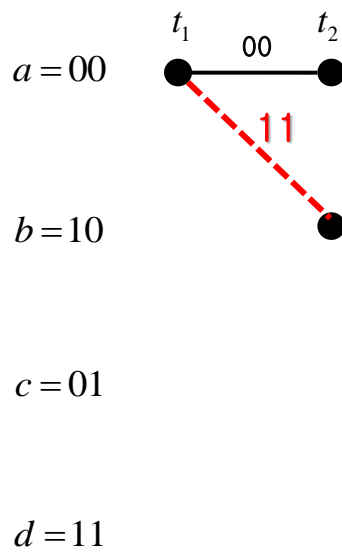
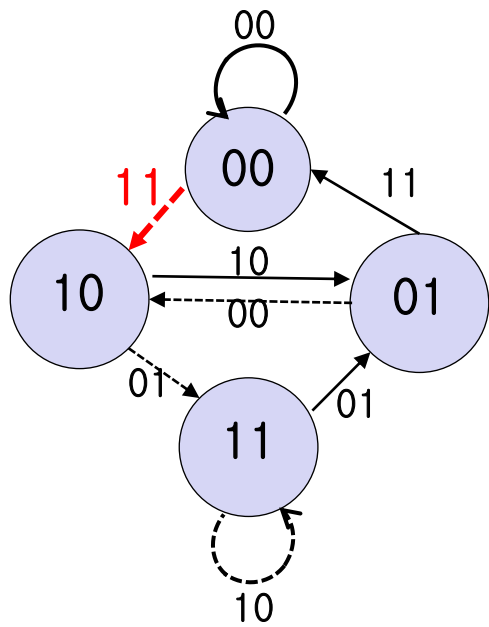


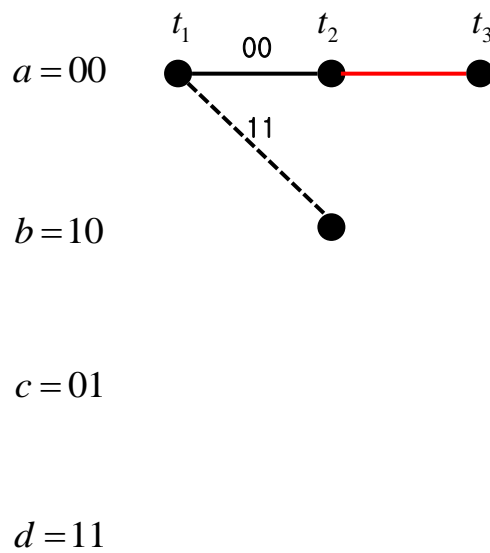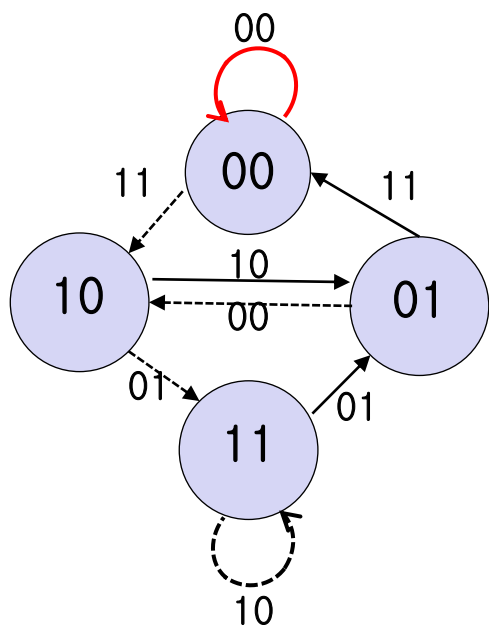

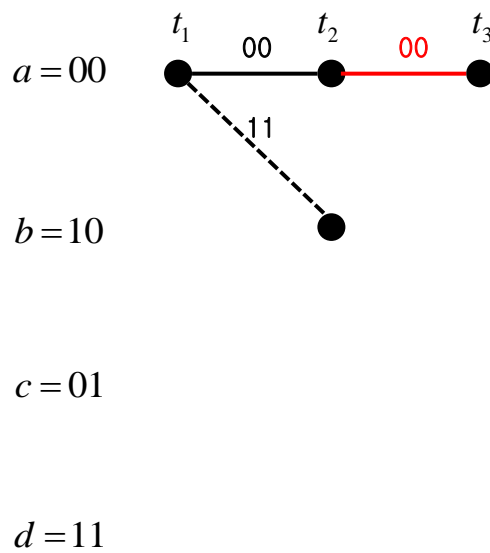
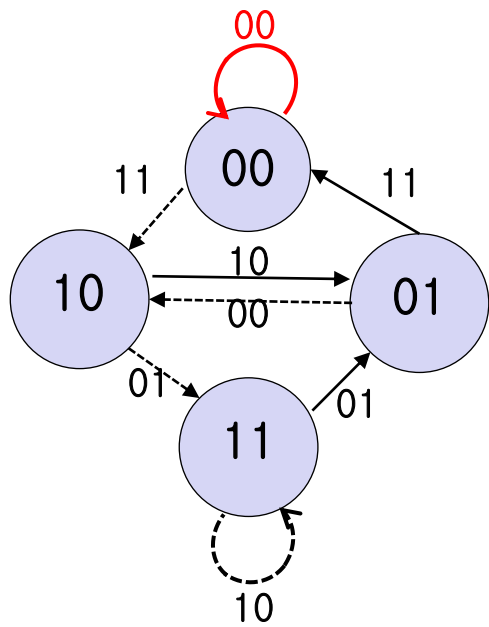


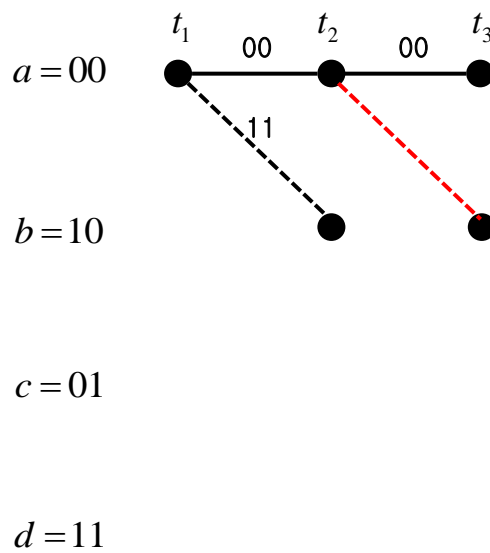
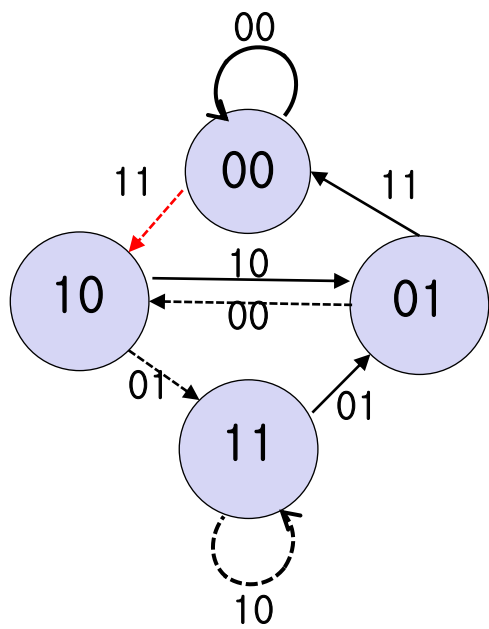


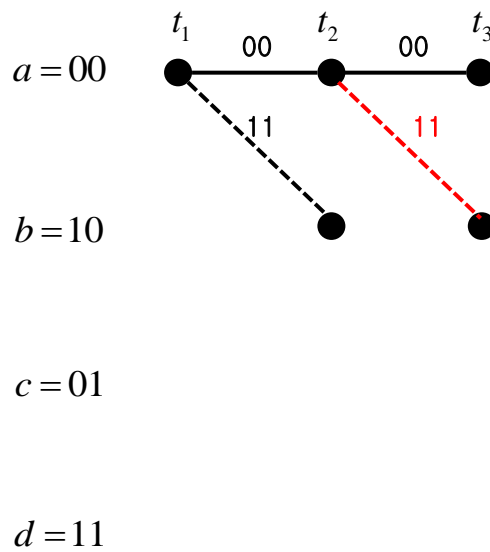
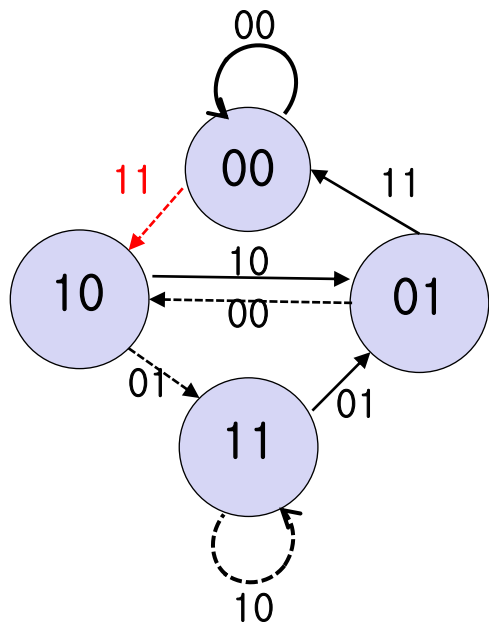


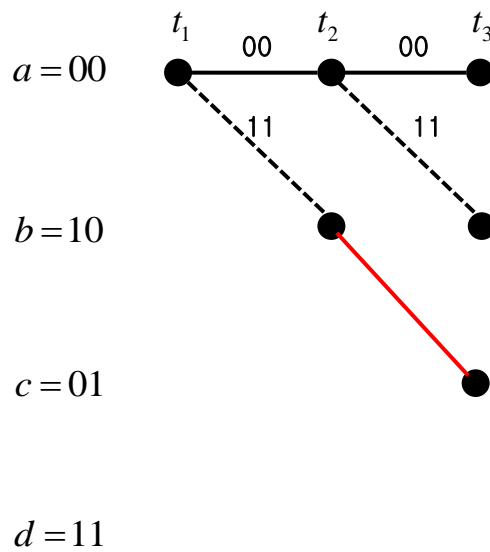
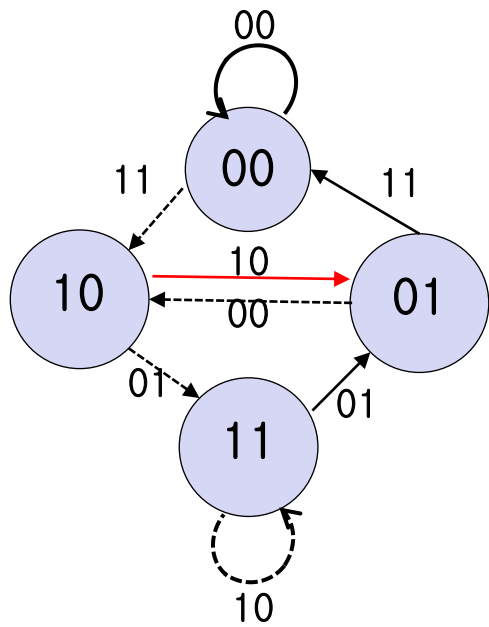






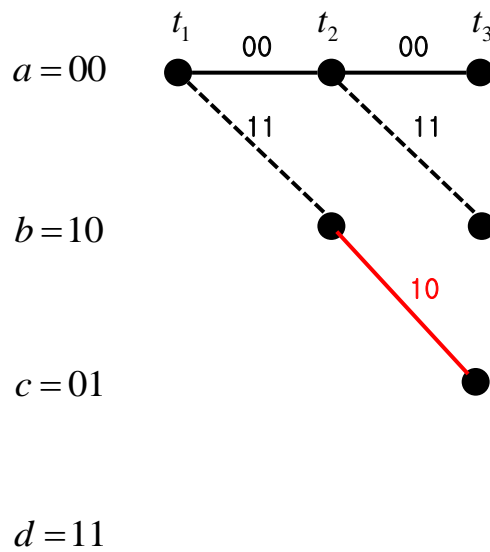
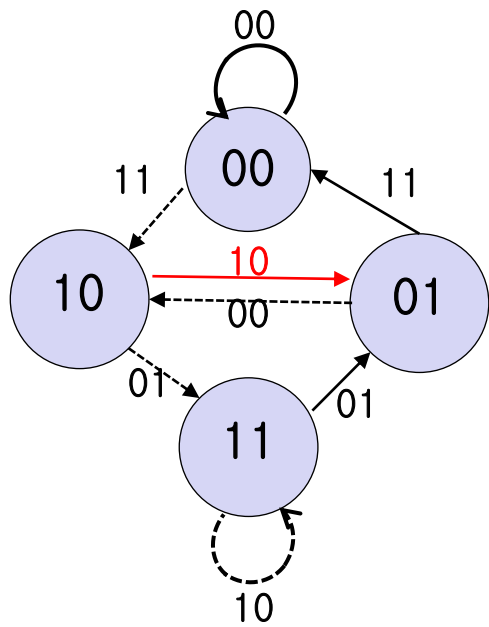


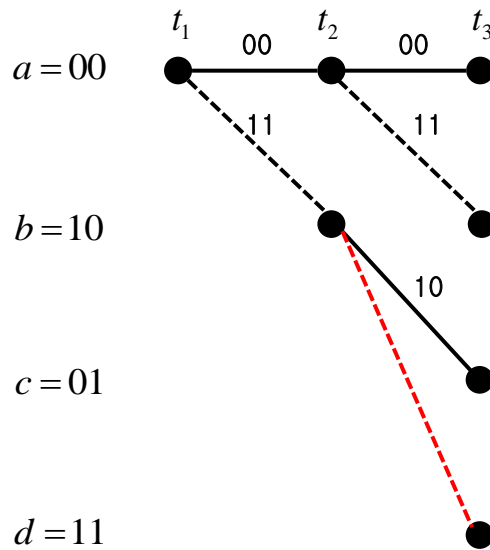
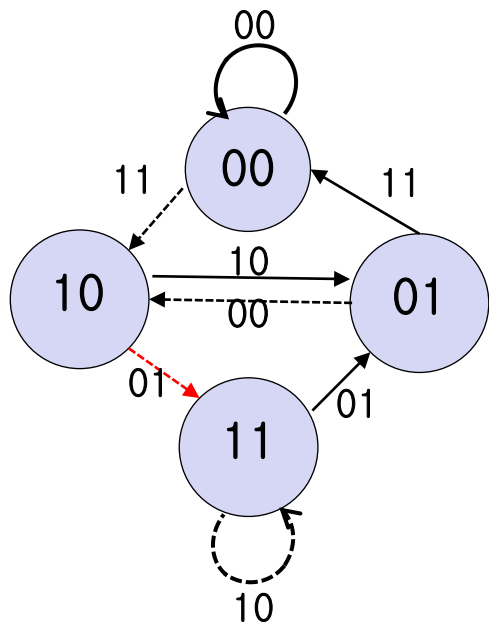


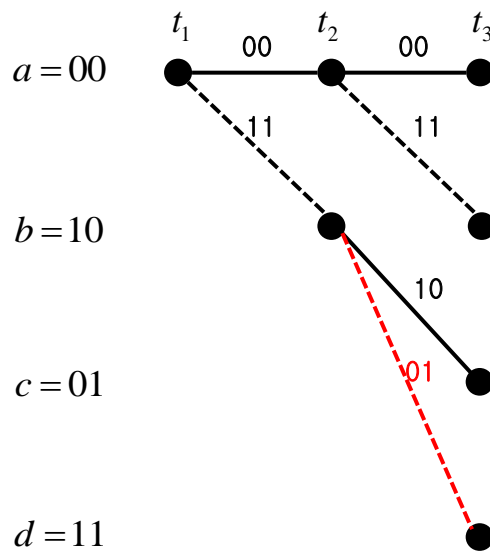
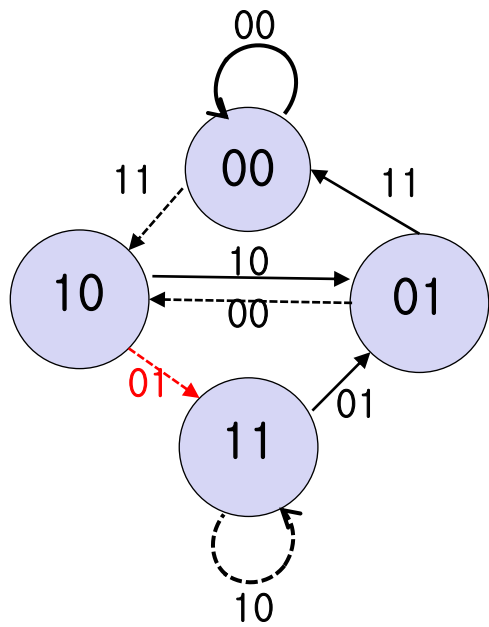


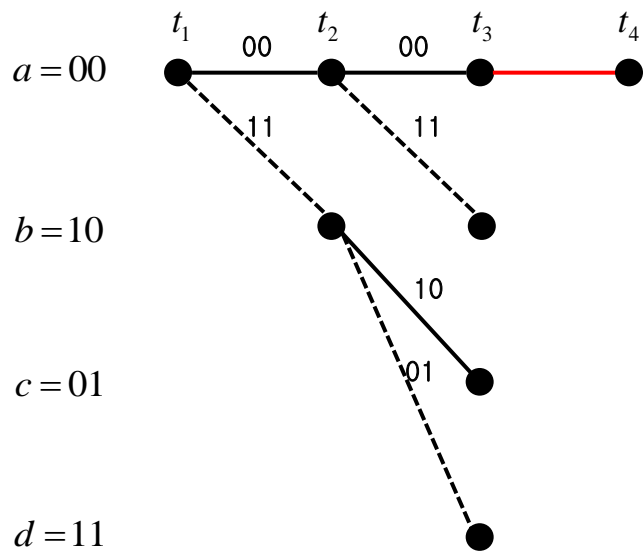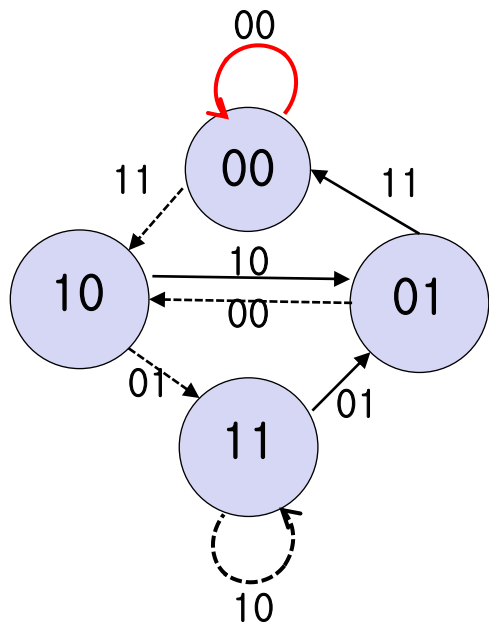

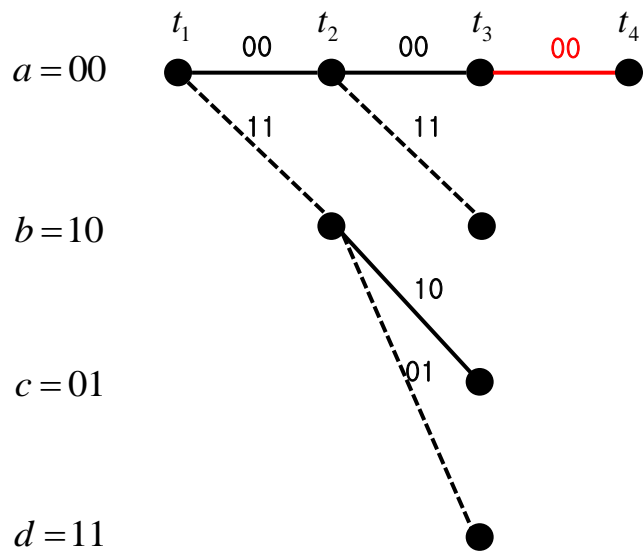
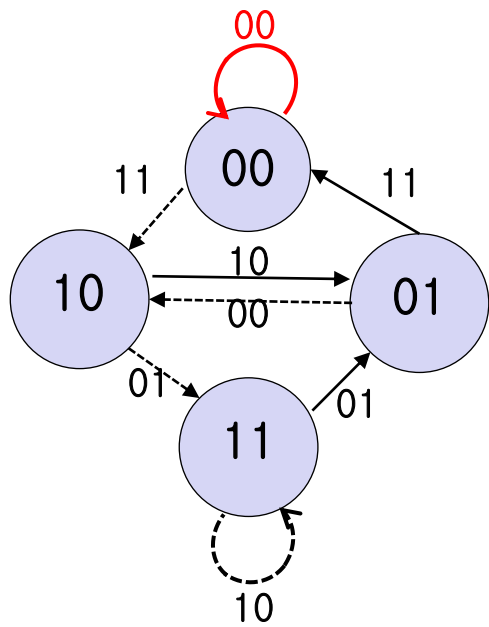


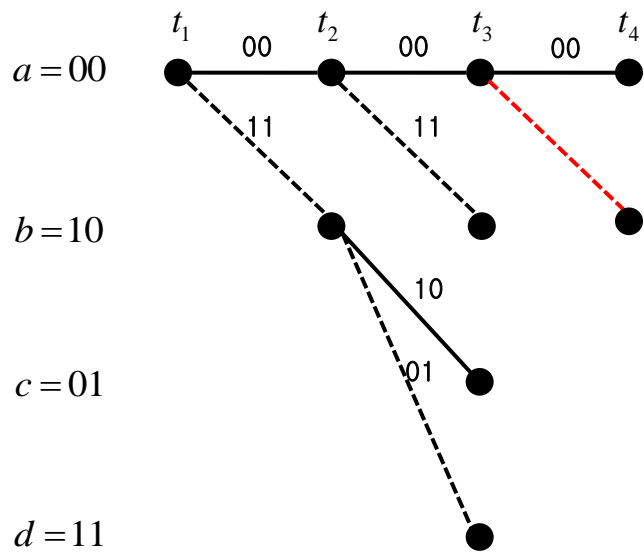
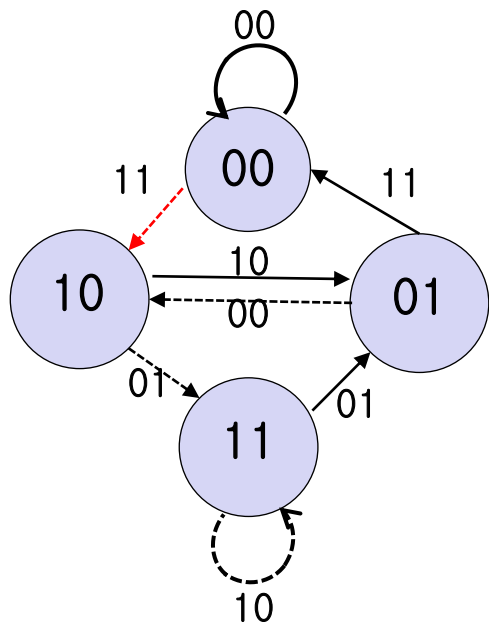


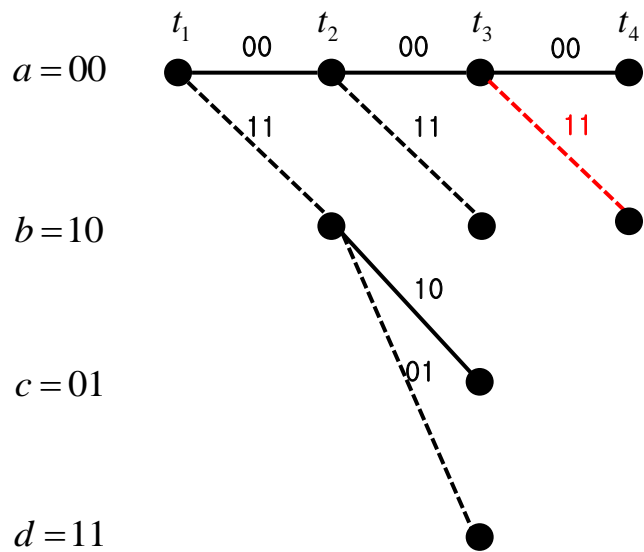
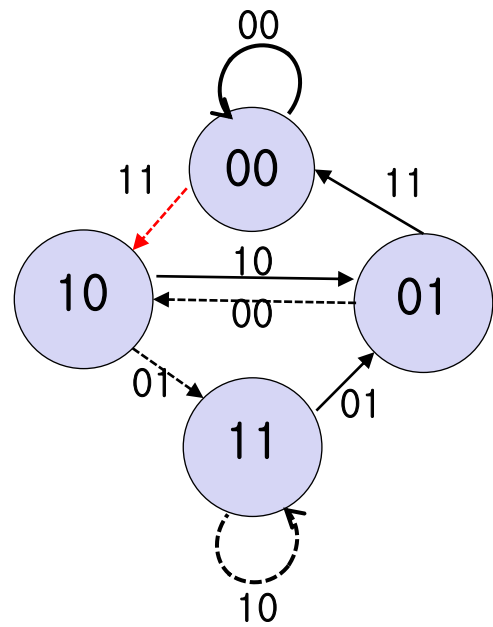


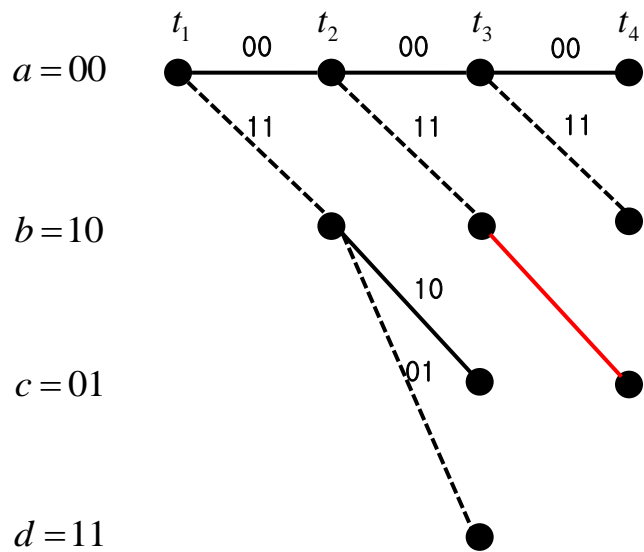
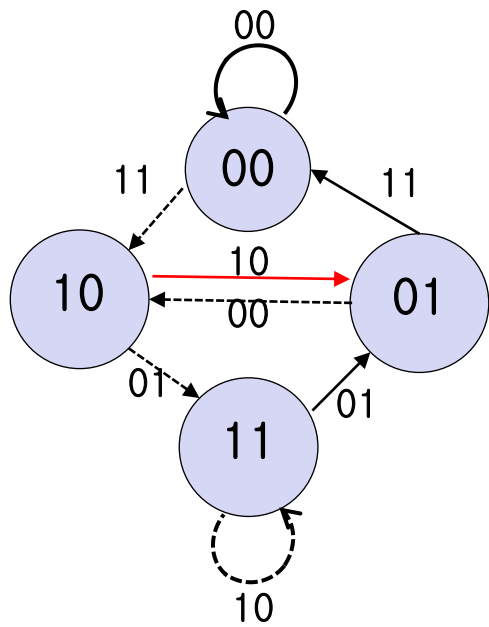






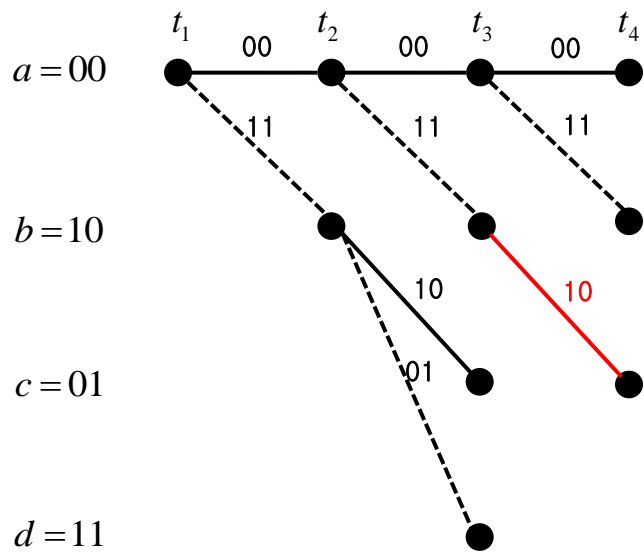
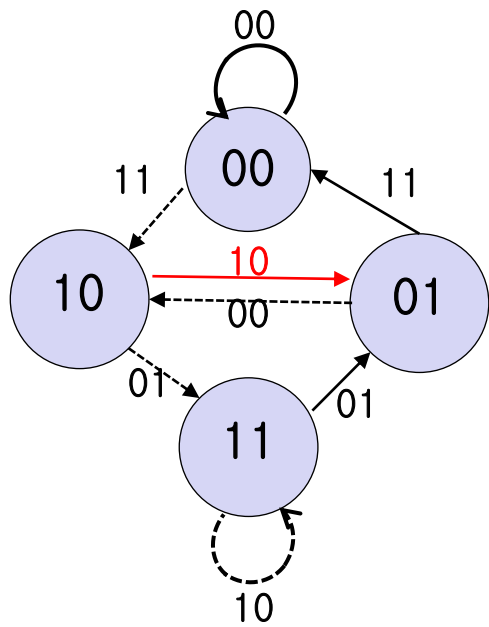


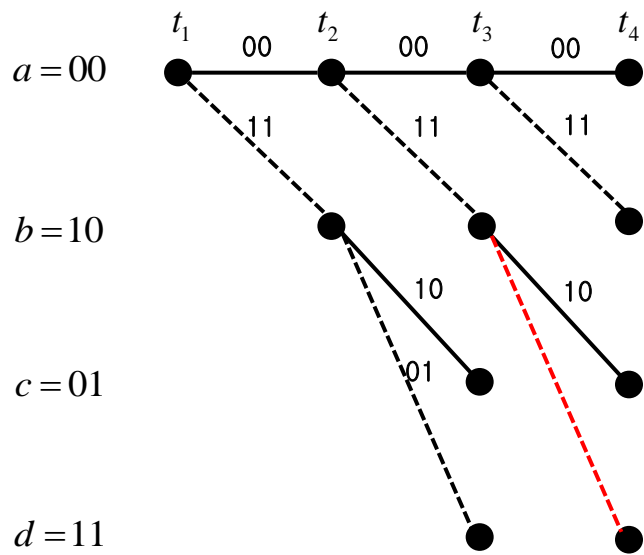
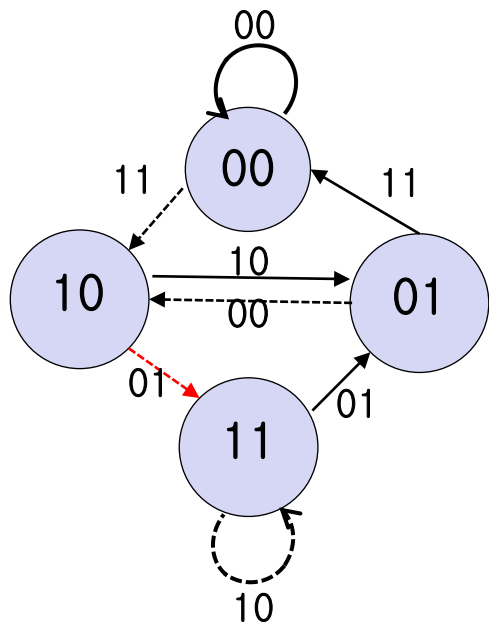


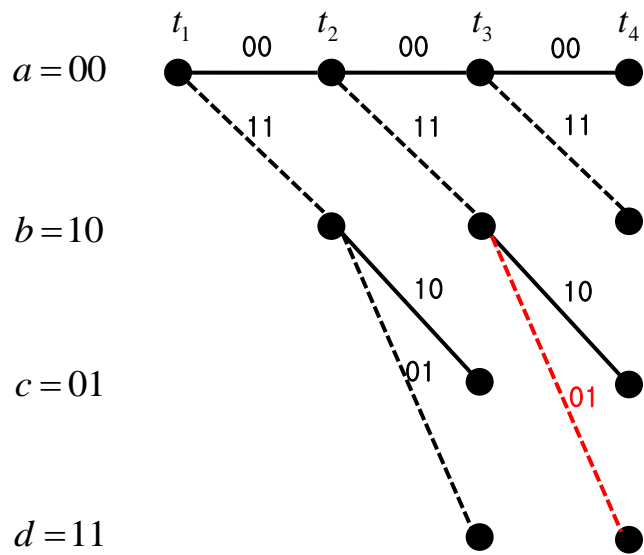
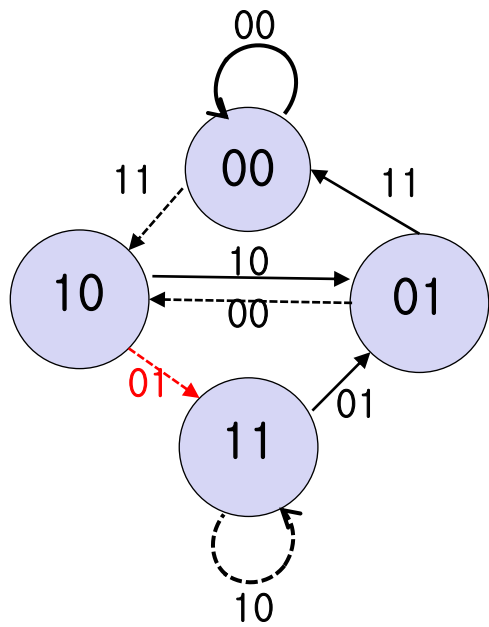


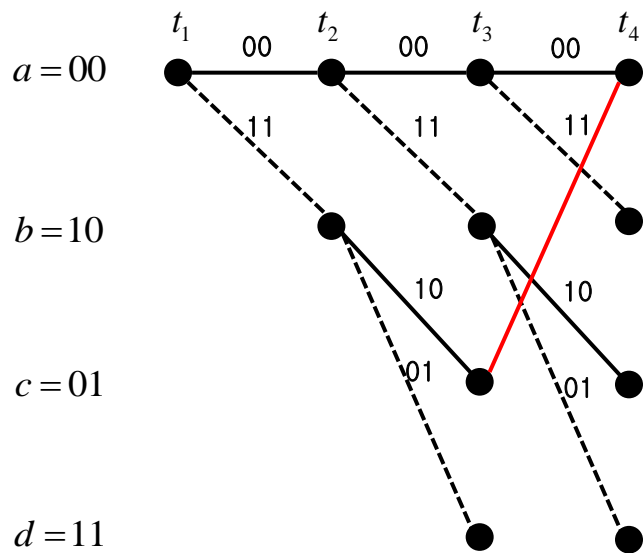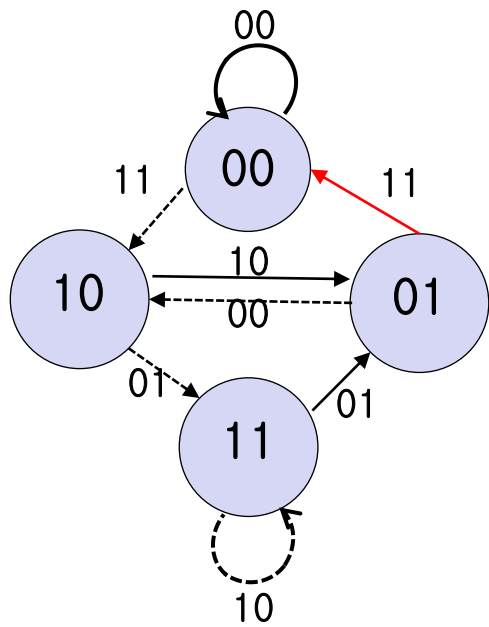

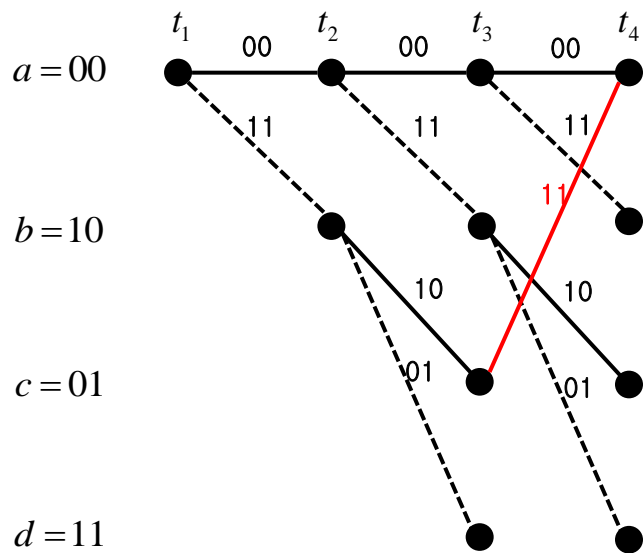
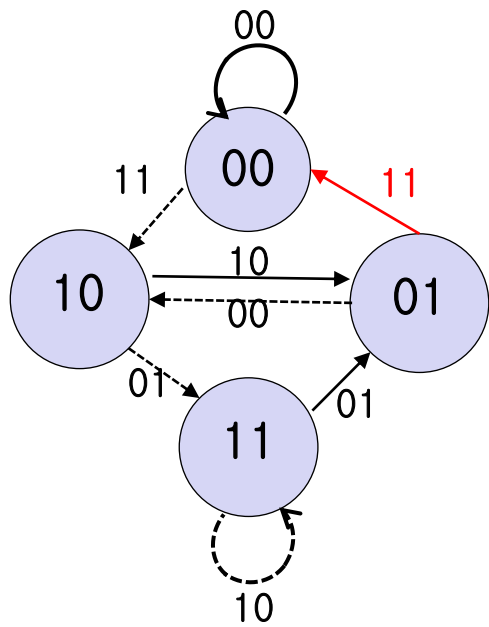


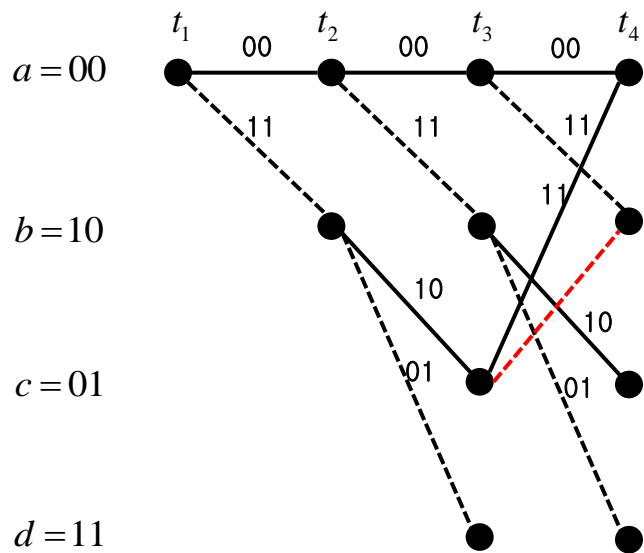
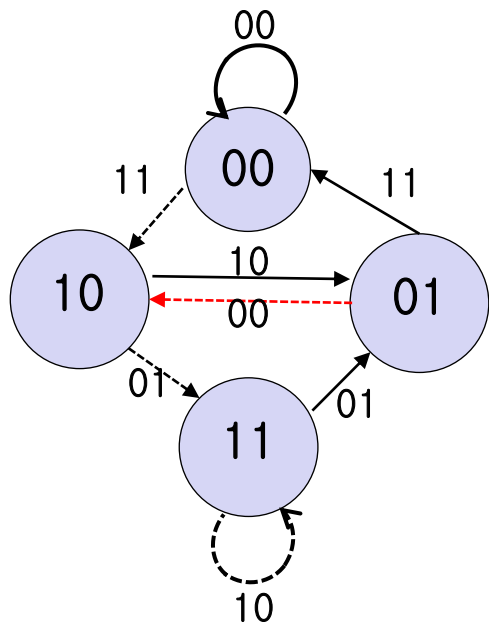


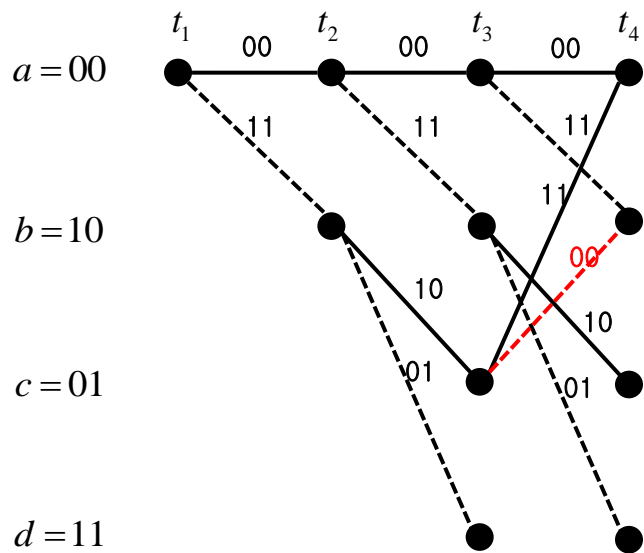
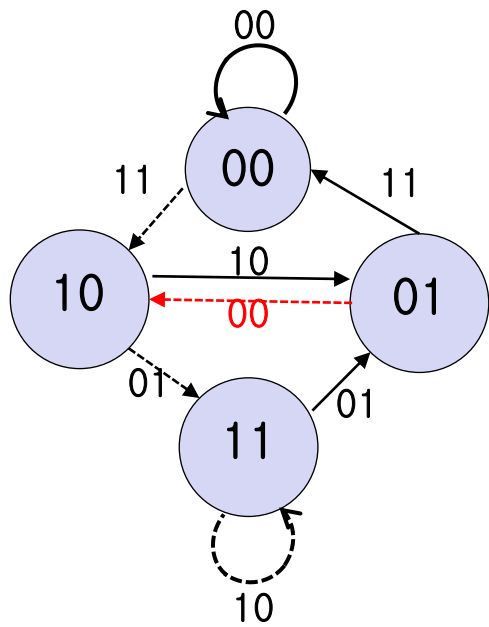


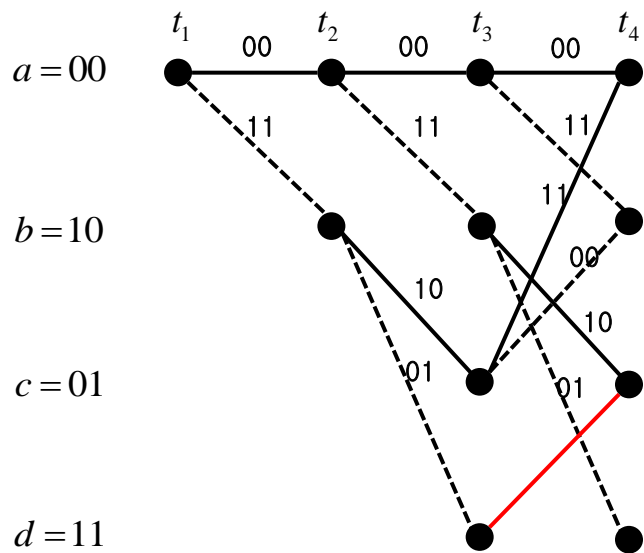
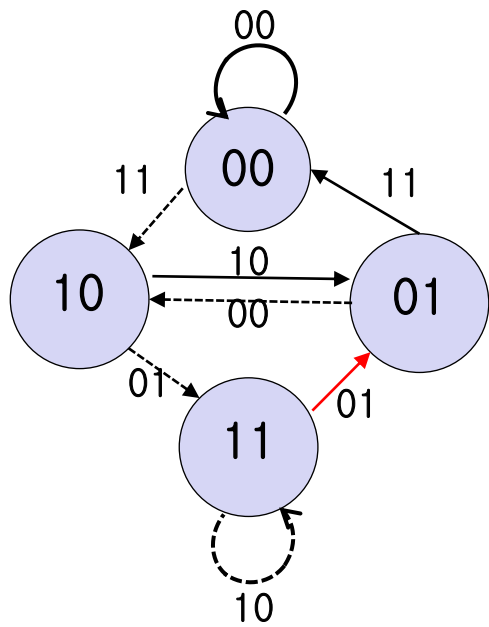






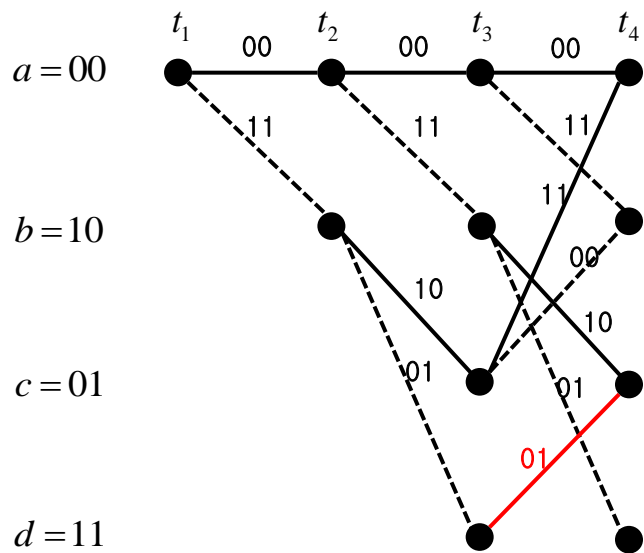
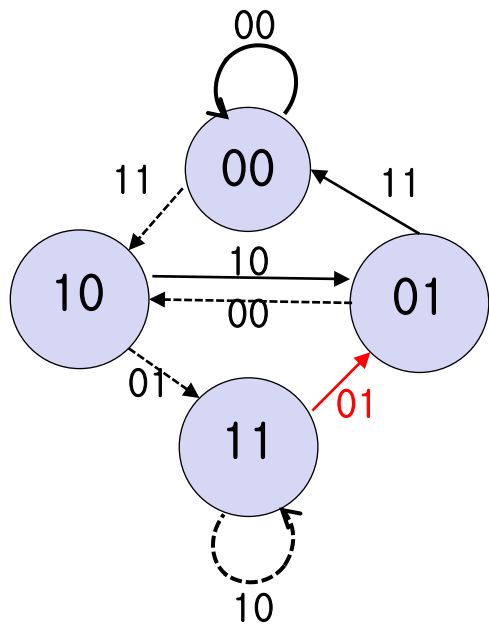


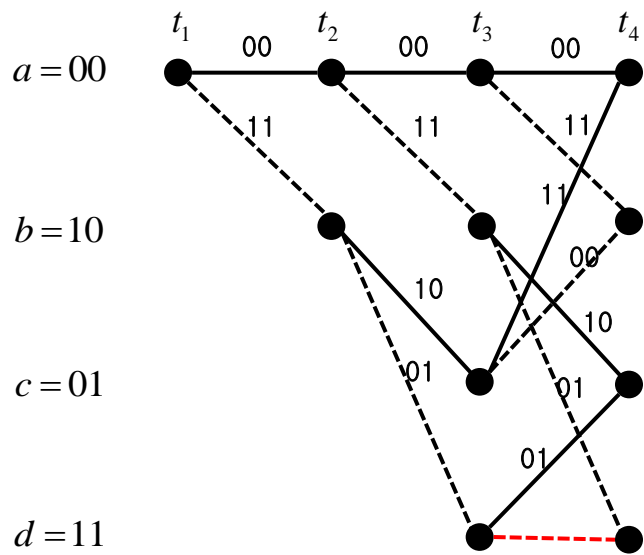
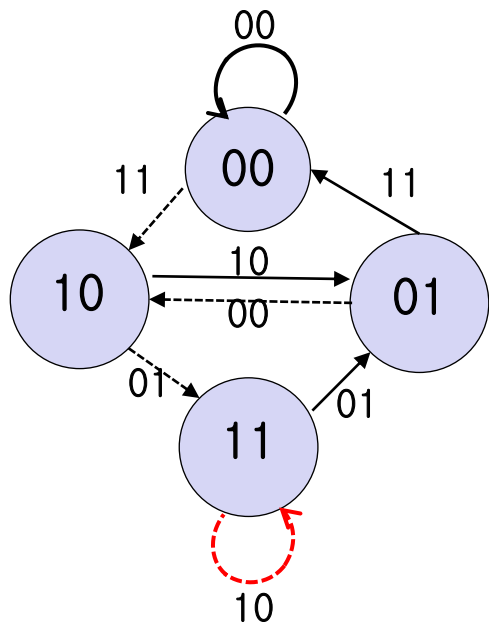


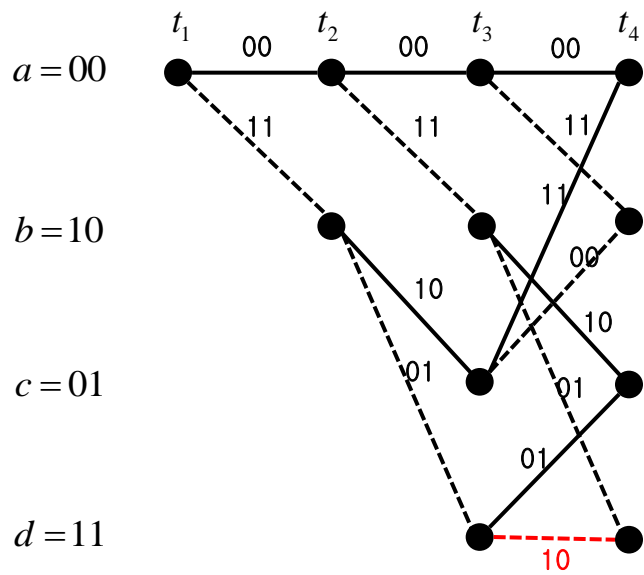
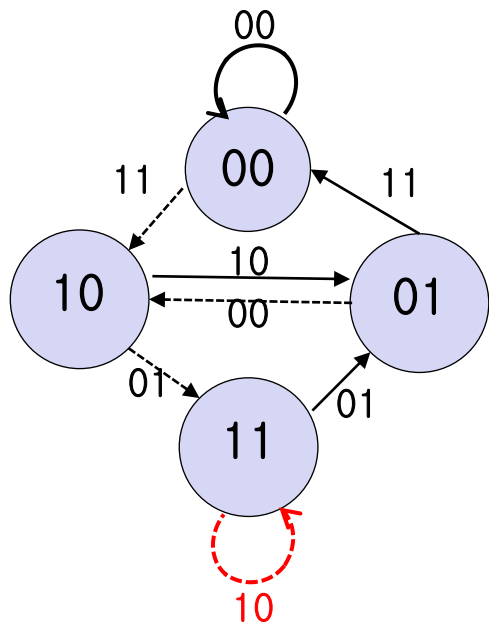


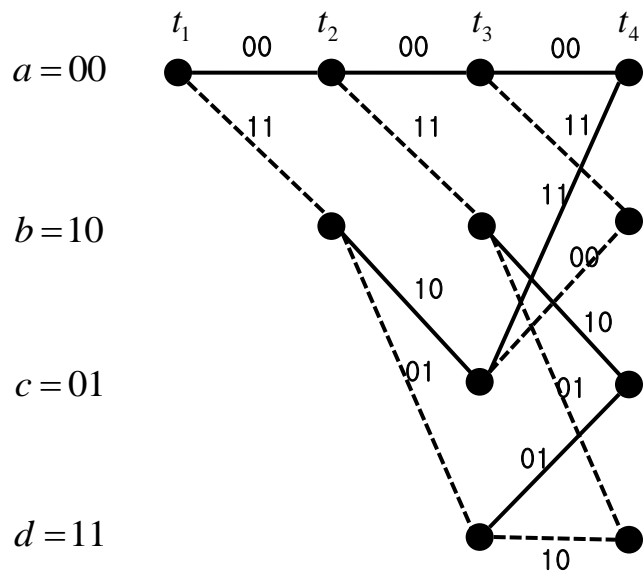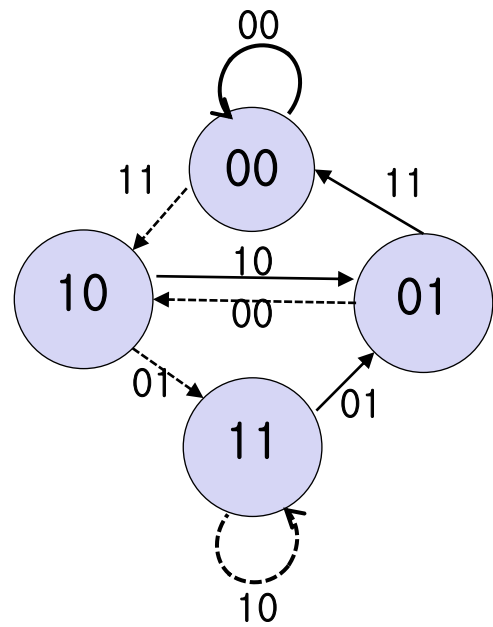

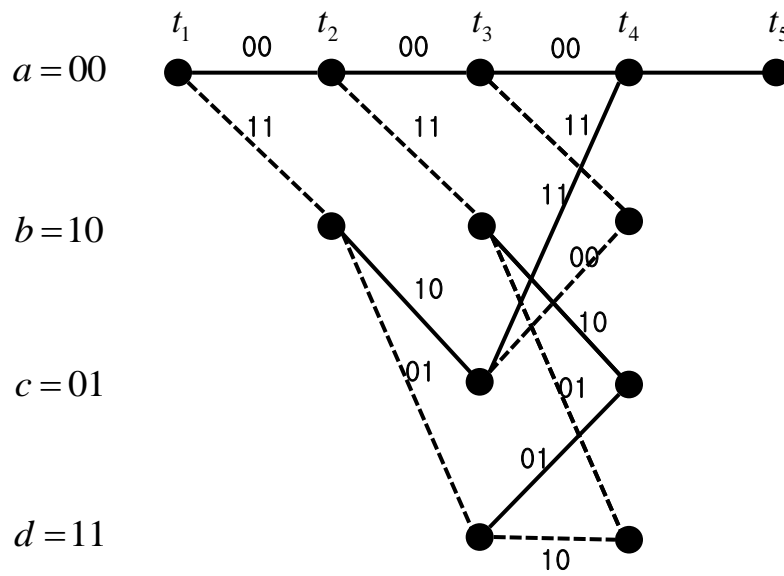
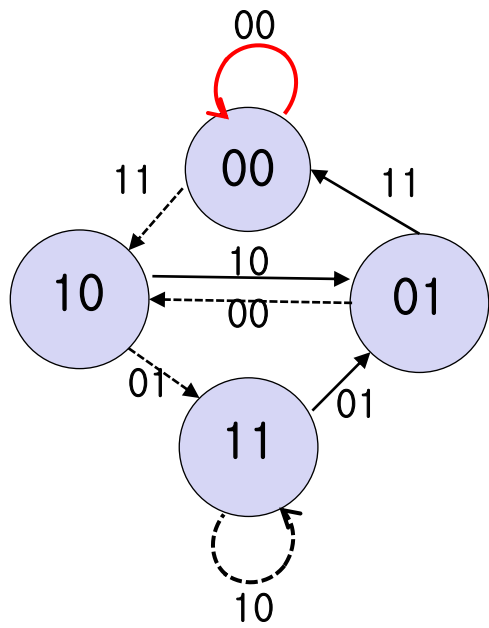


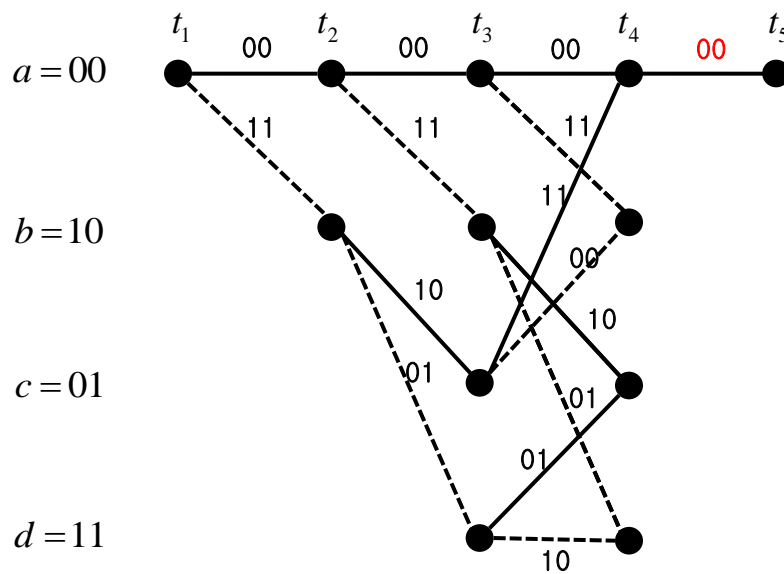
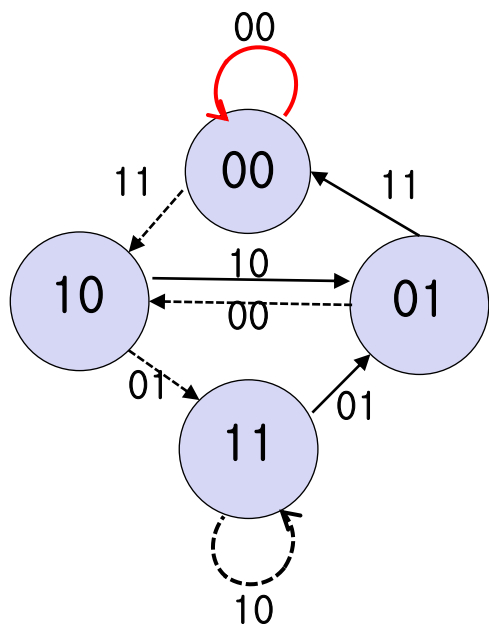


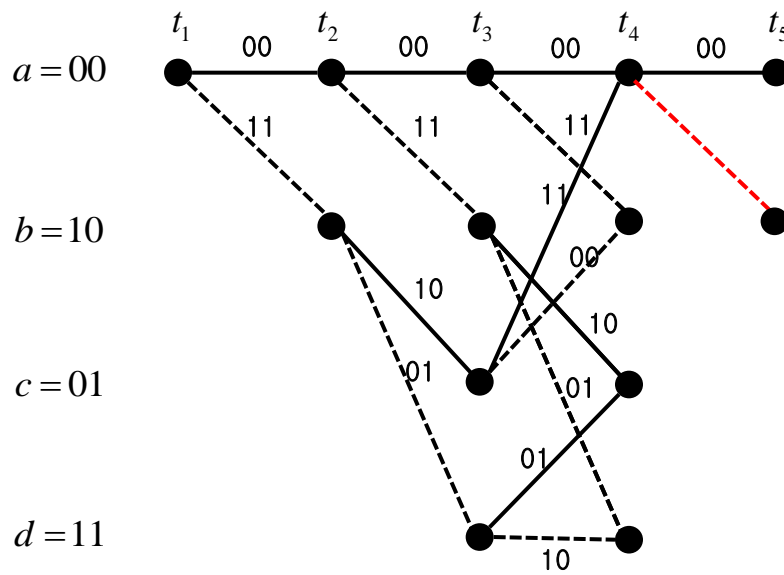
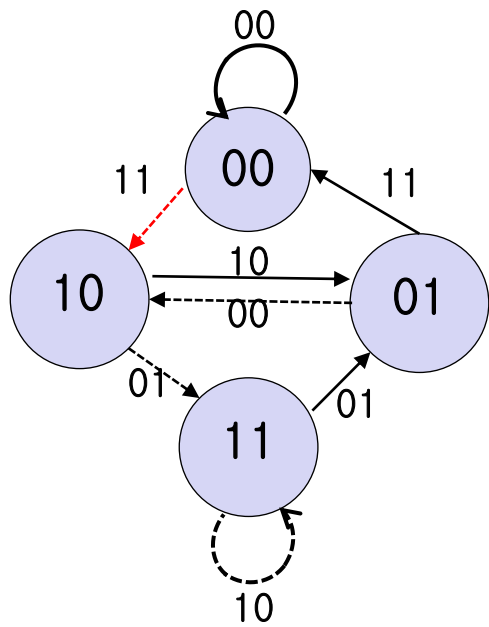


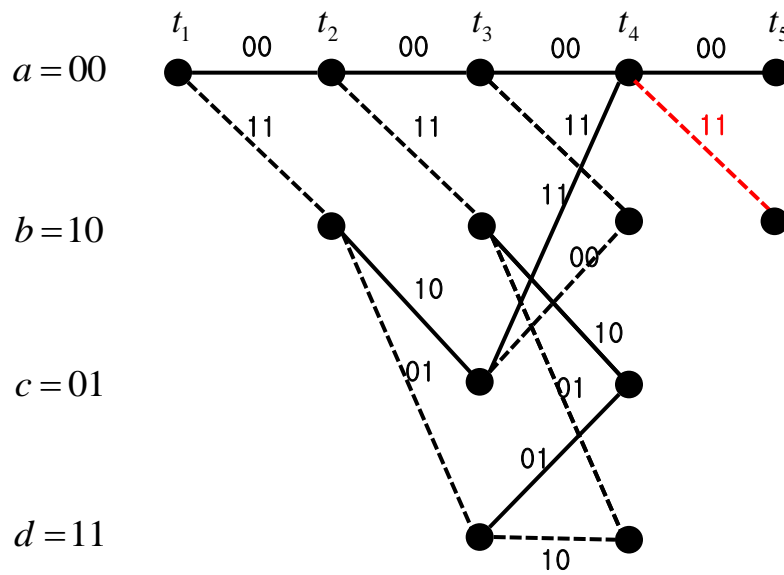
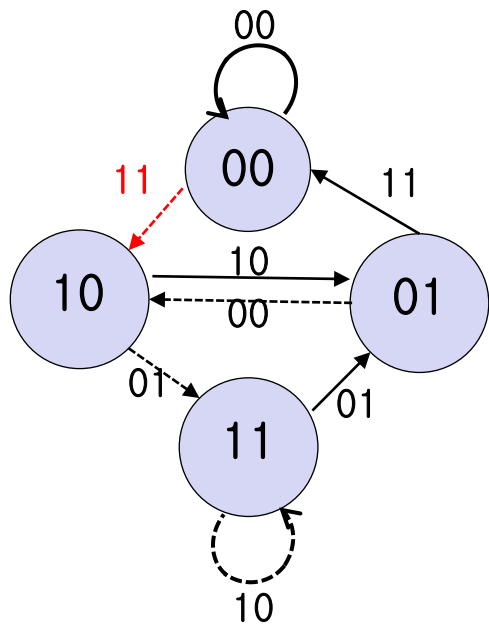






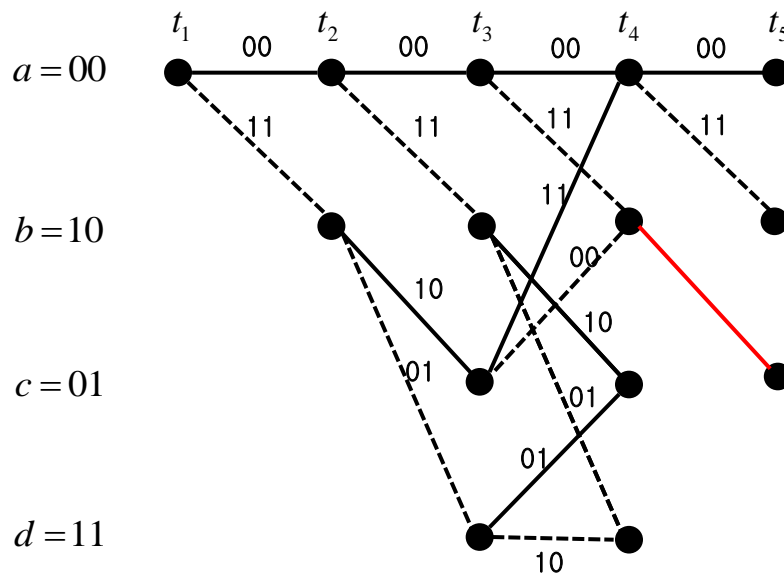
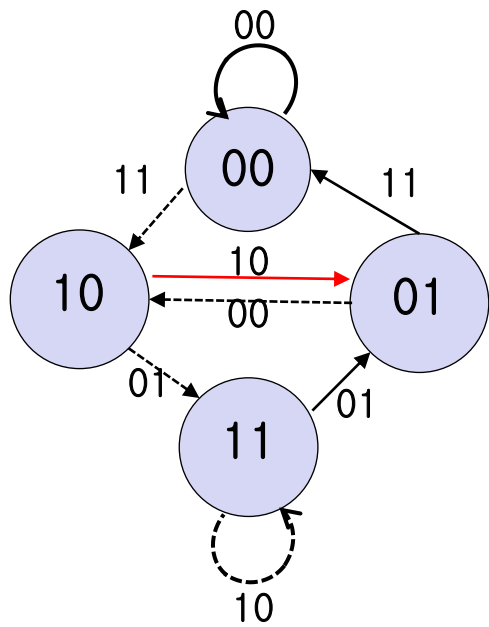


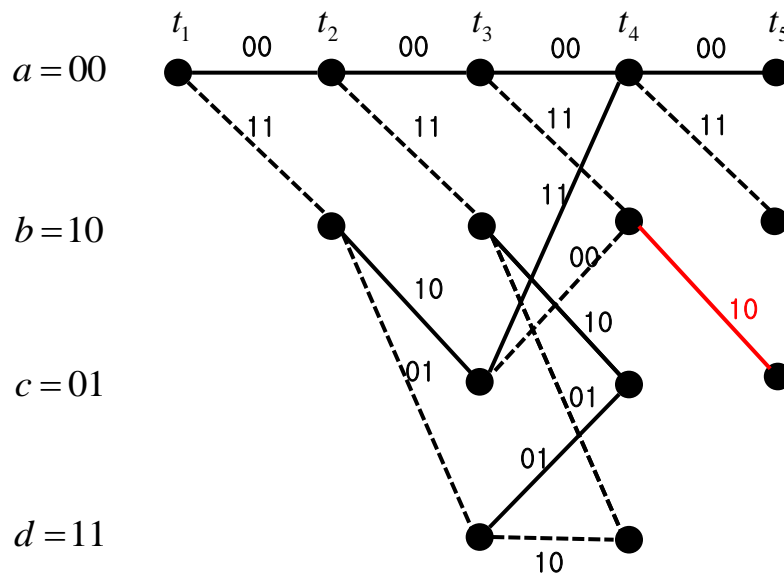
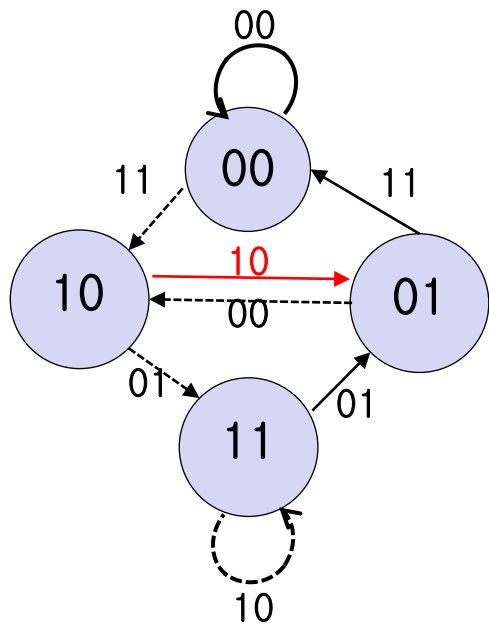


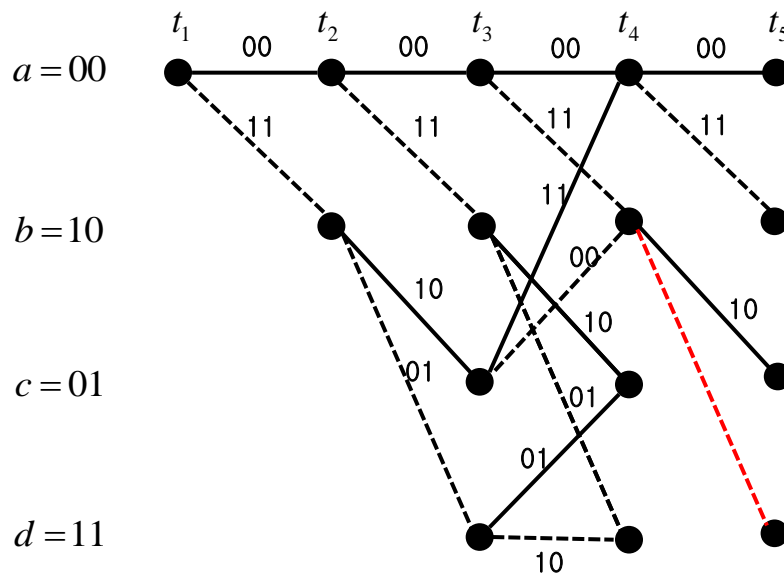
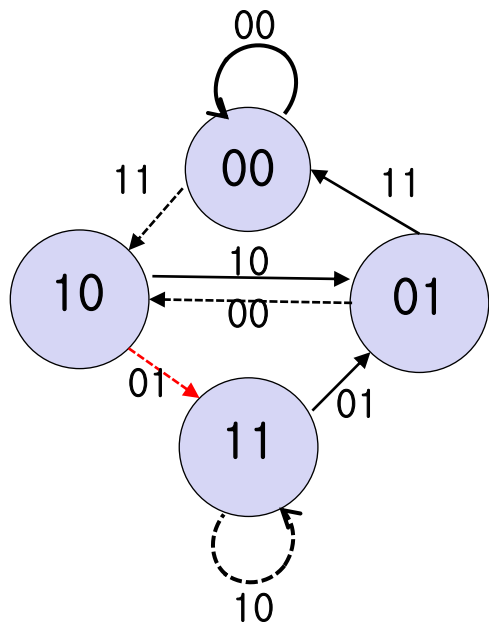


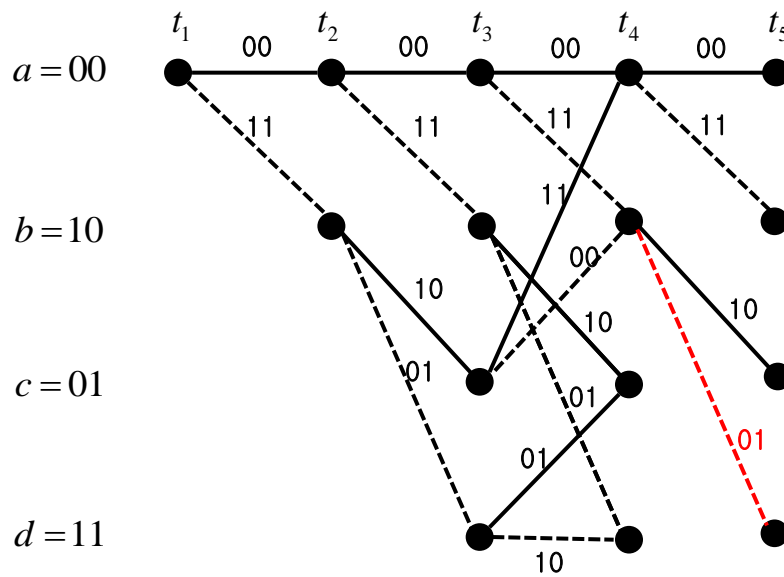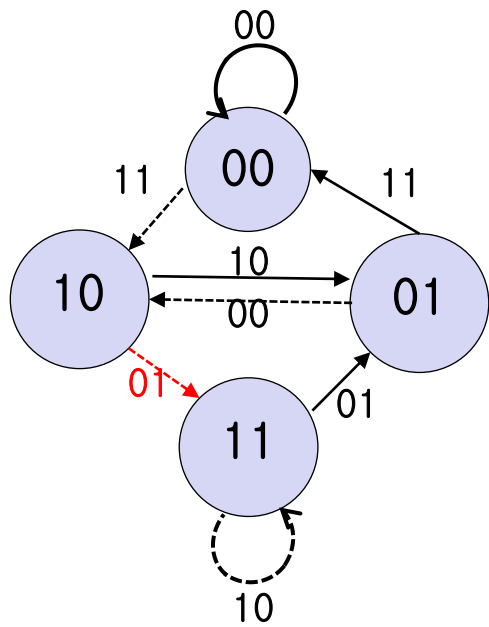

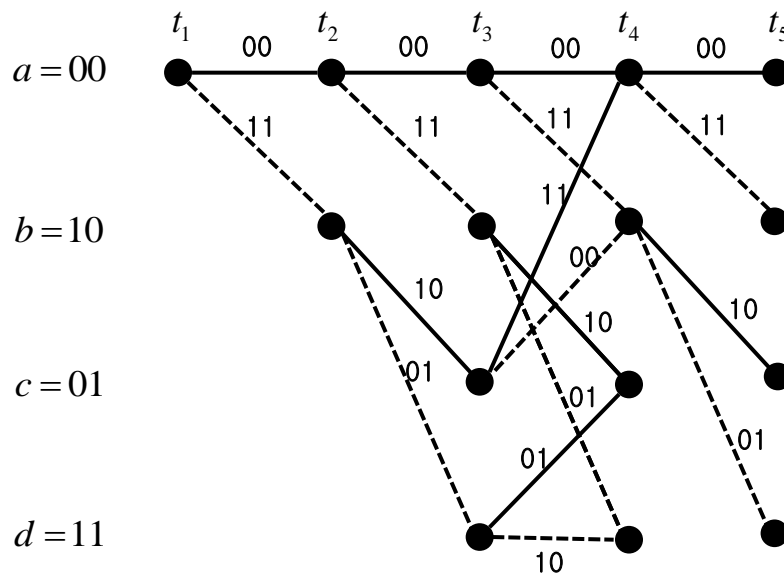
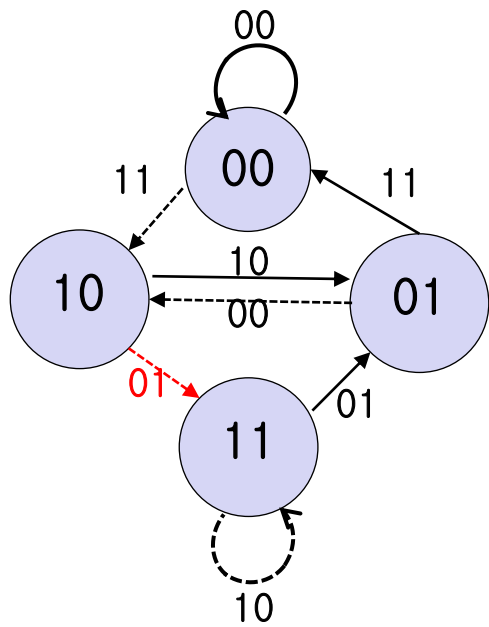


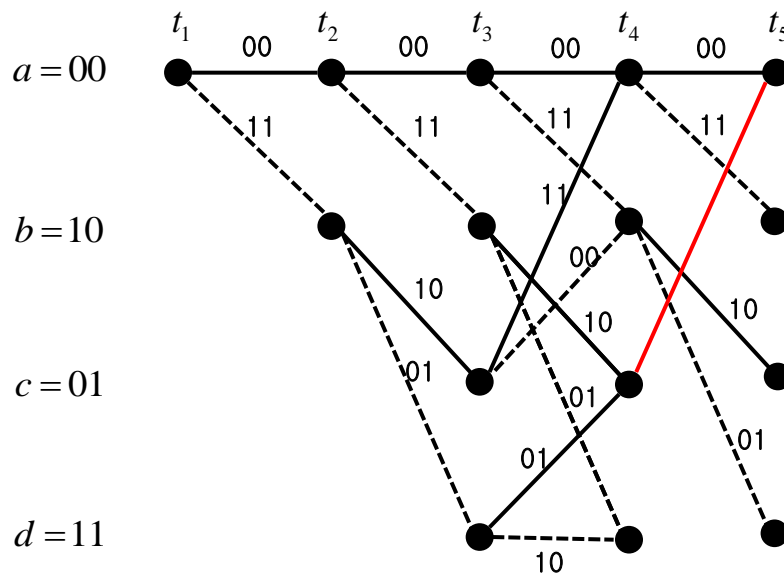
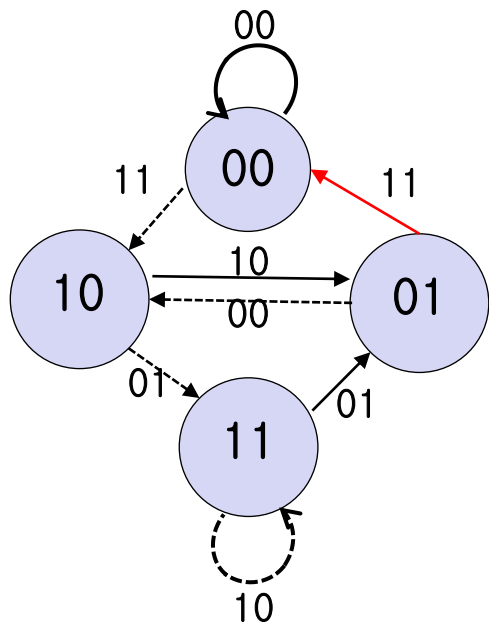


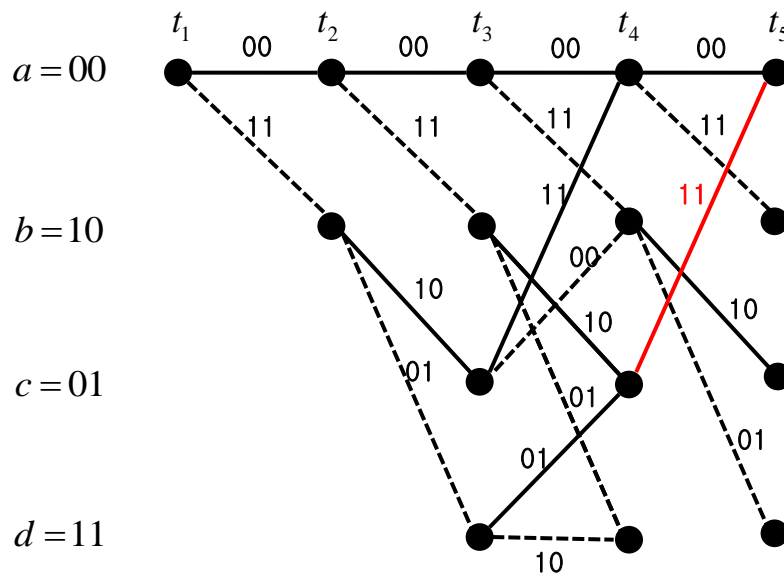
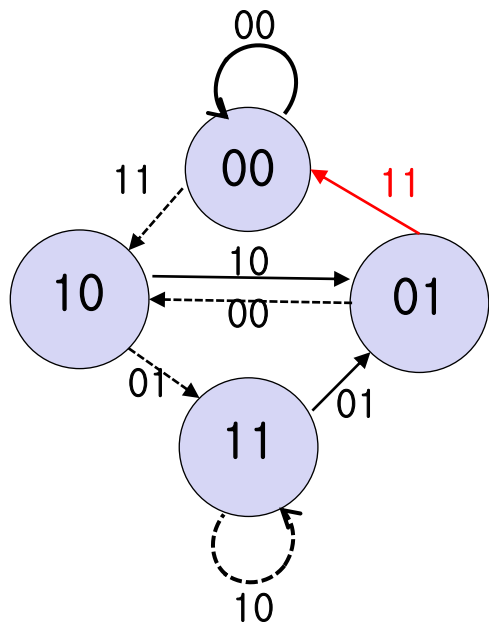


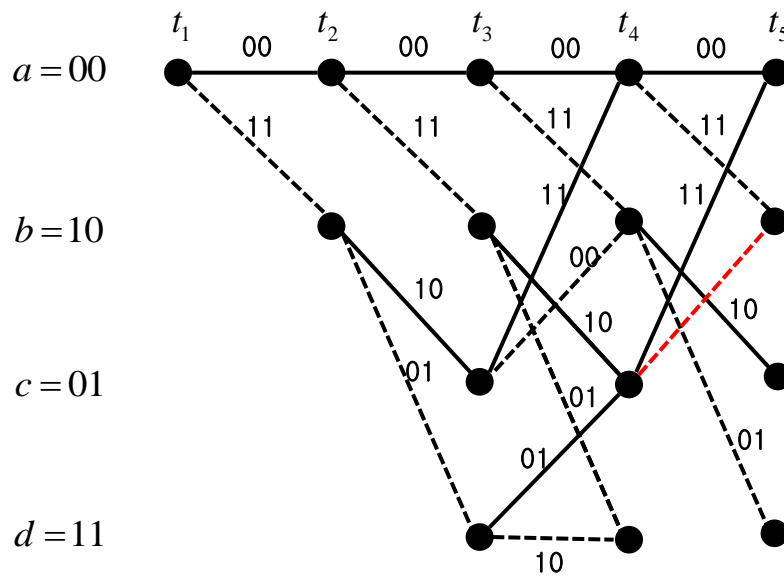
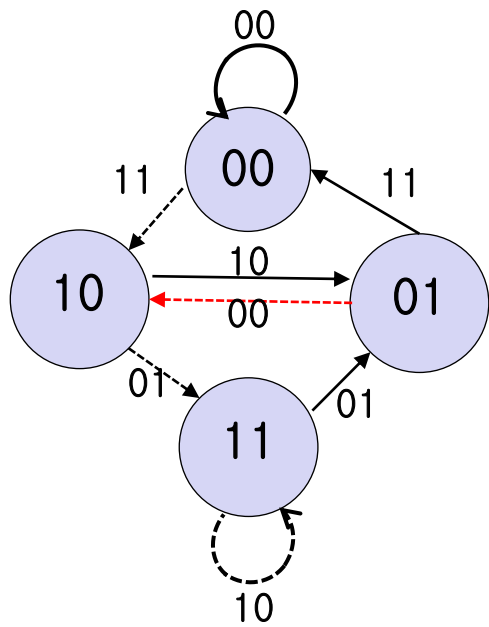






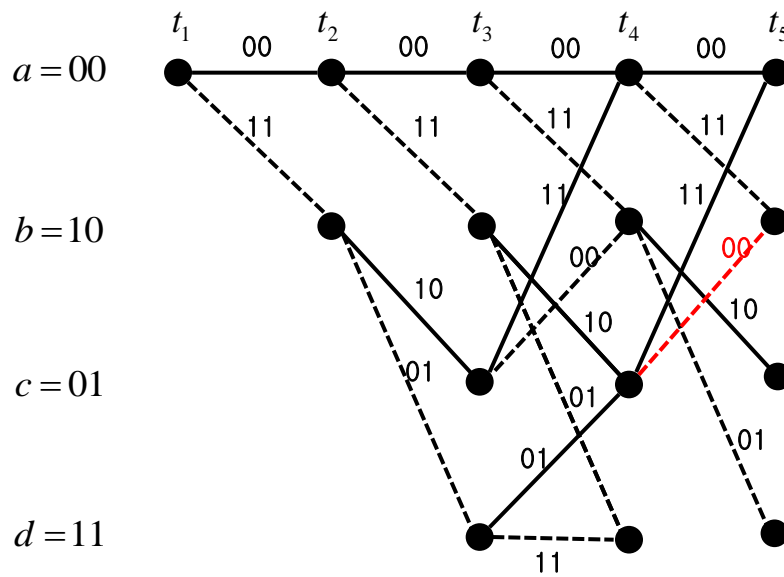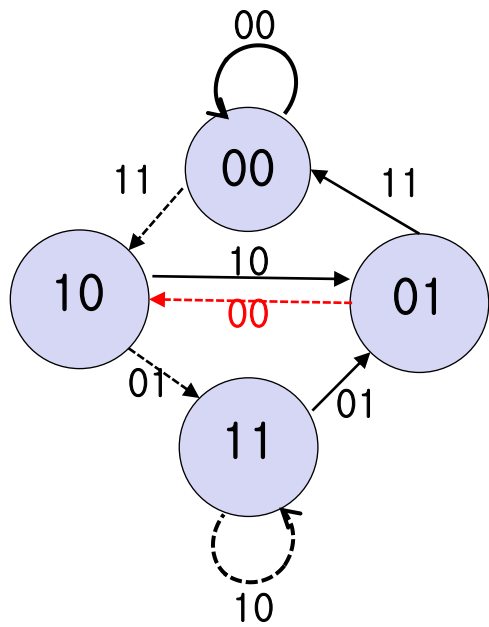

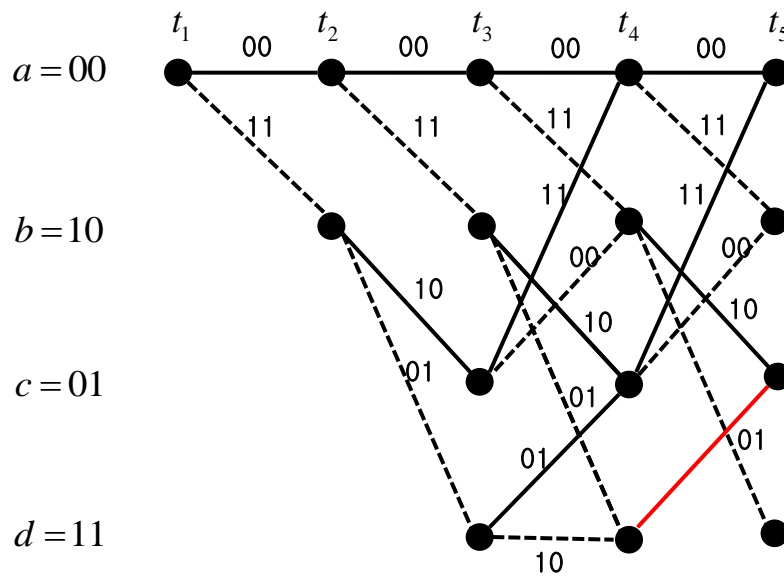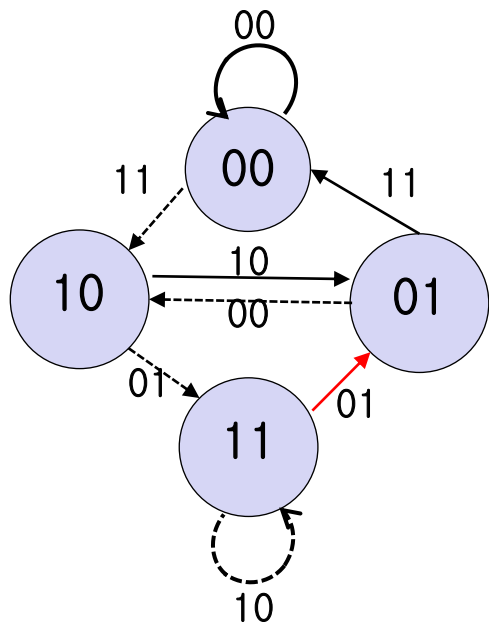

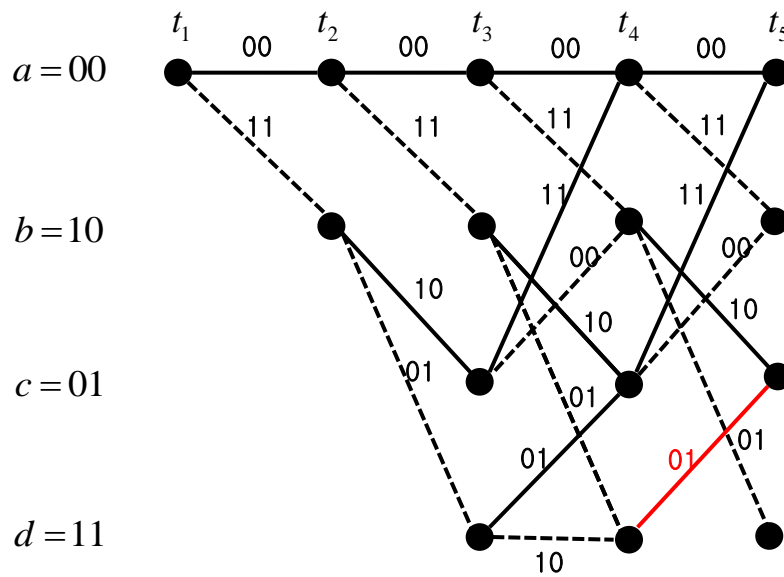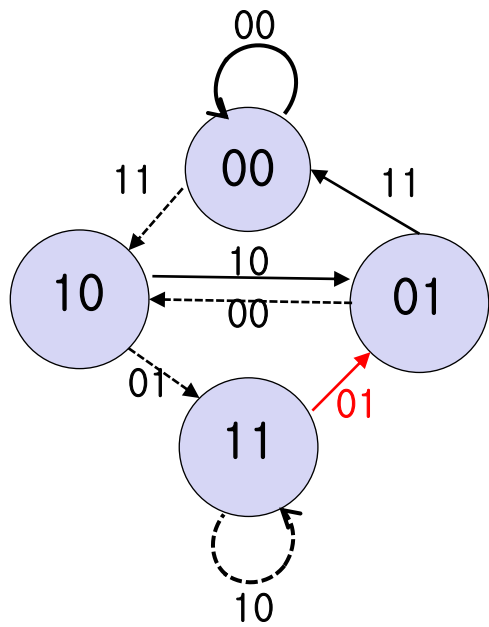

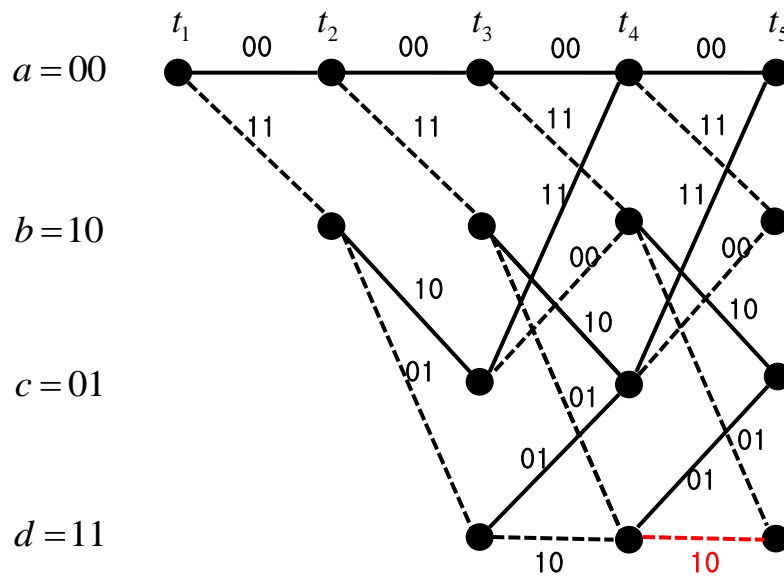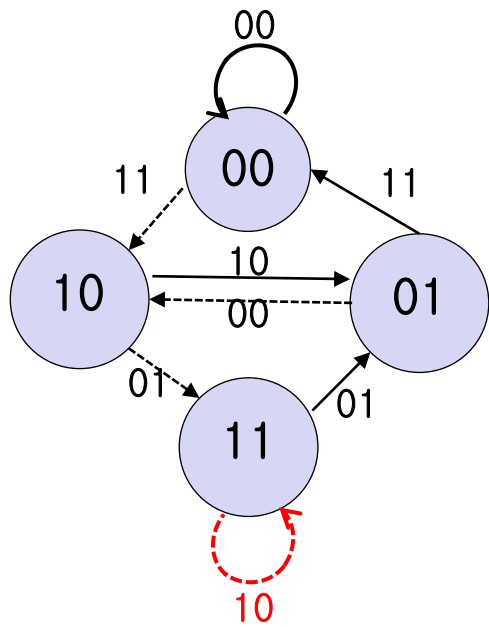


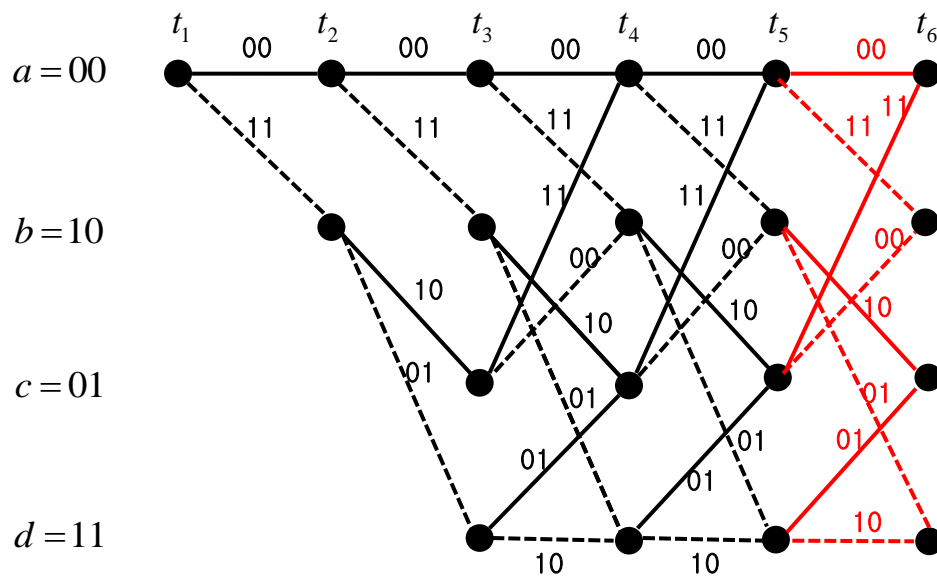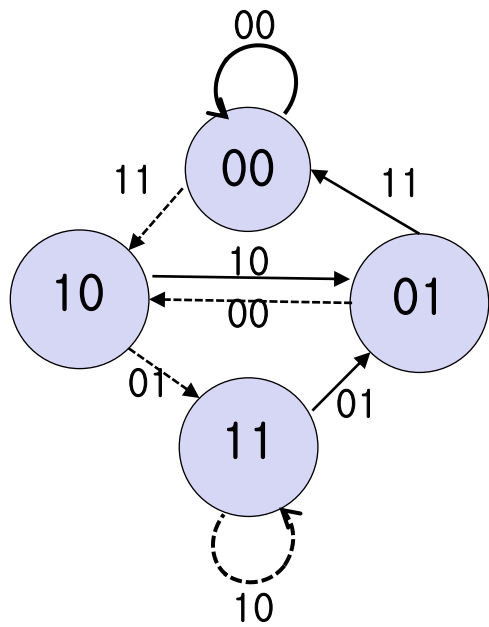


# Viterbi decoding

input data sequence	$m$ :	1	1	0	1	1	...
Transmitted codeword	$U$ :	11	01	01	00	01	...

Received sequence	$Z$ :	11	01	01	10	01	...
-------------------	-------	----	----	----	----	----	-----

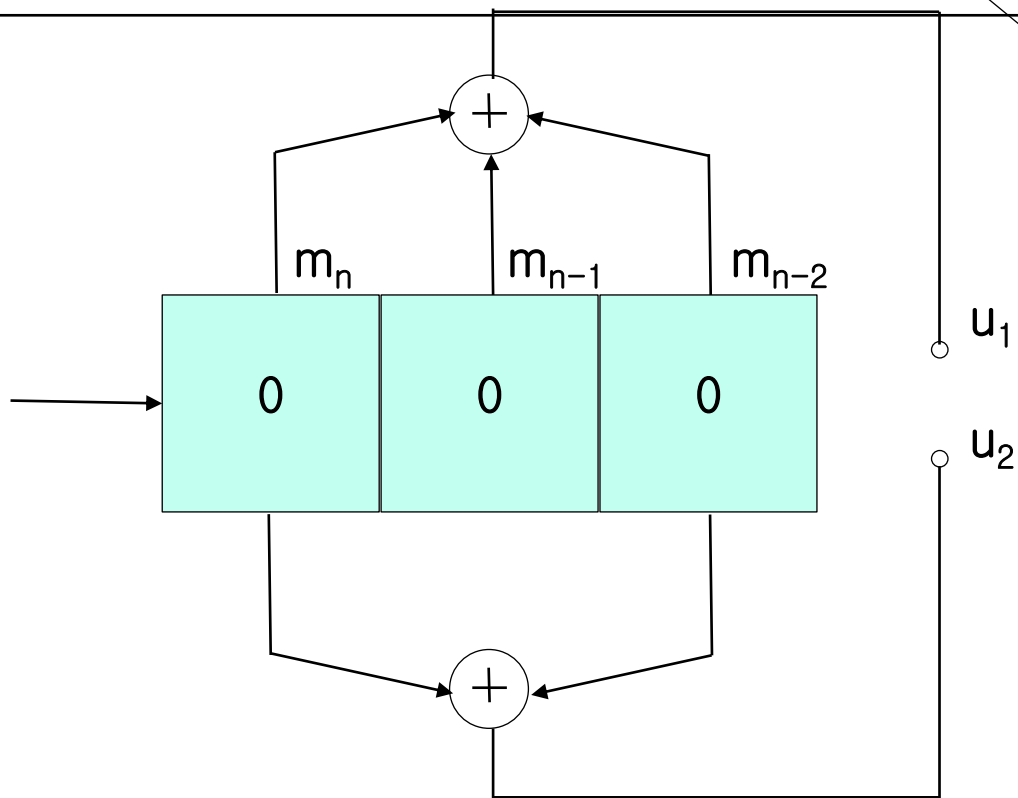


Demodulation error

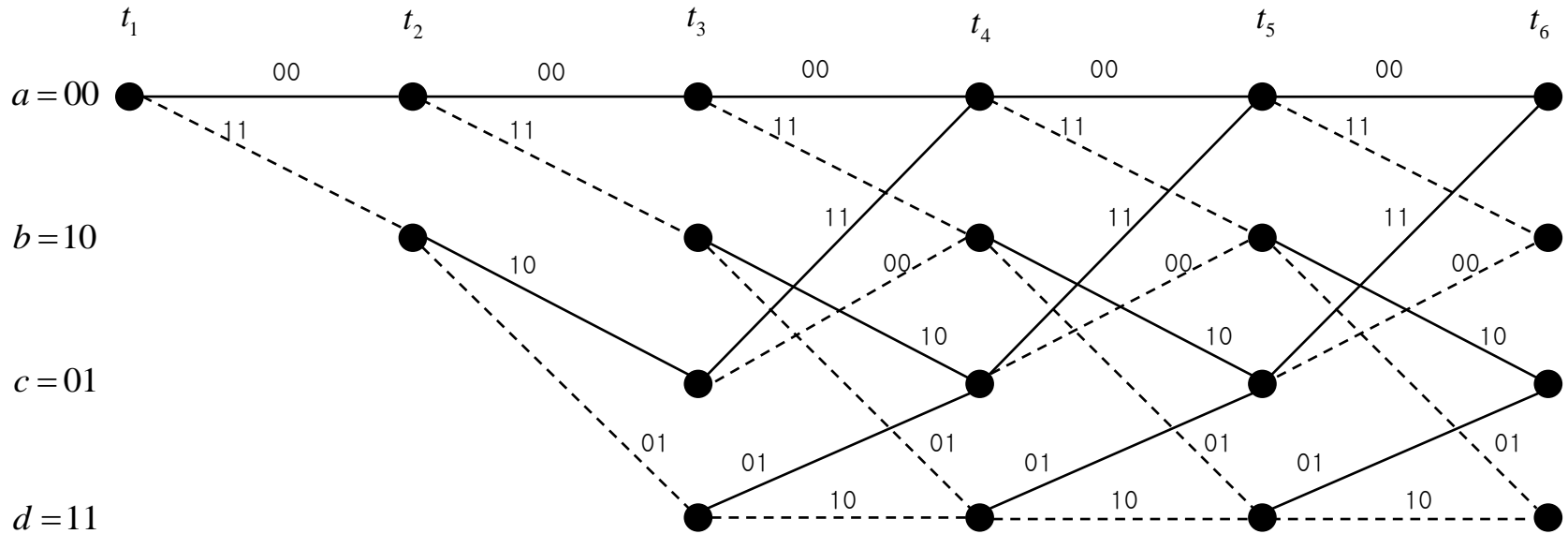

Prepare the trellis diagram.



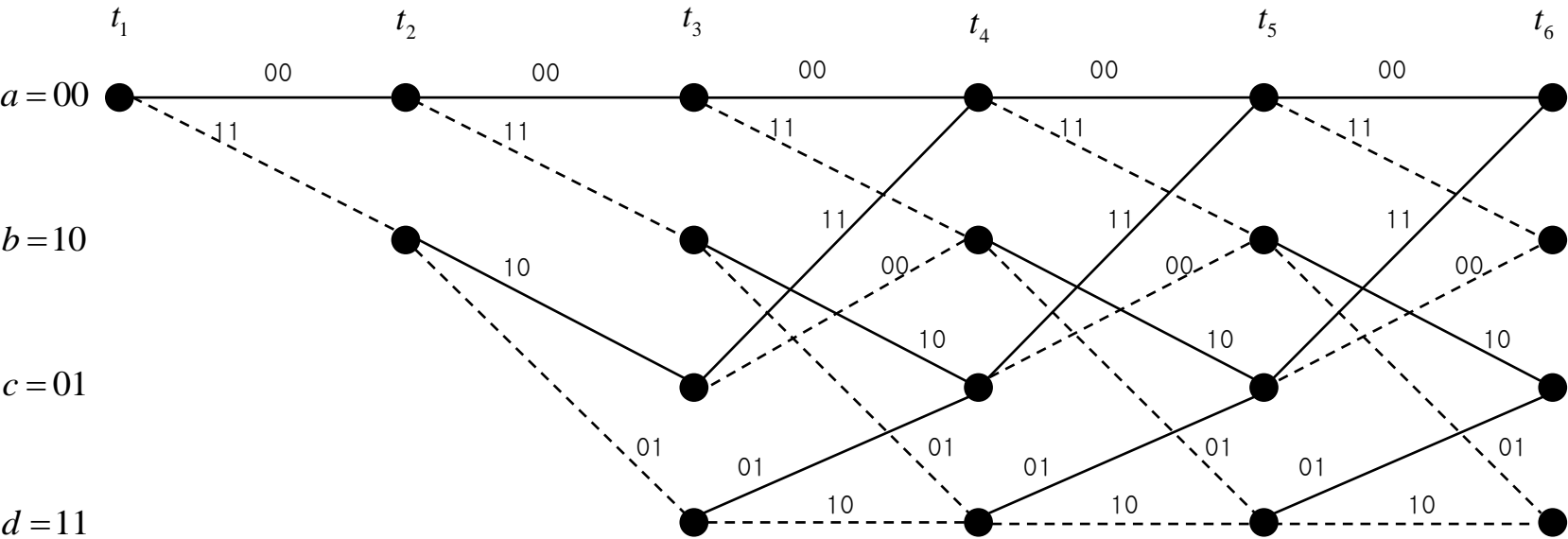
And prepare the table for the accumulated path metrics and the corresponding encoder input(decoder output)



	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0					
d2	0					
d3	0					
d4	0					
output1	None					
output2	None					
output3	None					
output4	None					

Z= decoder input, received (demodulated) sequence.


Z :

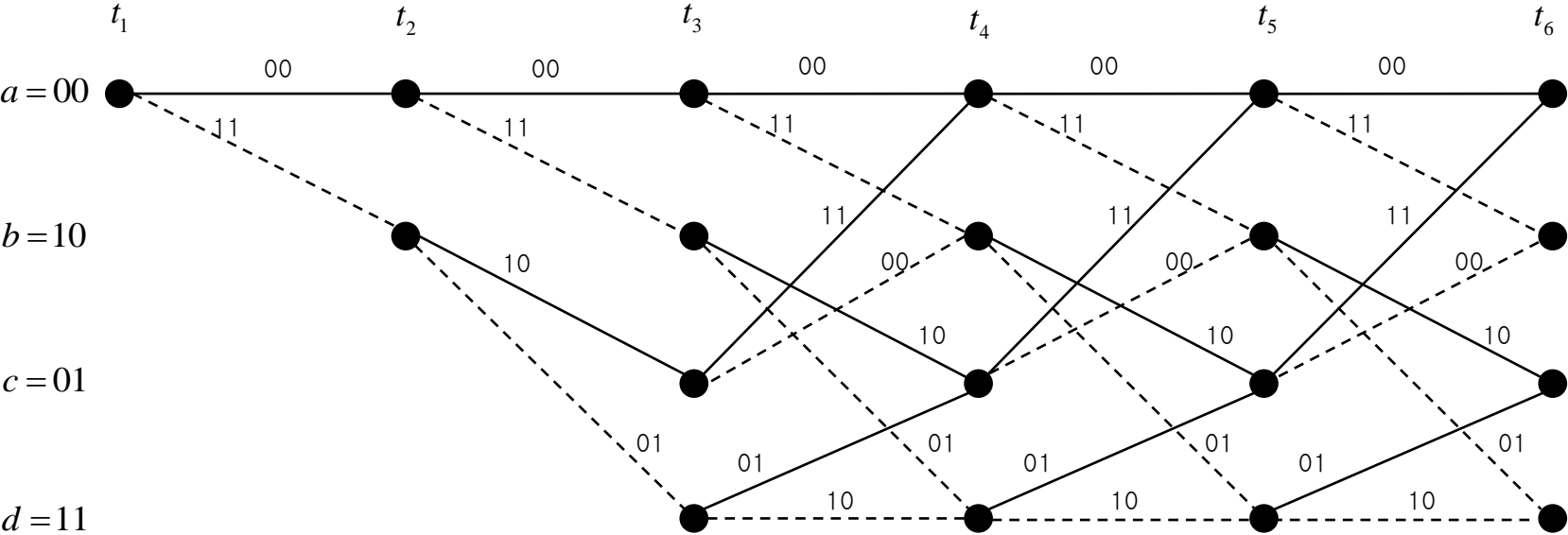

	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0					
d2	0					
d3	0					
d4	0					
output1	None					
output2	None					
output3	None					
output4	None					


Z= decoder input, received (demodulated) sequence.

Z : 11

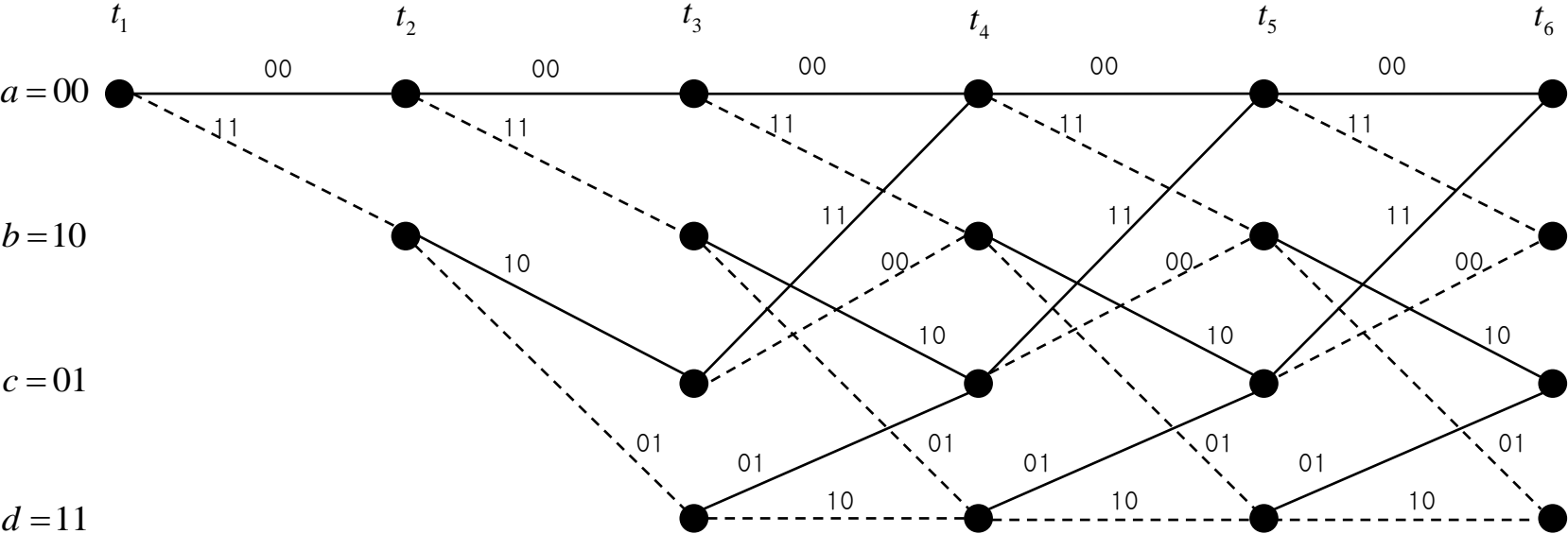


	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0					
d2	0					
d3	0					
d4	0					
output1	None					
output2	None					
output3	None					
output4	None					

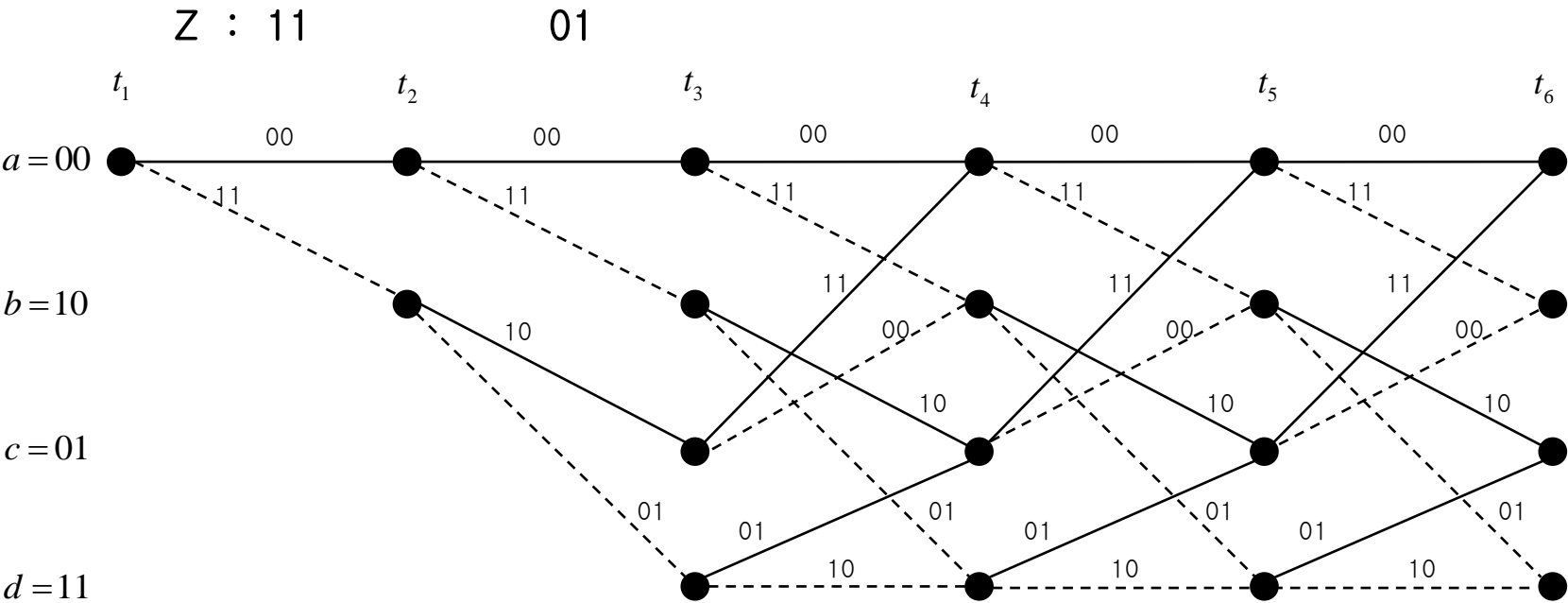Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0					
d2	0					
d3	0					
d4	0					
output1	None					
output2	None					
output3	None					
output4	None					

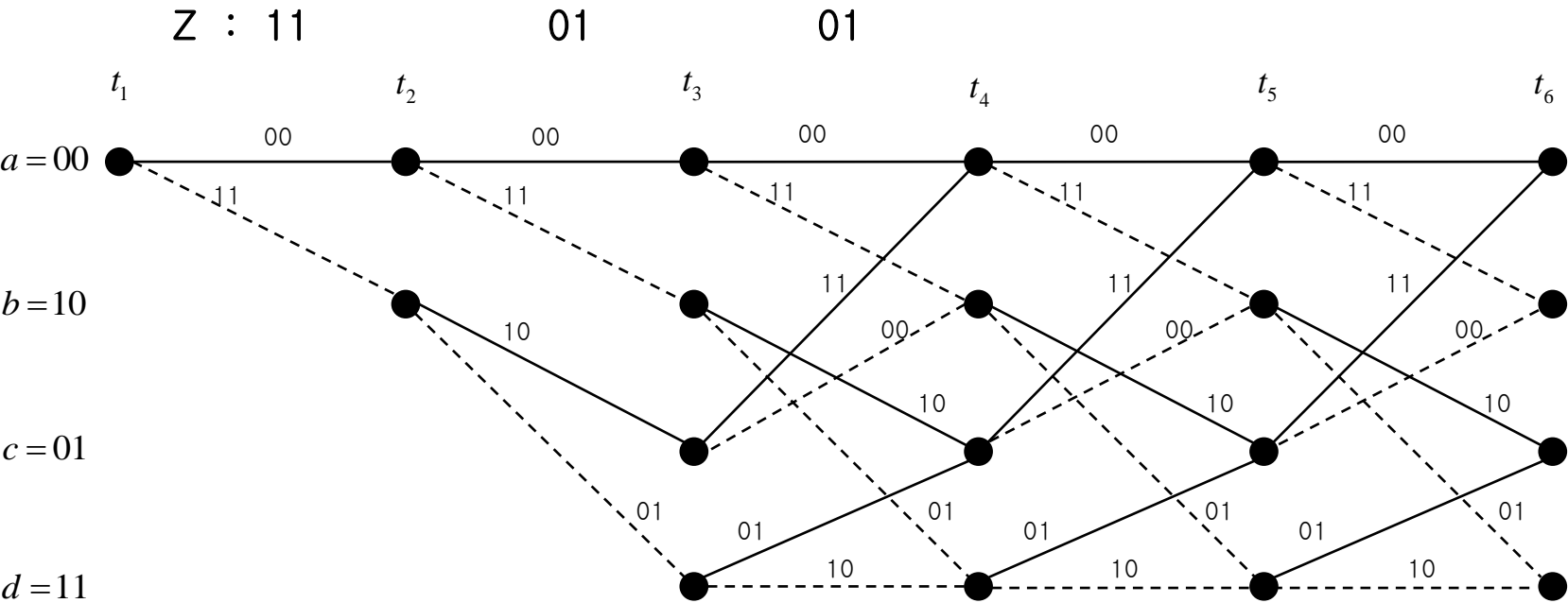Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0					
d2	0					
d3	0					
d4	0					
output1	None					
output2	None					
output3	None					
output4	None					

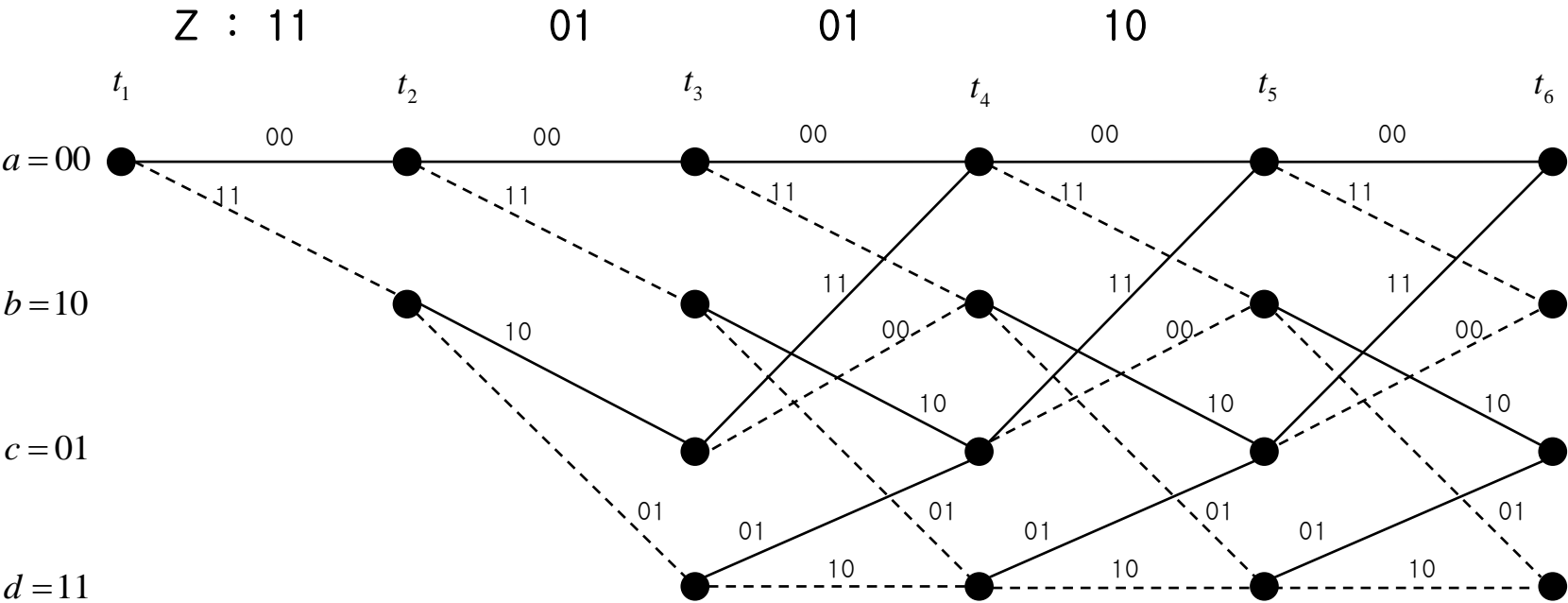Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0					
d2	0					
d3	0					
d4	0					
output1	None					
output2	None					
output3	None					
output4	None					

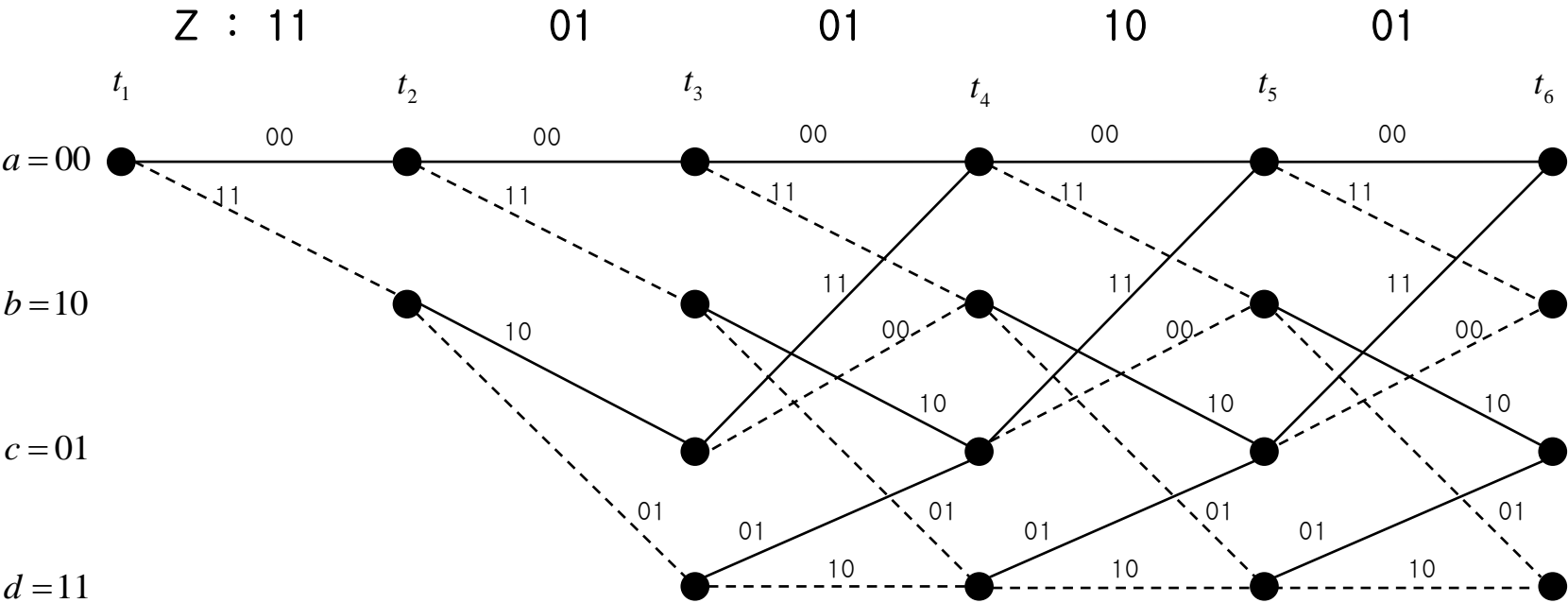Z= decoder input, received (demodulated) sequence.



	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0					
d2	0					
d3	0					
d4	0					
output1	None					
output2	None					
output3	None					
output4	None					

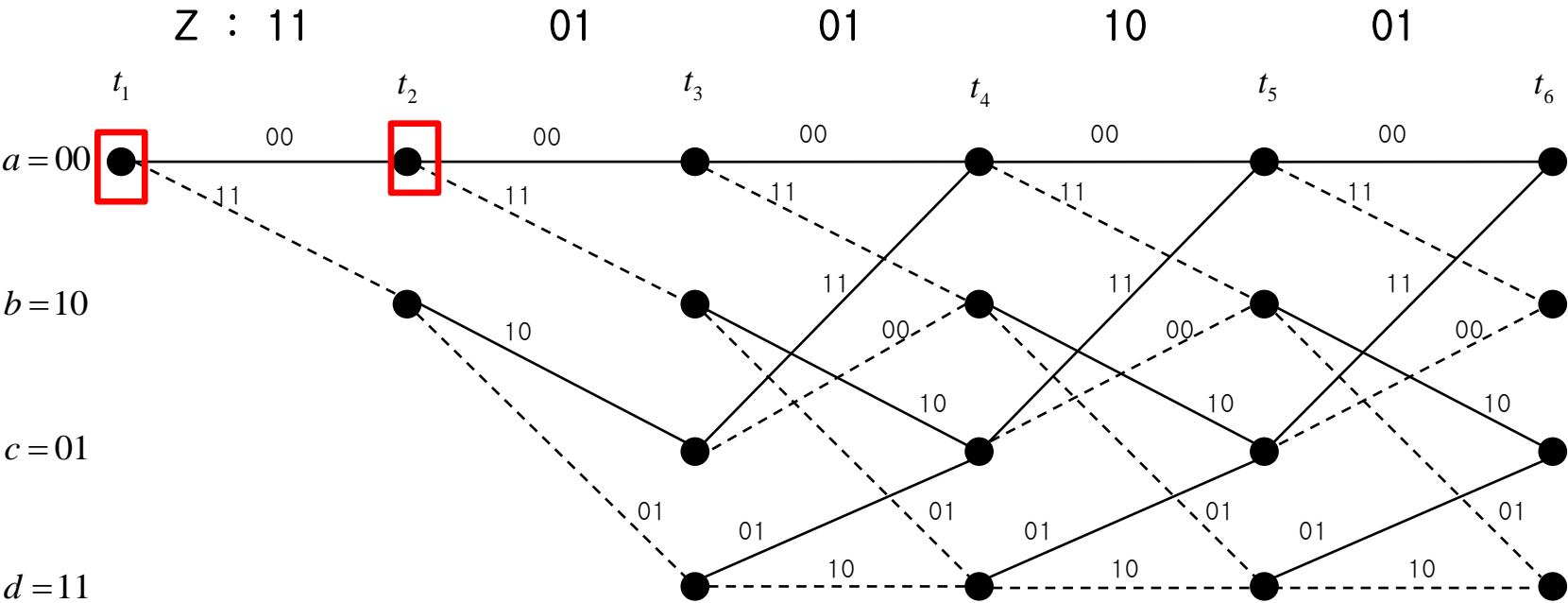
Z= decoder input, received (demodulated) sequence.



	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0					
d2	0					
d3	0					
d4	0					
output1	None					
output2	None					
output3	None					
output4	None					




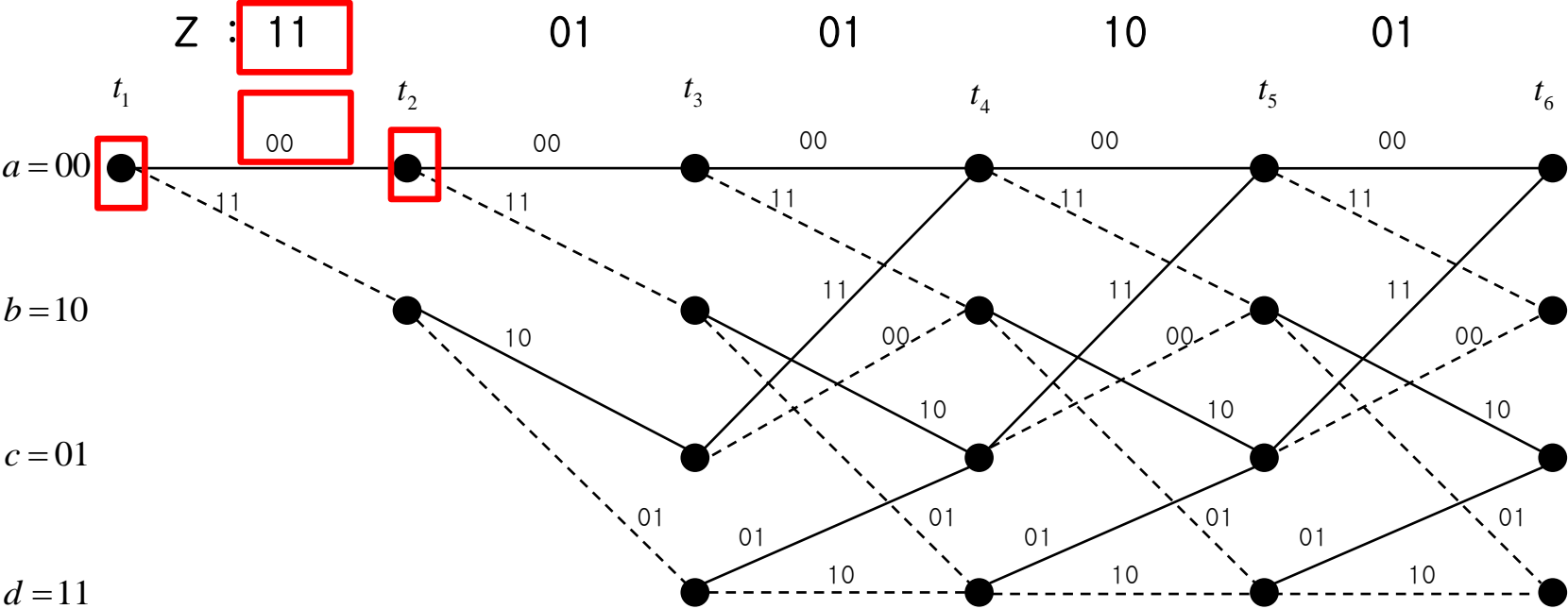Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0					
d2	0					
d3	0					
d4	0					
output1	None					
output2	None					
output3	None					
output4	None					

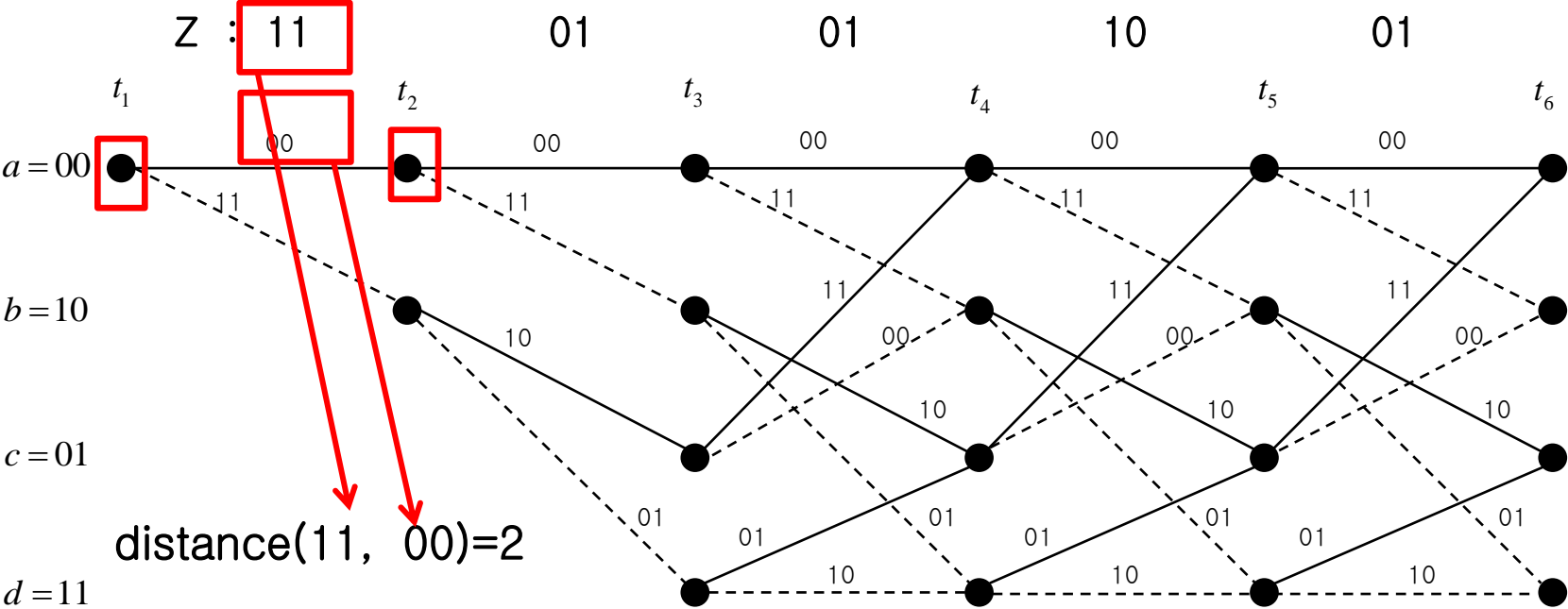Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0					
d2	0					
d3	0					
d4	0					
output1	None					
output2	None					
output3	None					
output4	None					

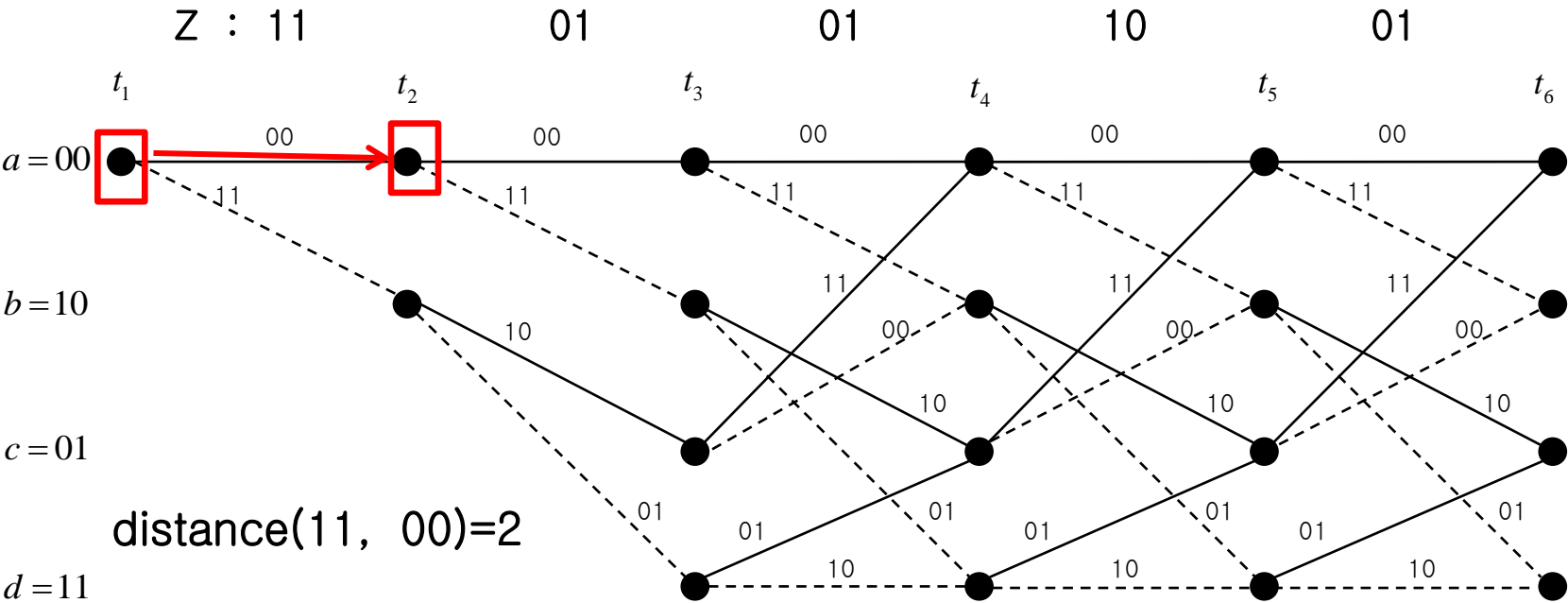Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0 <span style="color:red">→</span>					
d2	0					
d3	0					
d4	0					
output1	None <span style="color:red">→</span>					
output2	None					
output3	None					
output4	None					

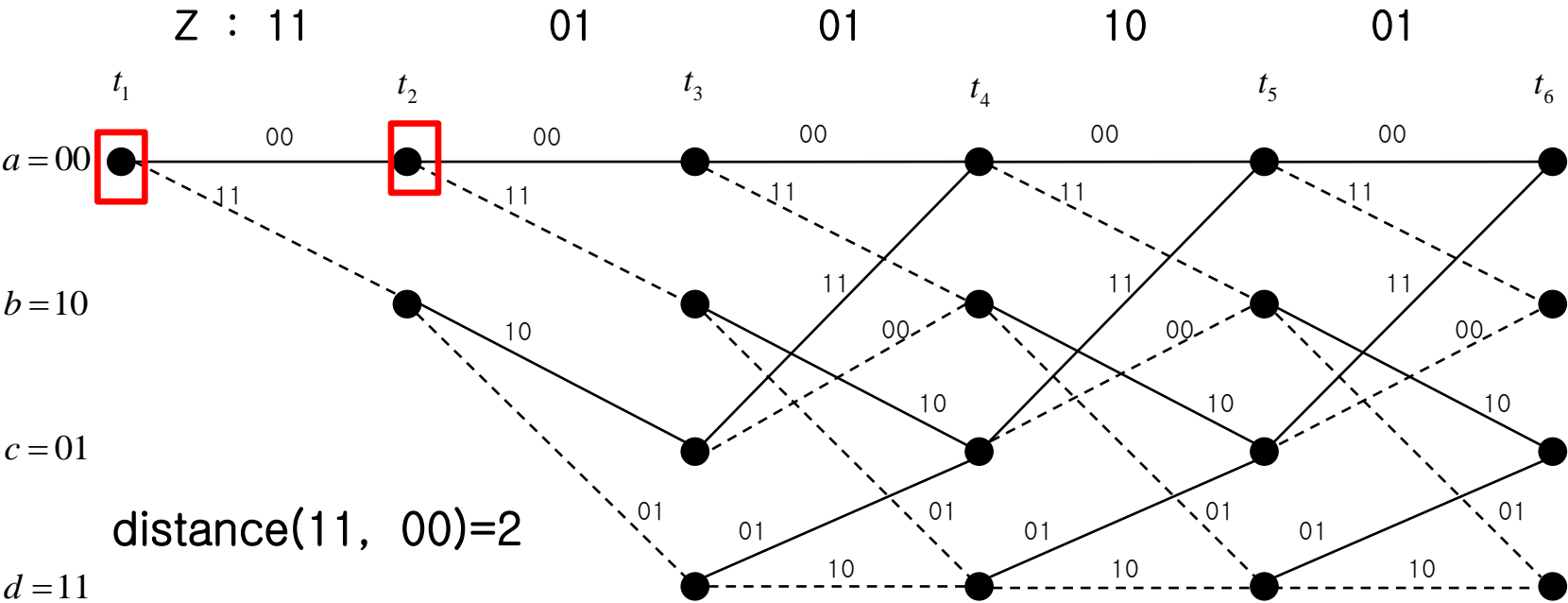Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0					
d2	0					
d3	0					
d4	0					
output1	None					
output2	None					
output3	None					
output4	None					

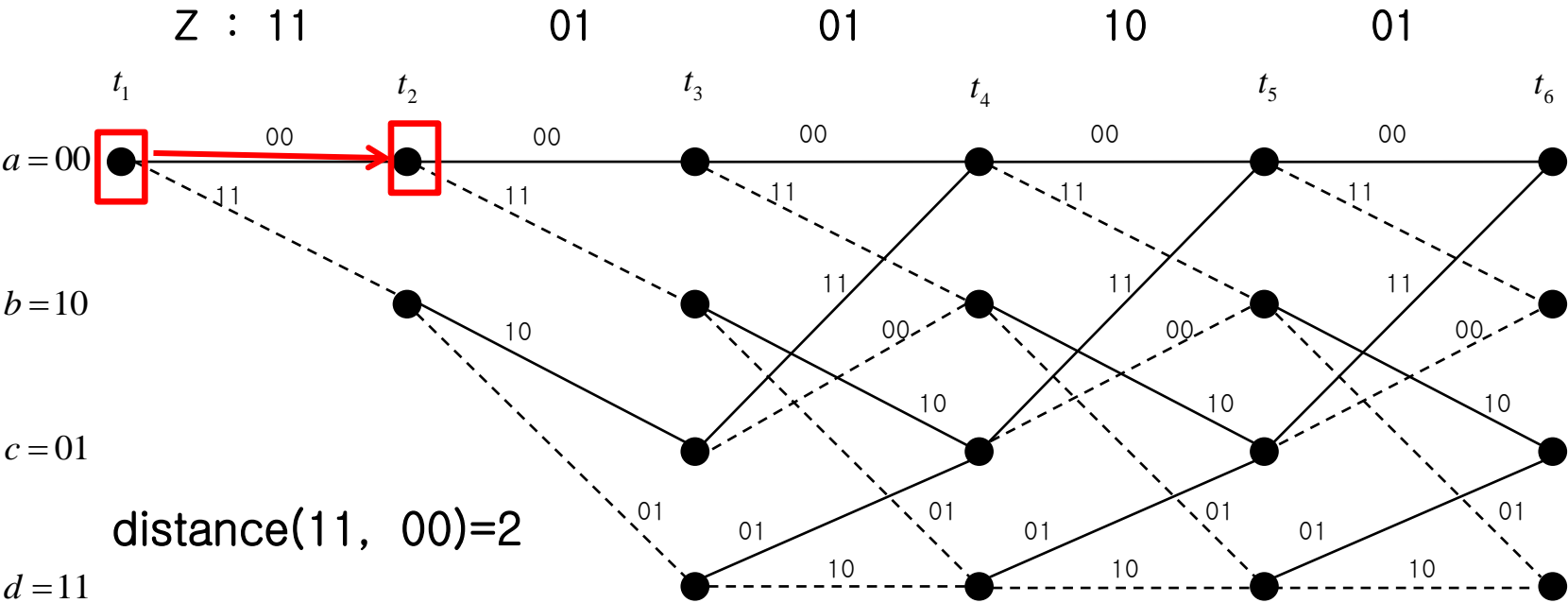Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0 <span style="color:red">→</span>					
d2	0					
d3	0					
d4	0					
output1	None <span style="color:red">→</span>					
output2	None					
output3	None					
output4	None					

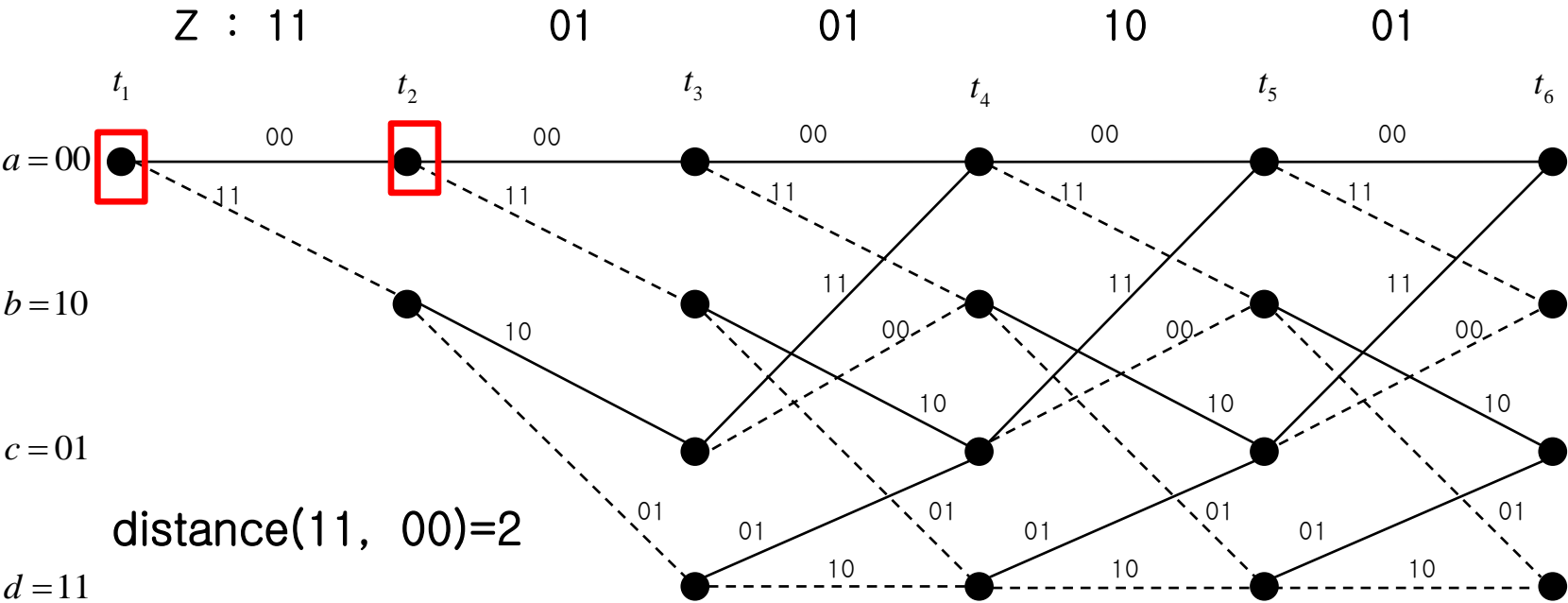Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0					
d2	0					
d3	0					
d4	0					
output1	None					
output2	None					
output3	None					
output4	None					

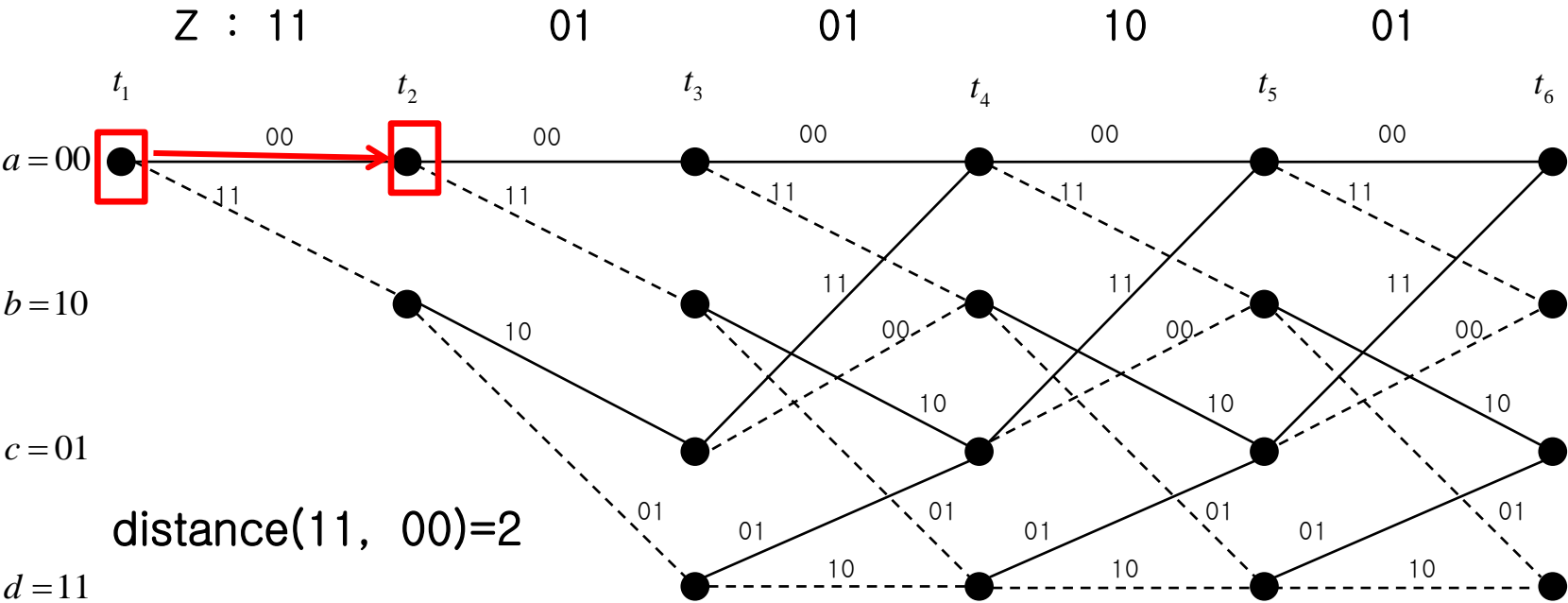Z= decoder input, received (demodulated) sequence.



	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0 <span style="color:red">→</span>					
d2	0					
d3	0					
d4	0					
output1	None <span style="color:red">→</span>					
output2	None					
output3	None					
output4	None					

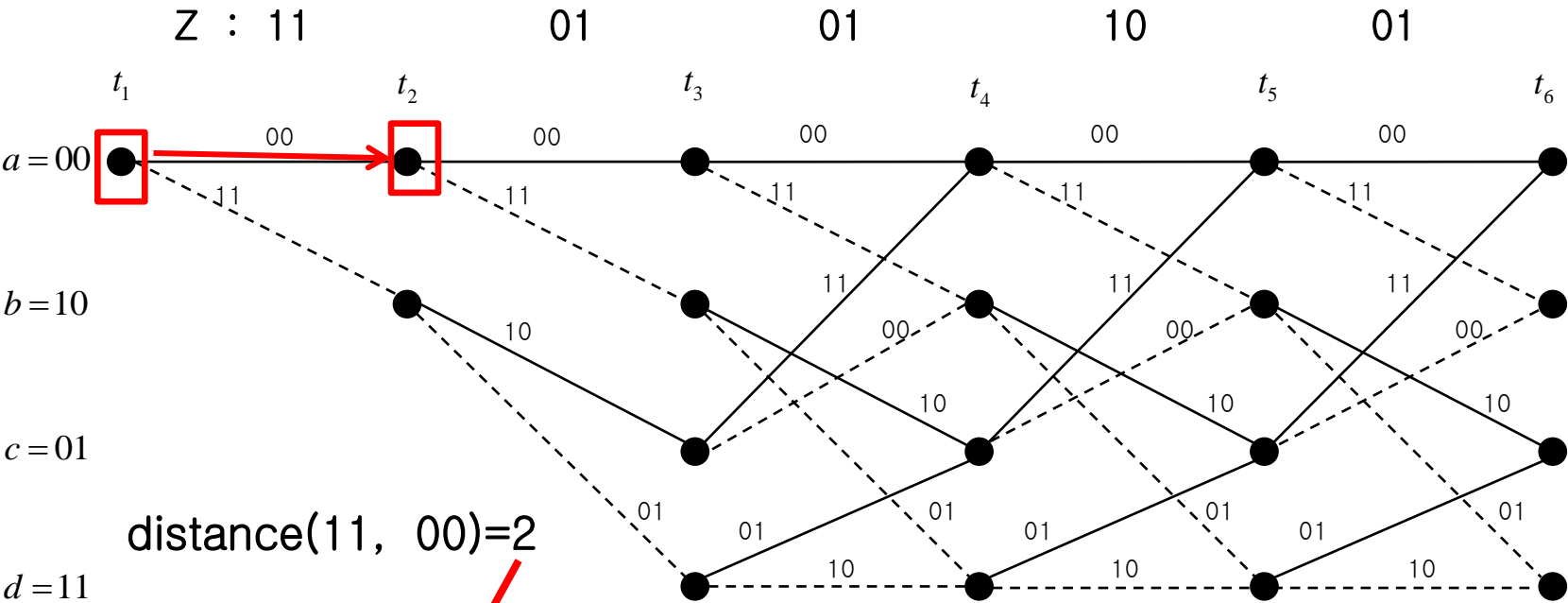
Z= decoder input, received (demodulated) sequence.



	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	0 + 2 = 2				
d2	0					
d3	0					
d4	0					
output1	None					
output2	None					
output3	None					
output4	None					




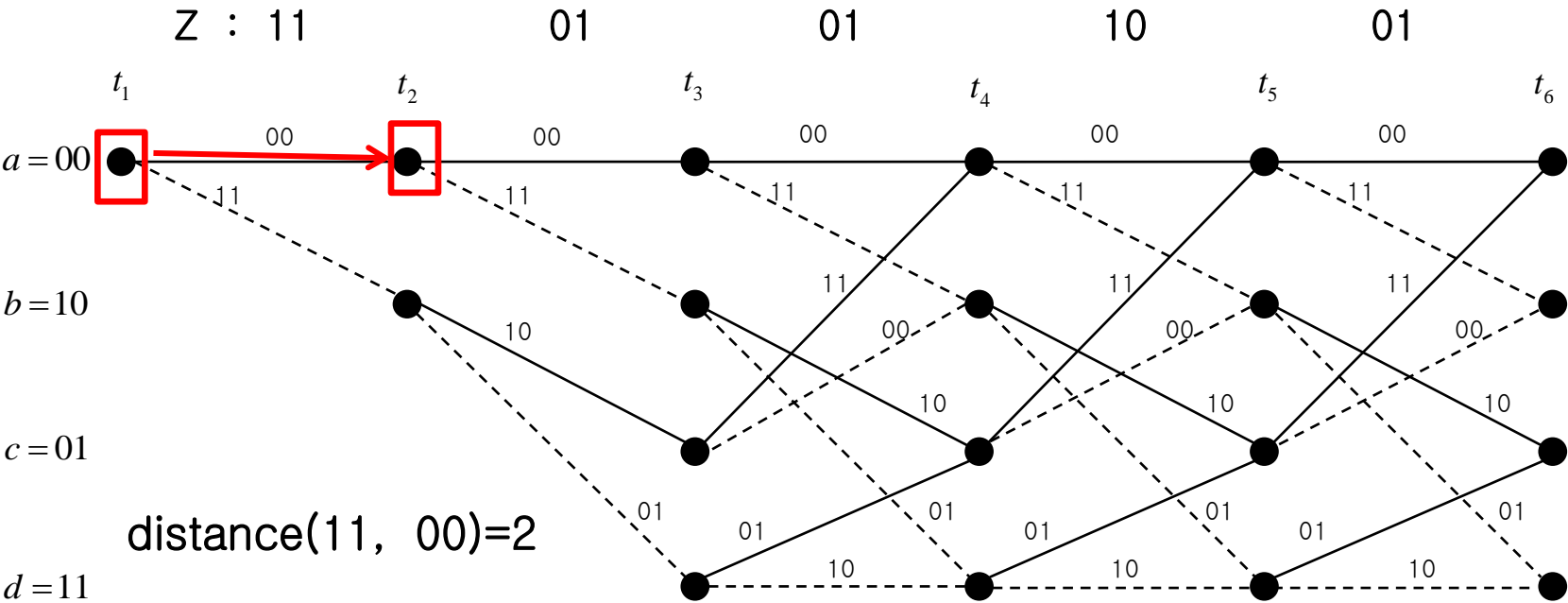Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2				
d2	0					
d3	0					
d4	0					
output1	None	0 (Solid line = 0)				
output2	None					
output3	None					
output4	None					

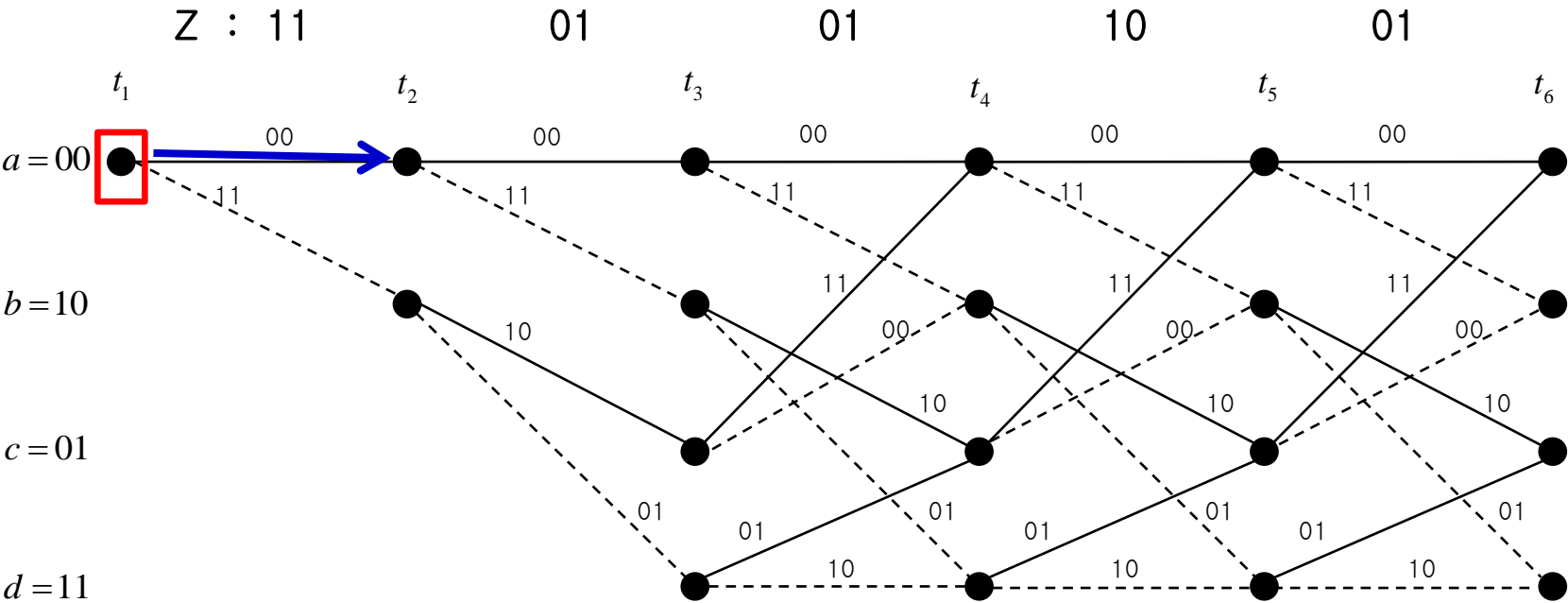Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2				
d2	0					
d3	0					
d4	0					
output1	None	0				
output2	None					
output3	None					
output4	None					

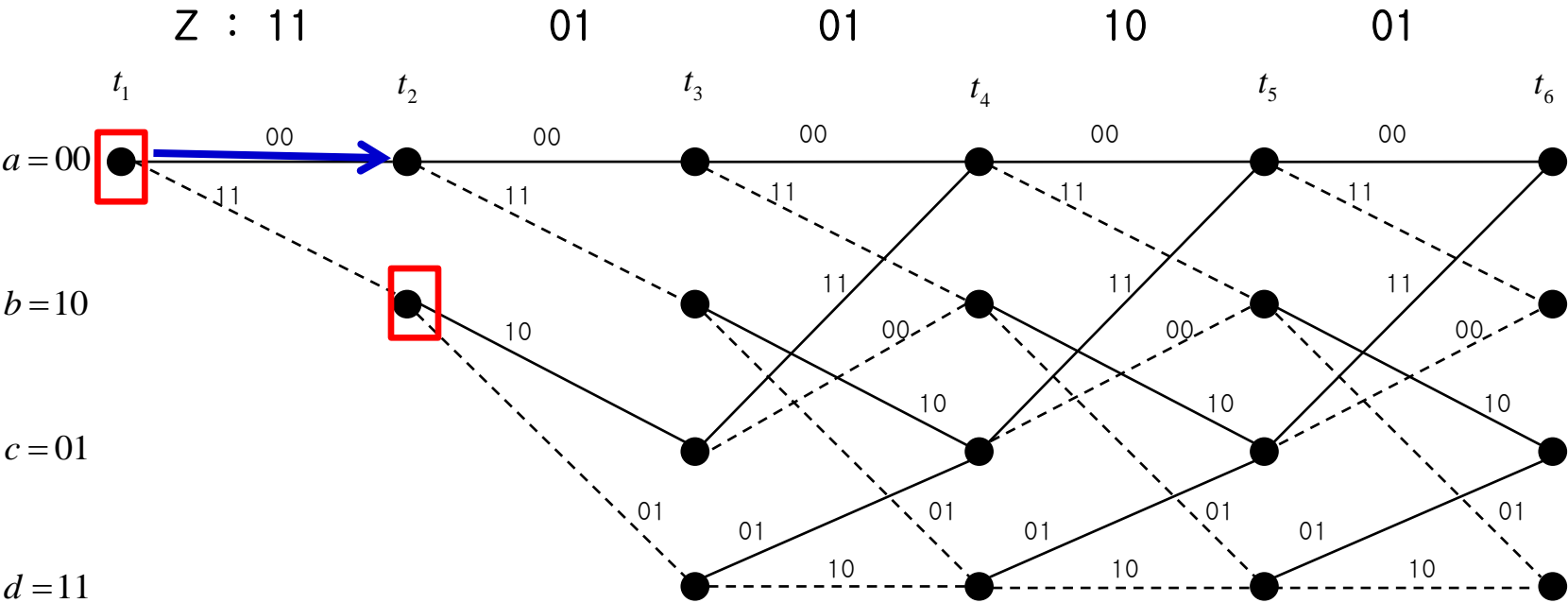Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2				
d2	0					
d3	0					
d4	0					
output1	None	0				
output2	None					
output3	None					
output4	None					

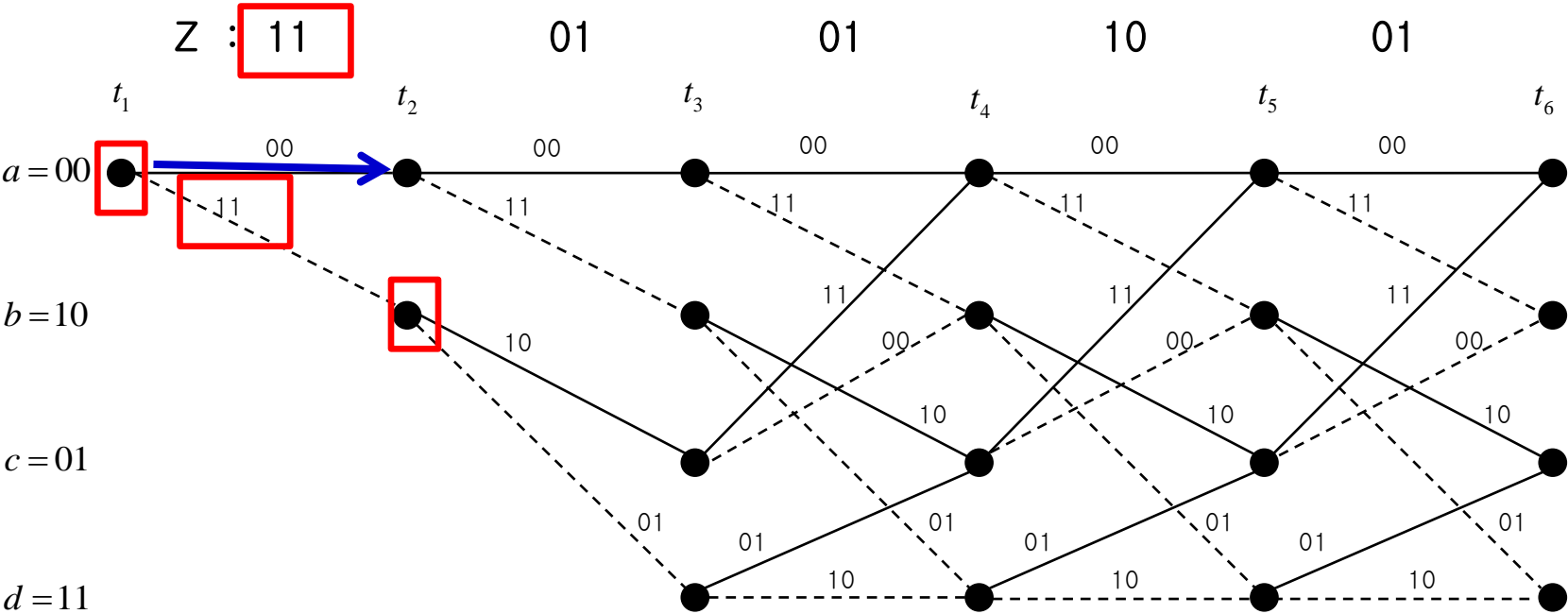Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2				
d2	0					
d3	0					
d4	0					
output1	None	0				
output2	None					
output3	None					
output4	None					

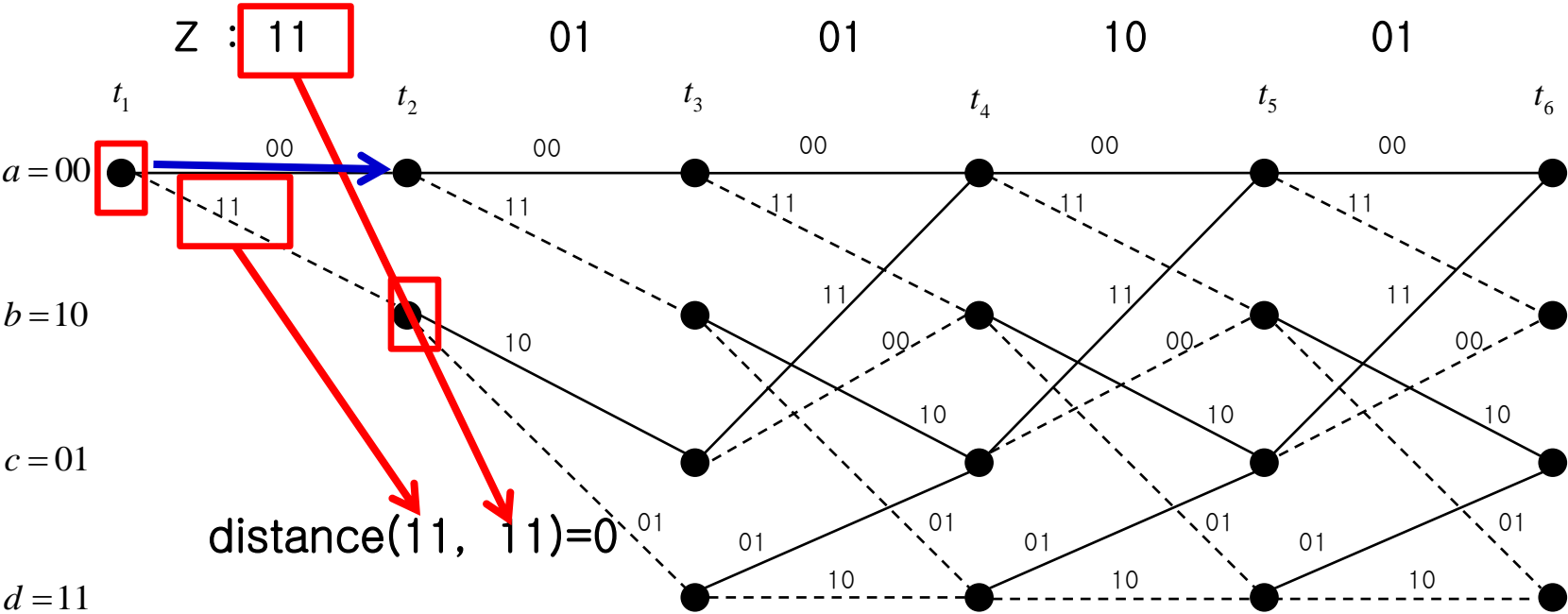Z= decoder input, received (demodulated) sequence.




	t <sub>1</sub> =0	t <sub>1</sub> ->t <sub>2</sub>	t <sub>2</sub> ->t <sub>3</sub>	t <sub>3</sub> ->t <sub>4</sub>	t <sub>4</sub> ->t <sub>5</sub>	t <sub>5</sub> ->t <sub>6</sub>
d1	0	2				
d2	0					
d3	0					
d4	0					
output1	None	0				
output2	None					
output3	None					
output4	None					

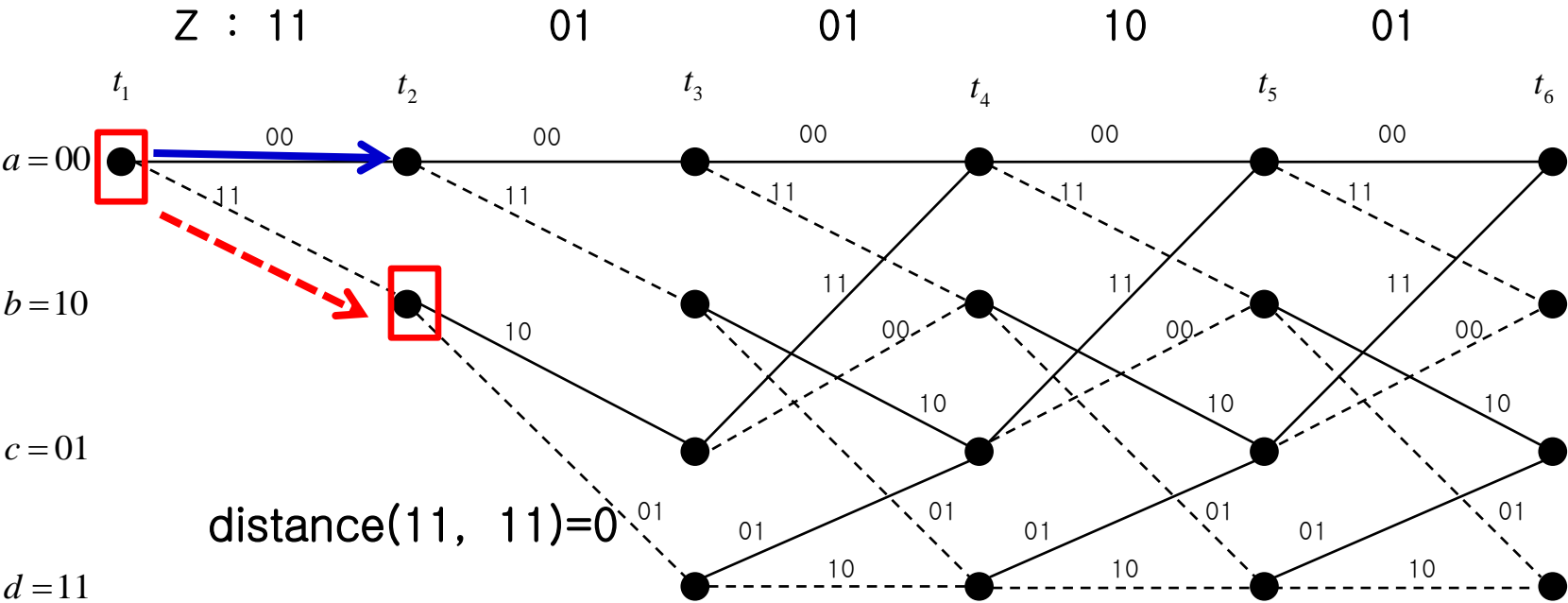Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2				
d2	0					
d3	0					
d4	0					
output1	None	0				
output2	None					
output3	None					
output4	None					

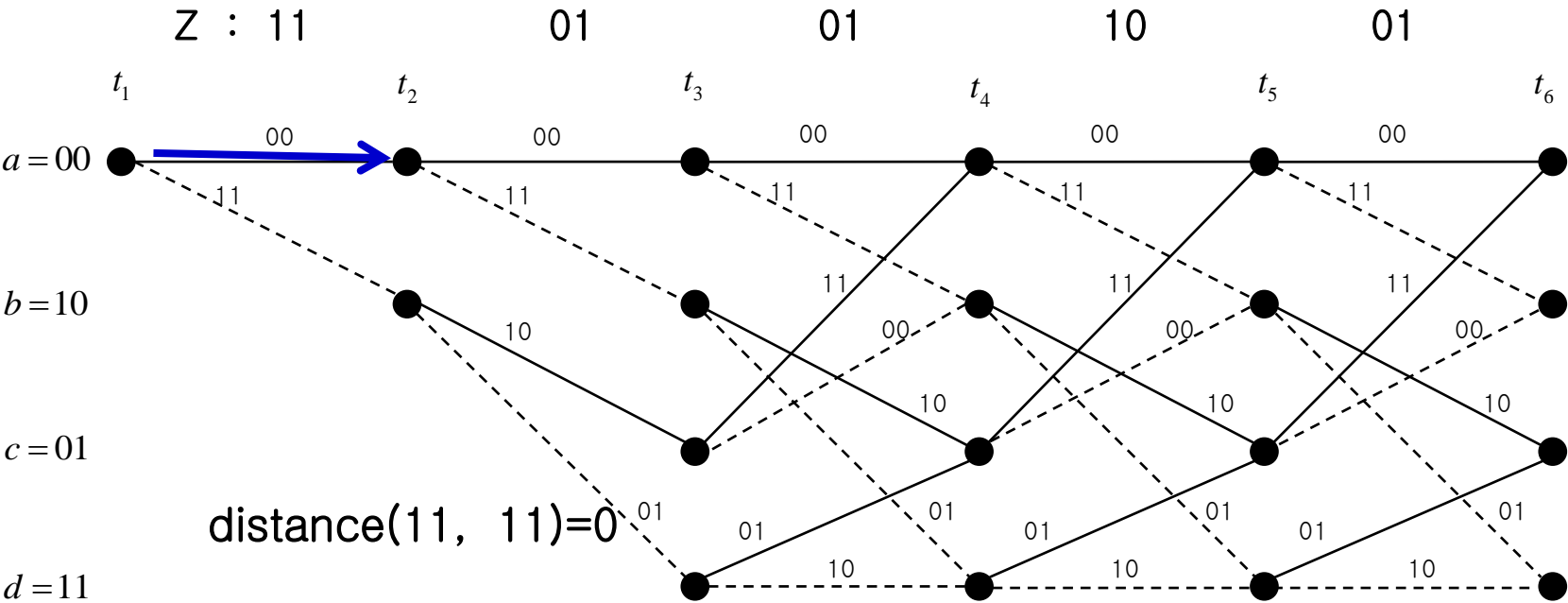Z= decoder input, received (demodulated) sequence.



	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2				
d2	0					
d3	0					
d4	0					
output1	None	0				
output2	None					
output3	None					
output4	None					

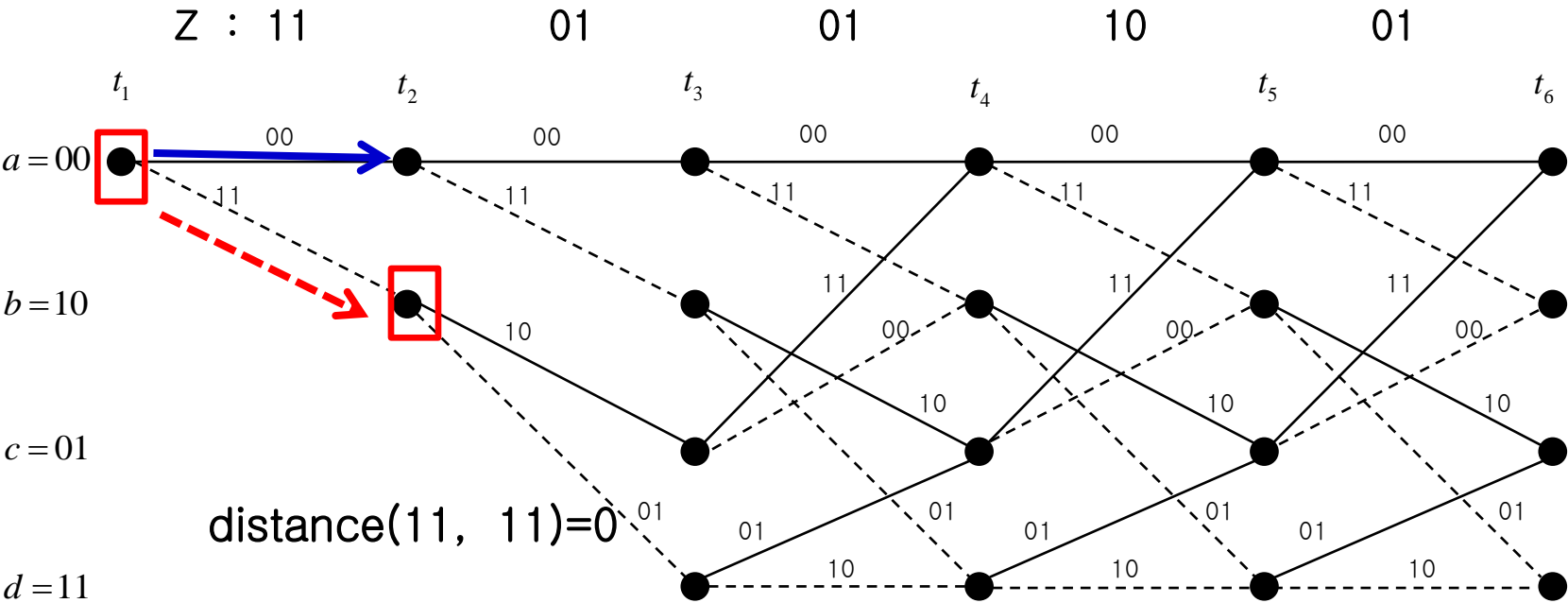
Z= decoder input, received (demodulated) sequence.



	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2				
d2	0					
d3	0					
d4	0					
output1	None	0				
output2	None					
output3	None					
output4	None					




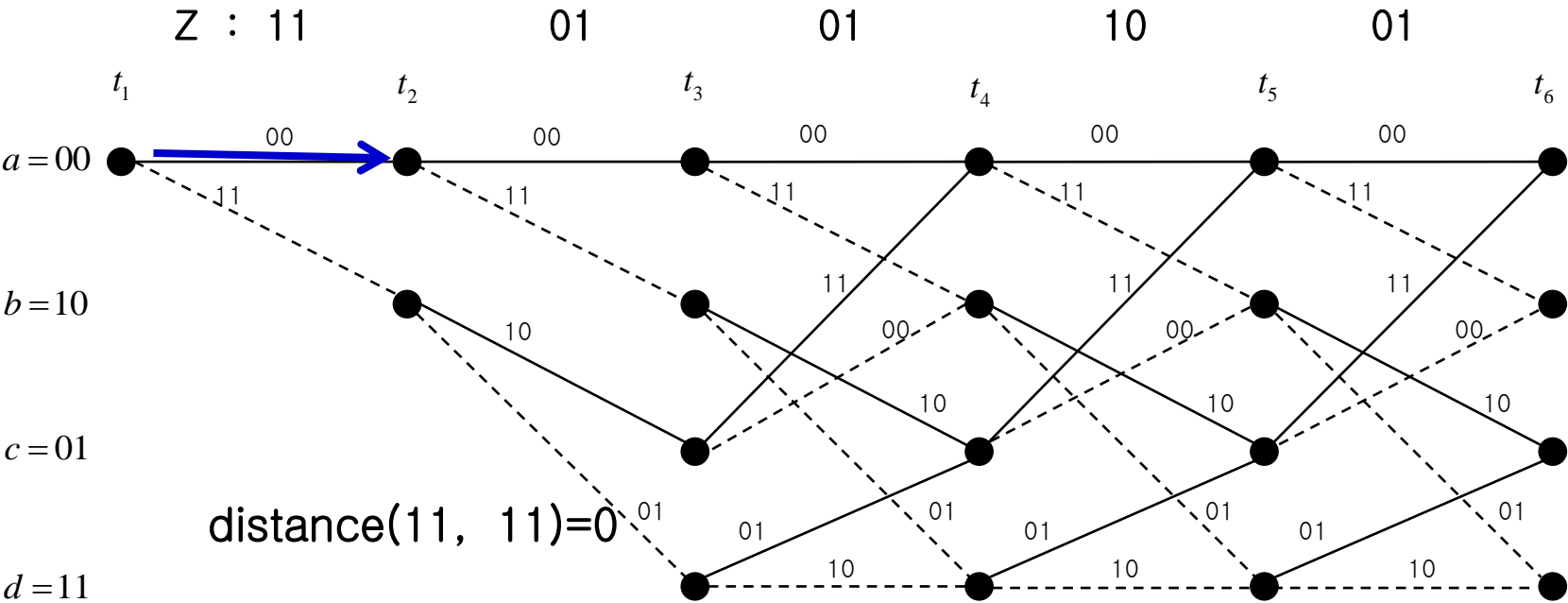Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2				
d2	0					
d3	0					
d4	0					
output1	None	0				
output2	None					
output3	None					
output4	None					

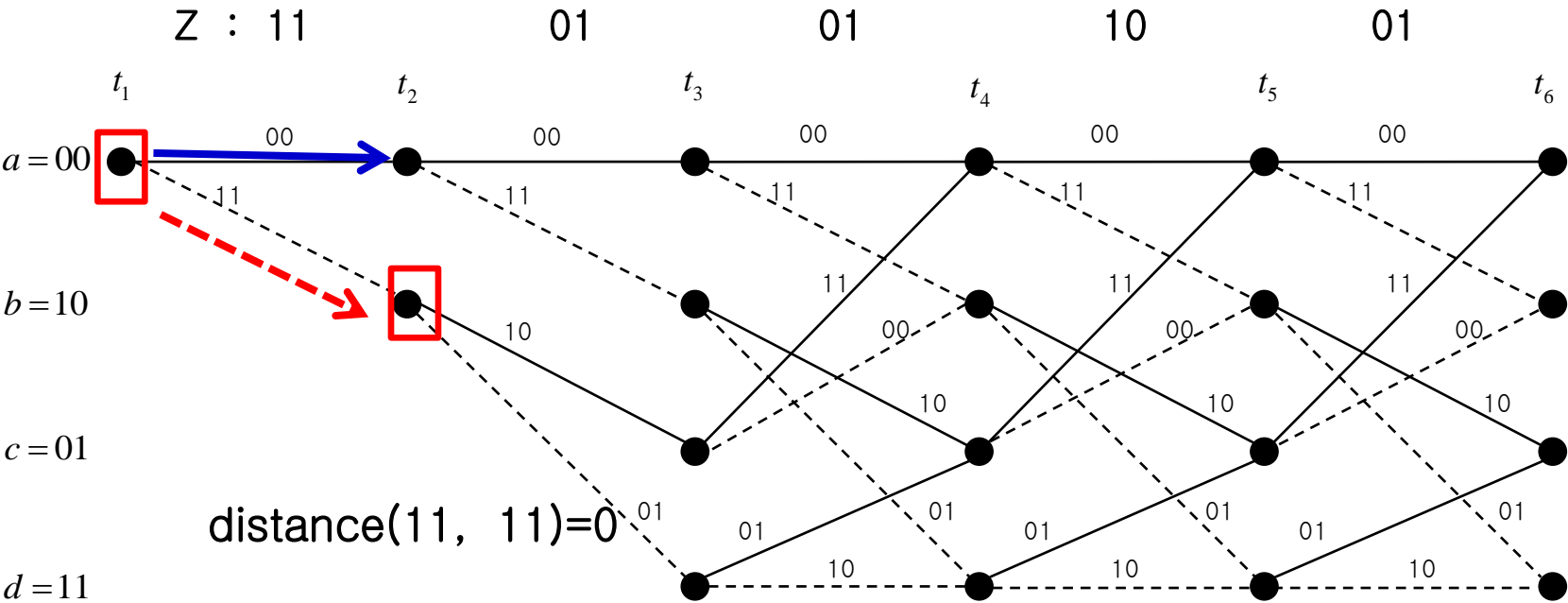Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2				
d2	0					
d3	0					
d4	0					
output1	None	0				
output2	None					
output3	None					
output4	None					

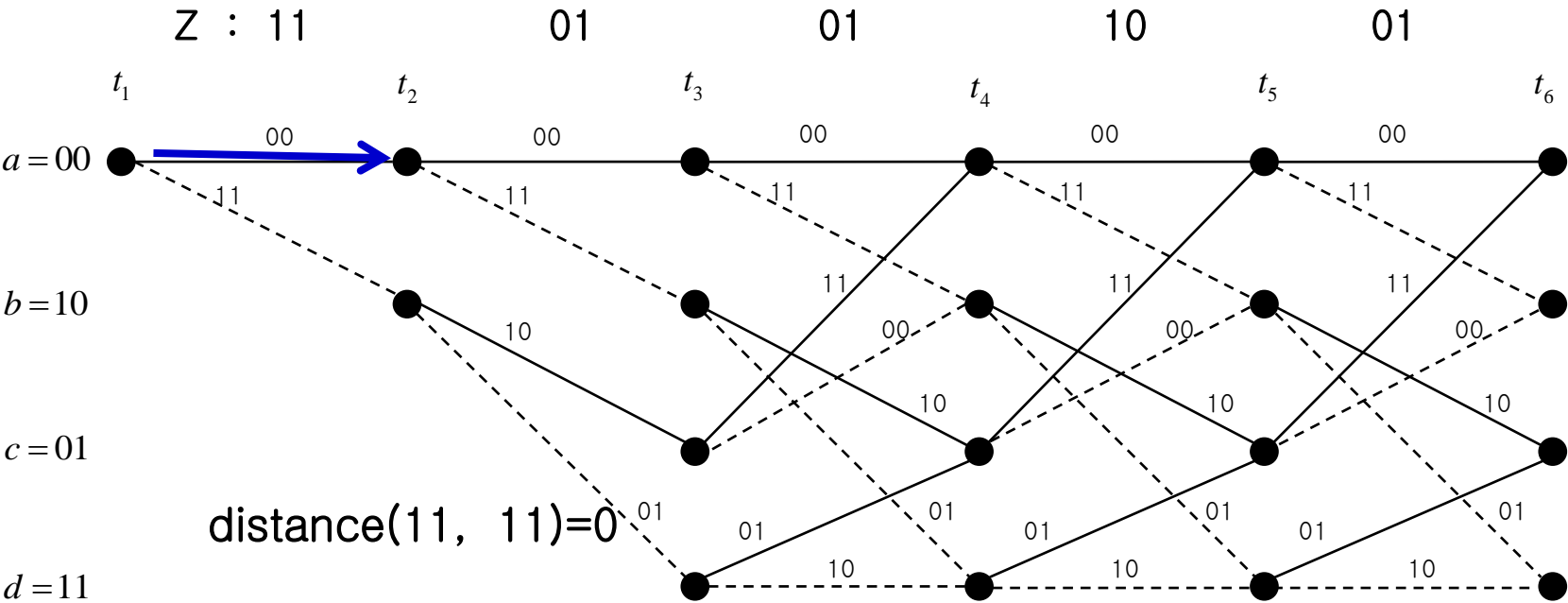Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2				
d2	0					
d3	0					
d4	0					
output1	None	0				
output2	None					
output3	None					
output4	None					

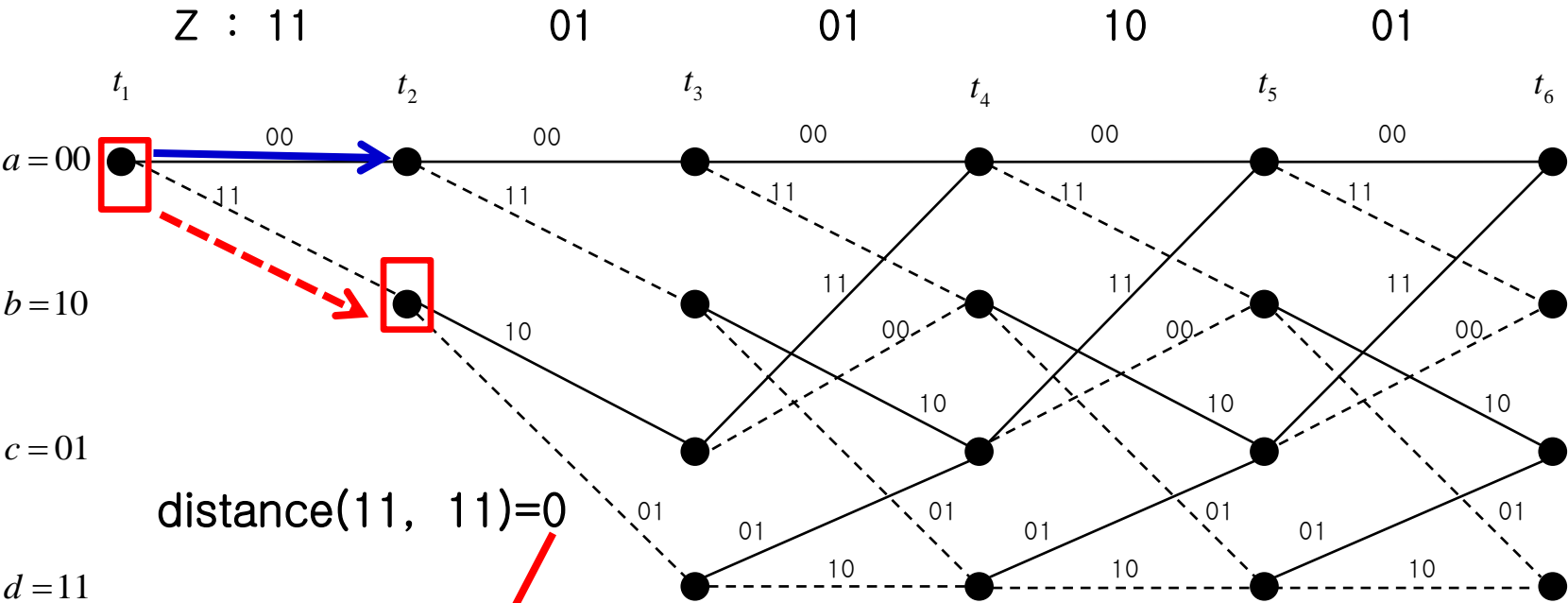Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2				
d2	0	$0+0=0$				
d3	0					
d4	0					
output1	None	0				
output2	None					
output3	None					
output4	None					

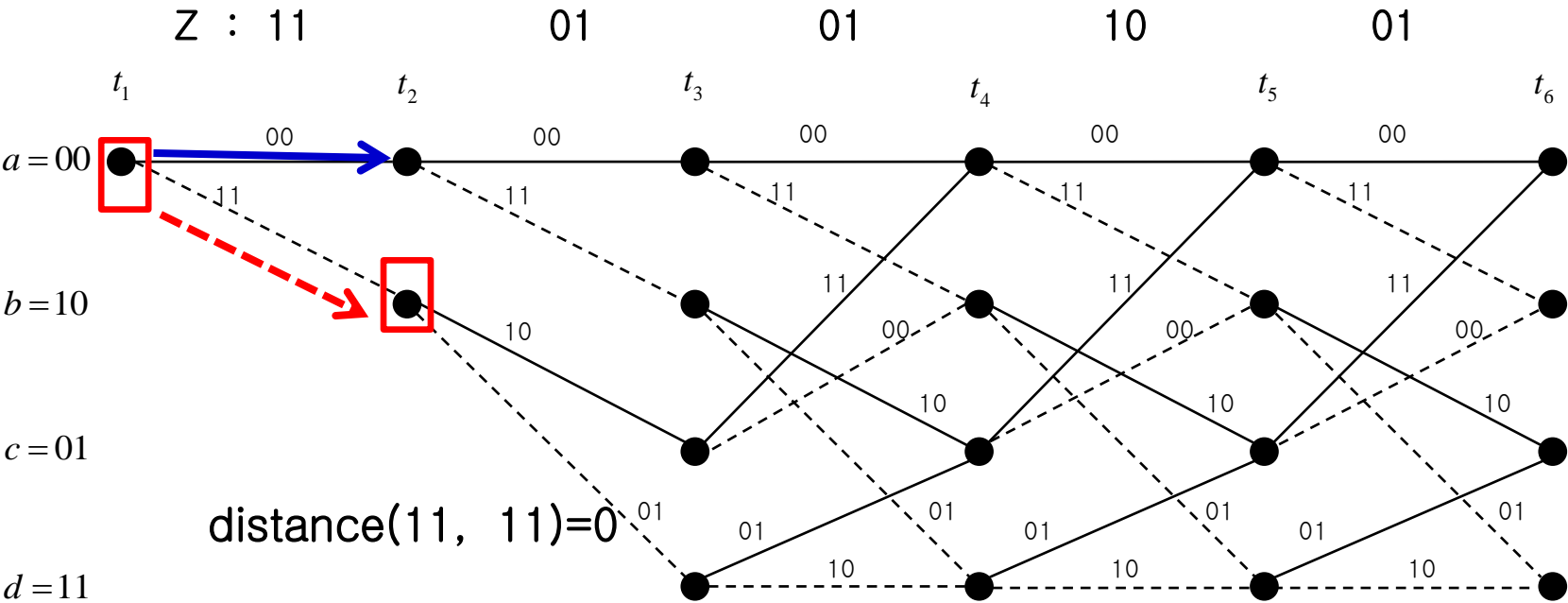Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2				
d2	0	0				
d3	0					
d4	0					
output1	None	0				
output2	None	1 (Dashed line = 1)				
output3	None					
output4	None					

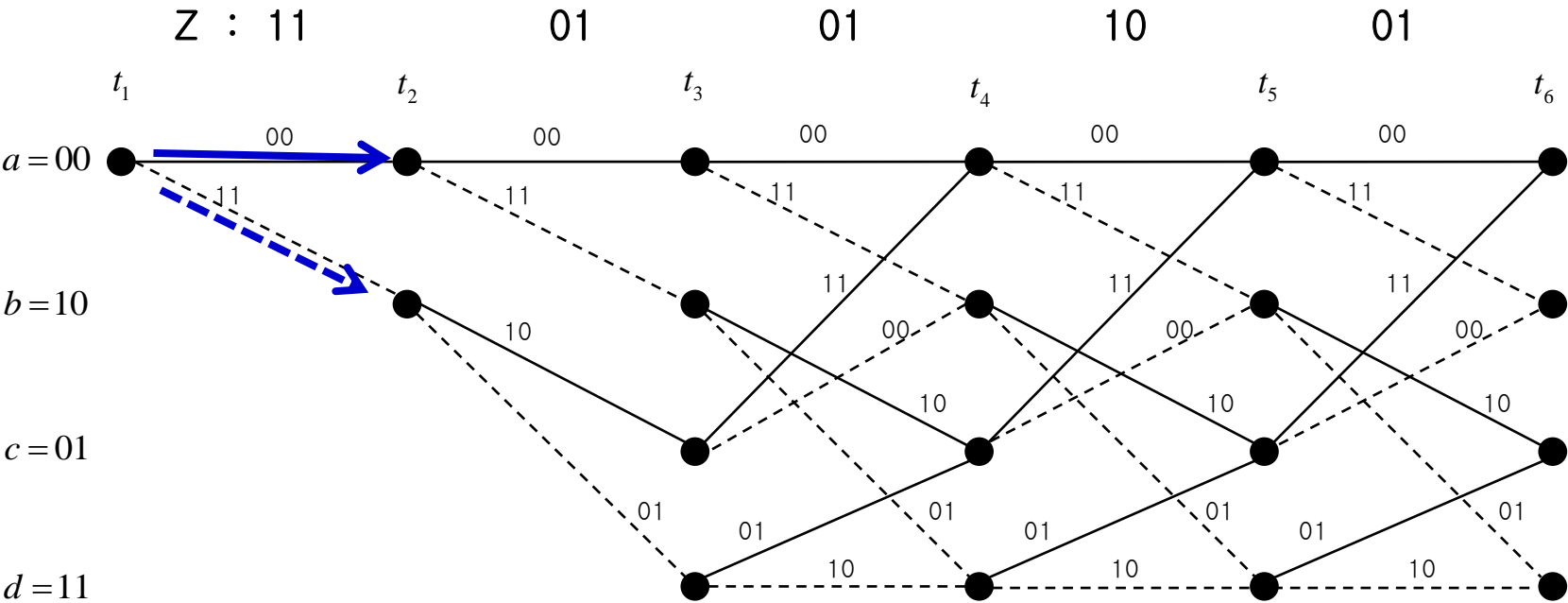Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2				
d2	0	0				
d3	0					
d4	0					
output1	None	0				
output2	None	1				
output3	None					
output4	None					

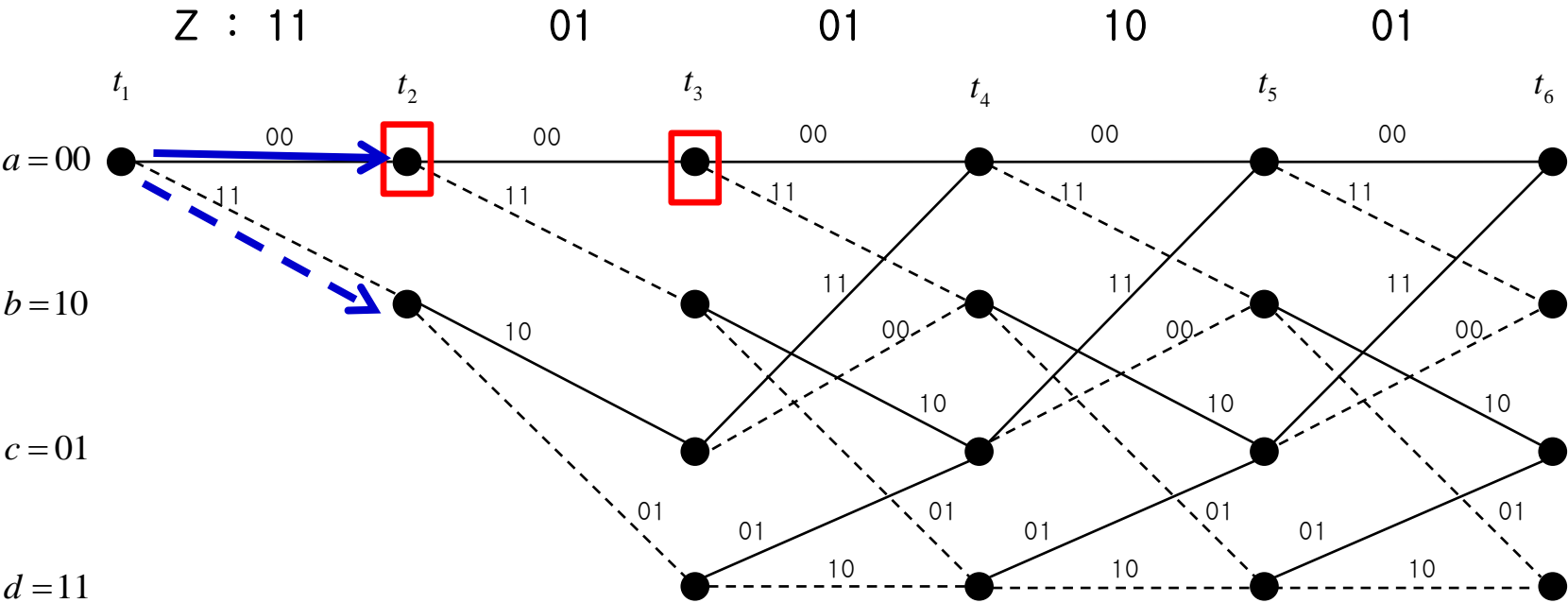Z= decoder input, received (demodulated) sequence.



	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2				
d2	0	0				
d3	0					
d4	0					
output1	None	0				
output2	None	1				
output3	None					
output4	None					

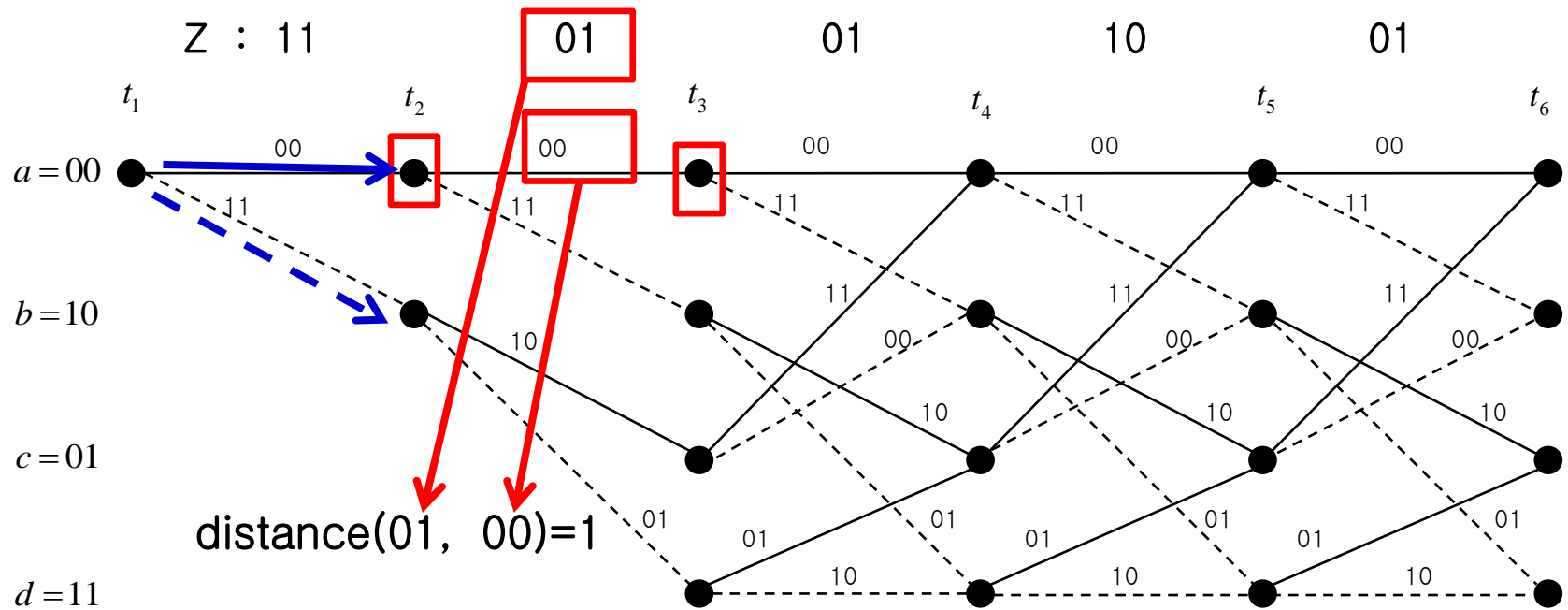
Z= decoder input, received (demodulated) sequence.



	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2				
d2	0	0				
d3	0					
d4	0					
output1	None	0				
output2	None	1				
output3	None					
output4	None					




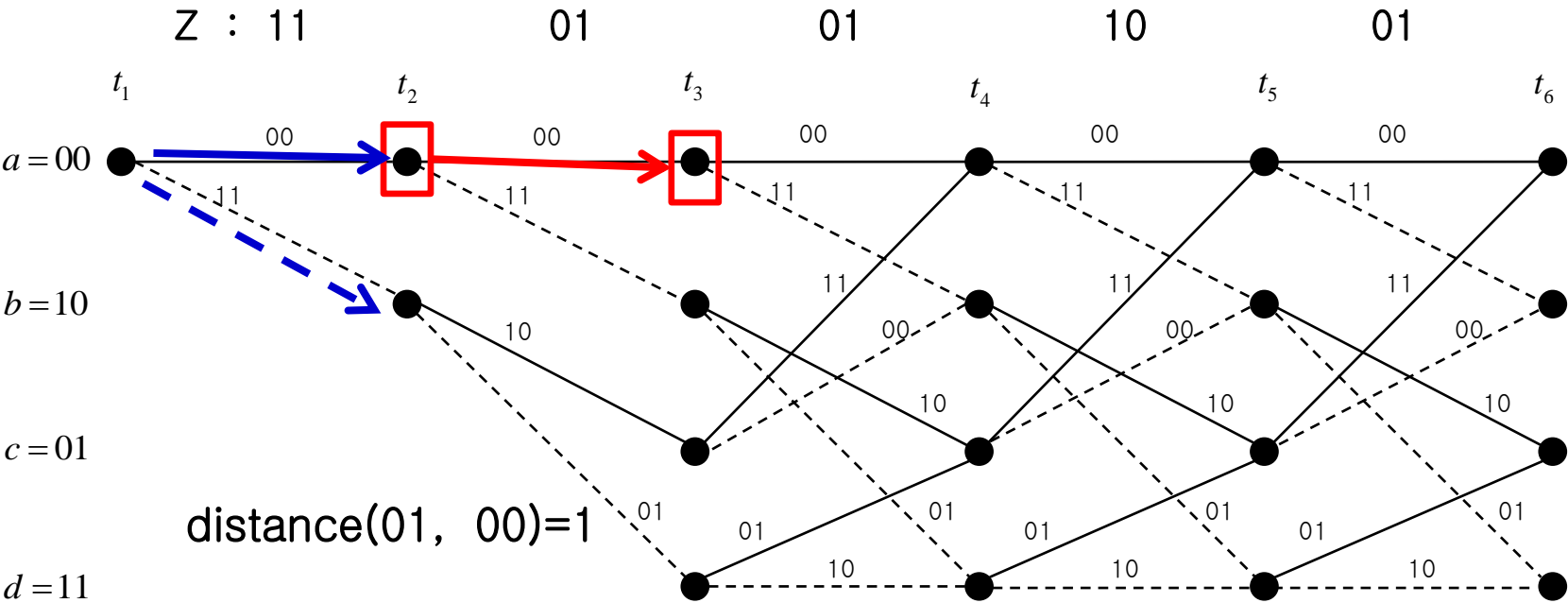Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2 <span style="color: red;">→</span>				
d2	0	0				
d3	0					
d4	0					
output1	None	0 <span style="color: red;">→</span>				
output2	None	1				
output3	None					
output4	None					

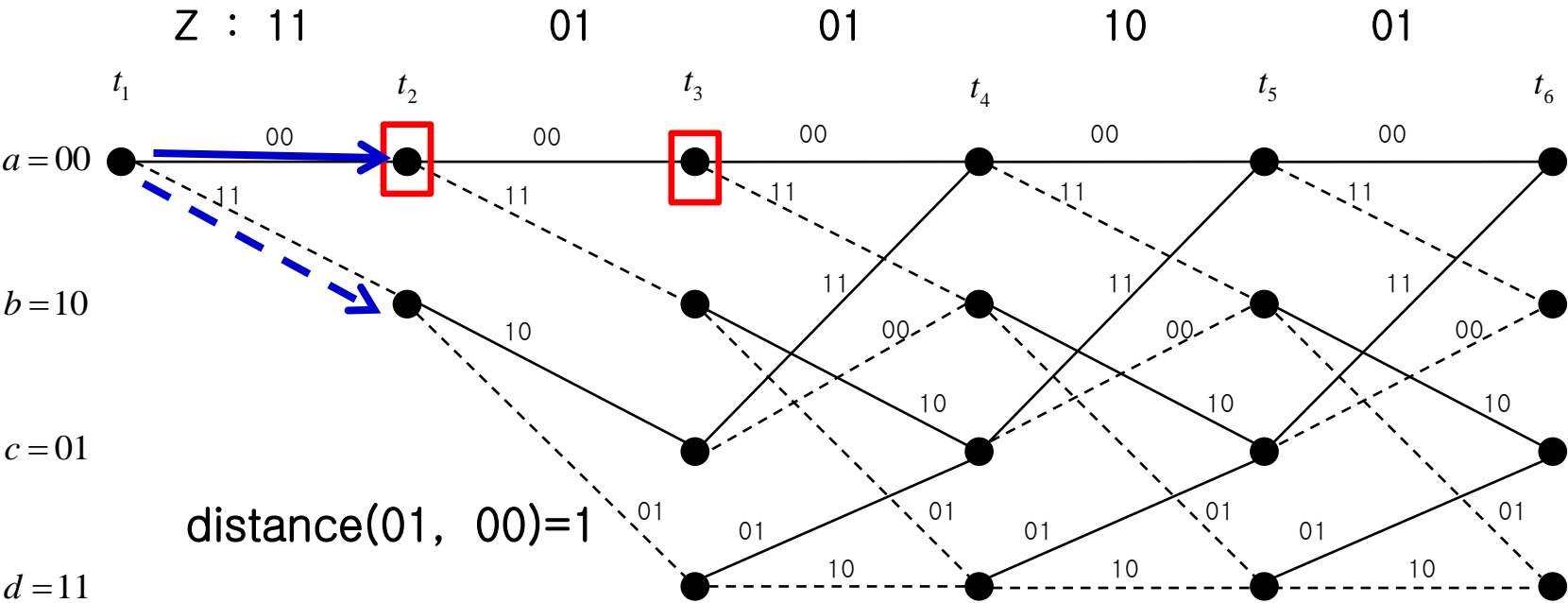Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2				
d2	0	0				
d3	0					
d4	0					
output1	None	0				
output2	None	1				
output3	None					
output4	None					

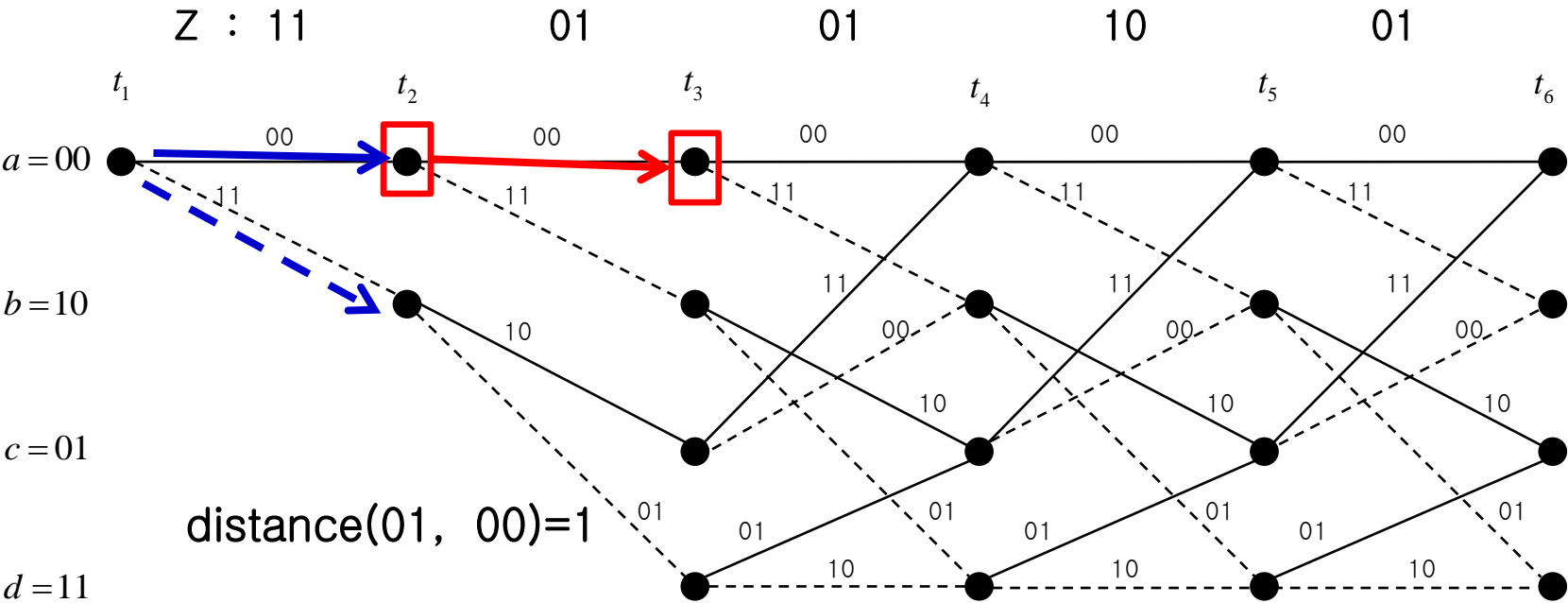Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2 <span style="color:red">→</span>				
d2	0	0				
d3	0					
d4	0					
output1	None	0 <span style="color:red">→</span>				
output2	None	1				
output3	None					
output4	None					

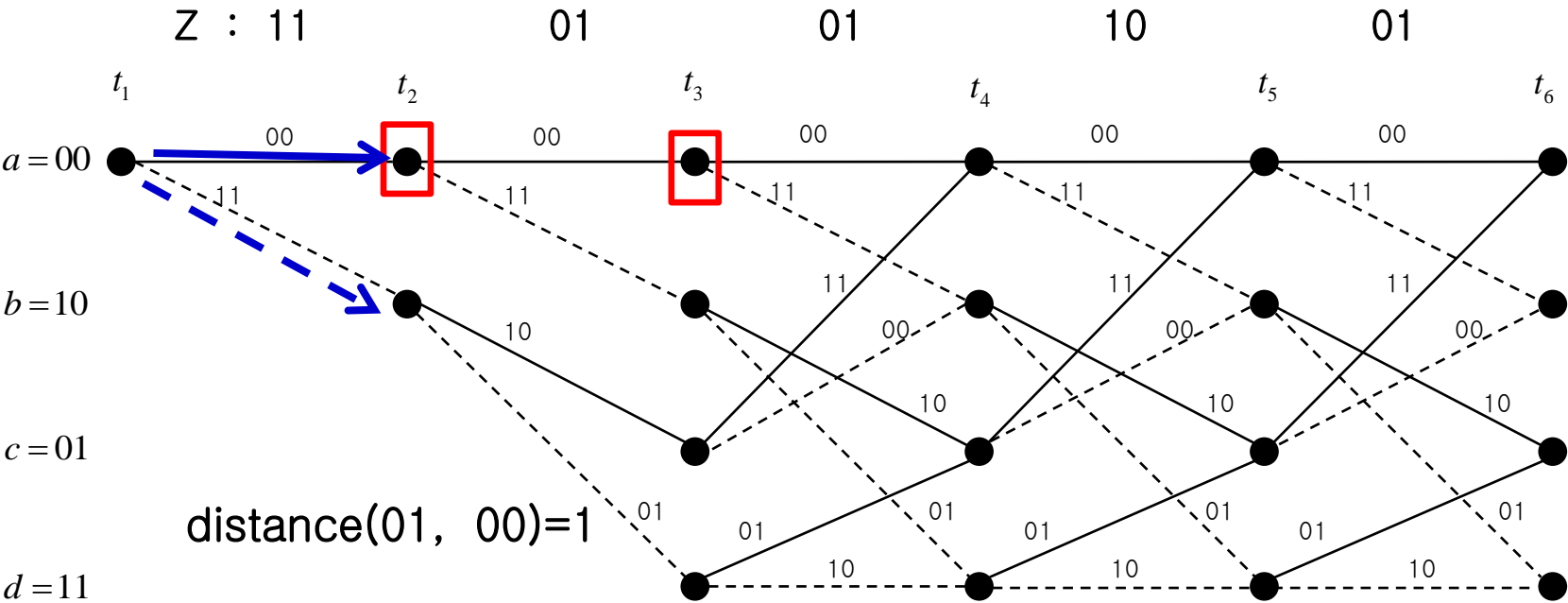Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2				
d2	0	0				
d3	0					
d4	0					
output1	None	0				
output2	None	1				
output3	None					
output4	None					

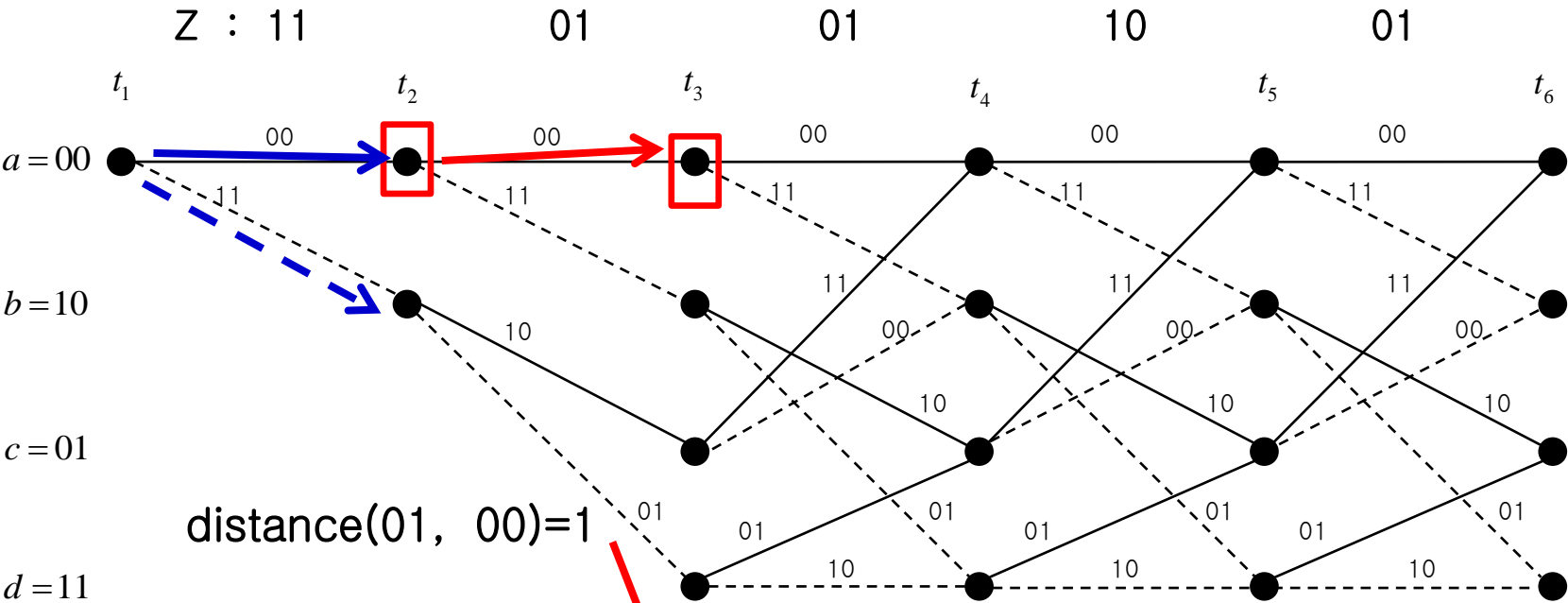Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	2+1=3			
d2	0	0				
d3	0					
d4	0					
output1	None	0				
output2	None	1				
output3	None					
output4	None					

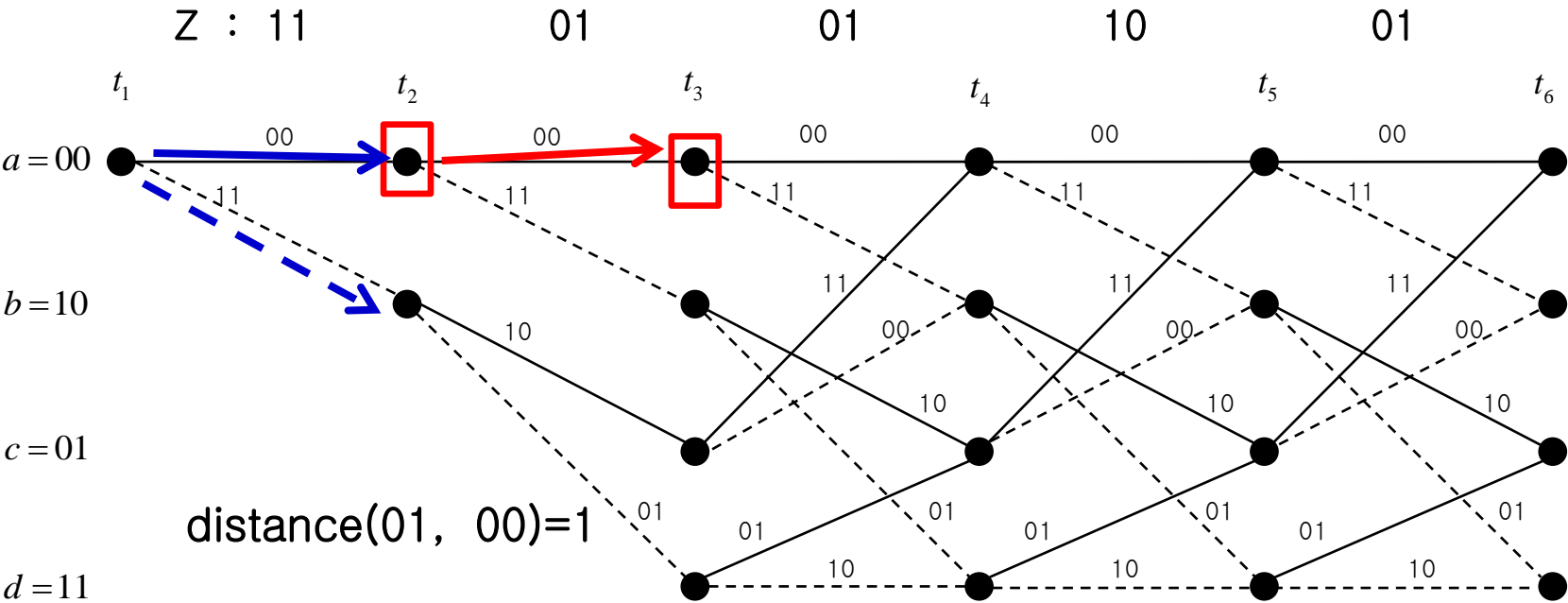Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0				
d3	0					
d4	0					
output1	None	0 <span style="color:red">→</span> 00 (Solid line = 0)				
output2	None	1				
output3	None					
output4	None					

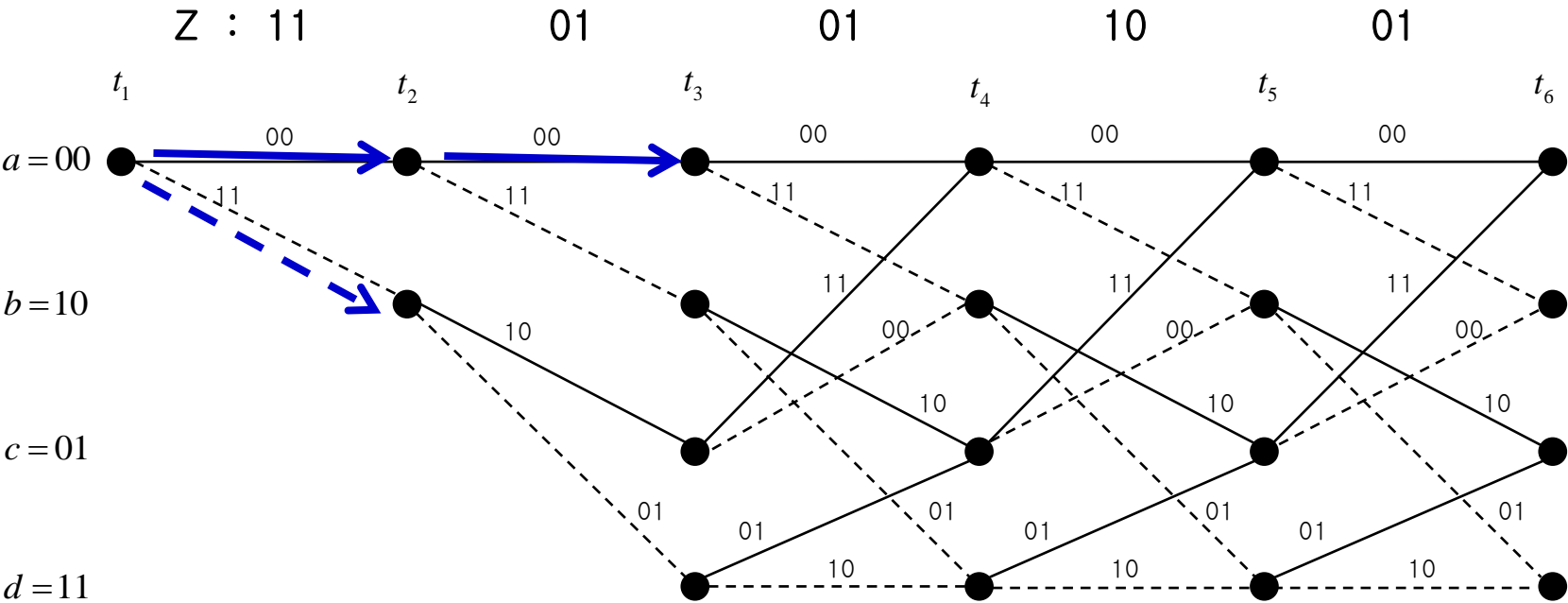Z= decoder input, received (demodulated) sequence.



	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0				
d3	0					
d4	0					
output1	None	0	00			
output2	None	1				
output3	None					
output4	None					

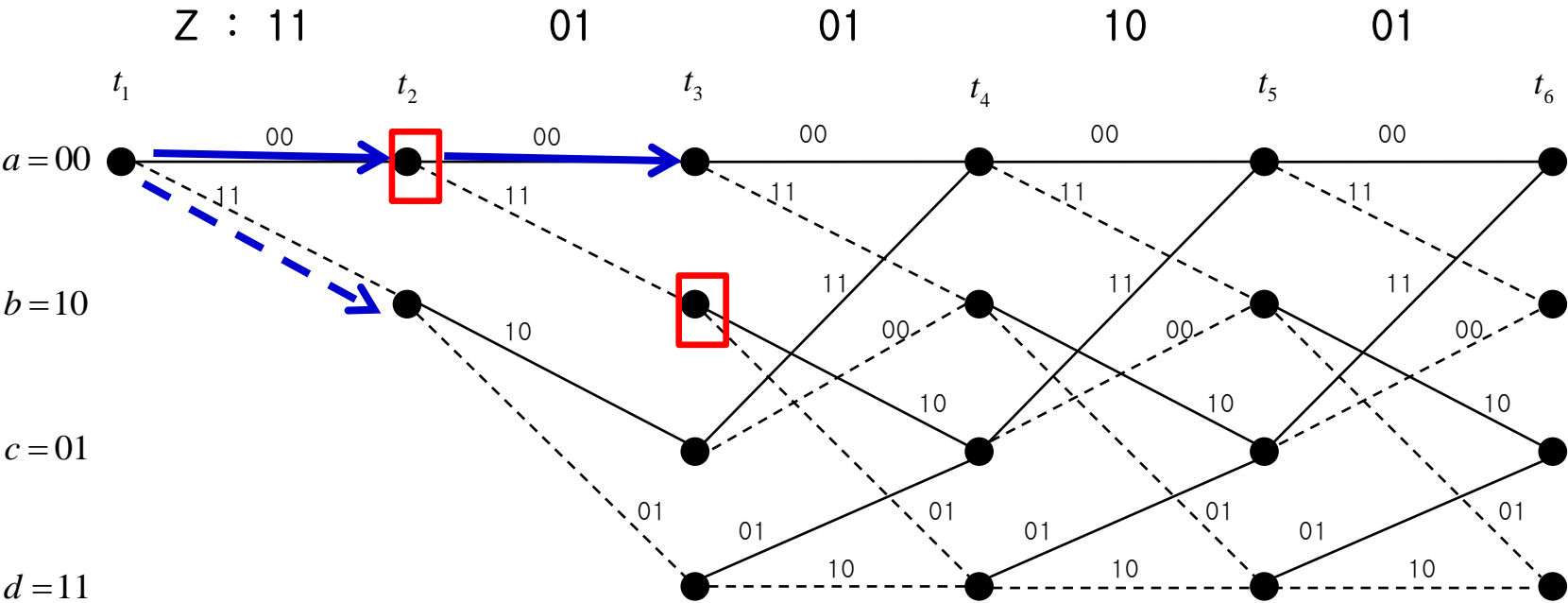
Z= decoder input, received (demodulated) sequence.



	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0				
d3	0					
d4	0					
output1	None	0	00			
output2	None	1				
output3	None					
output4	None					




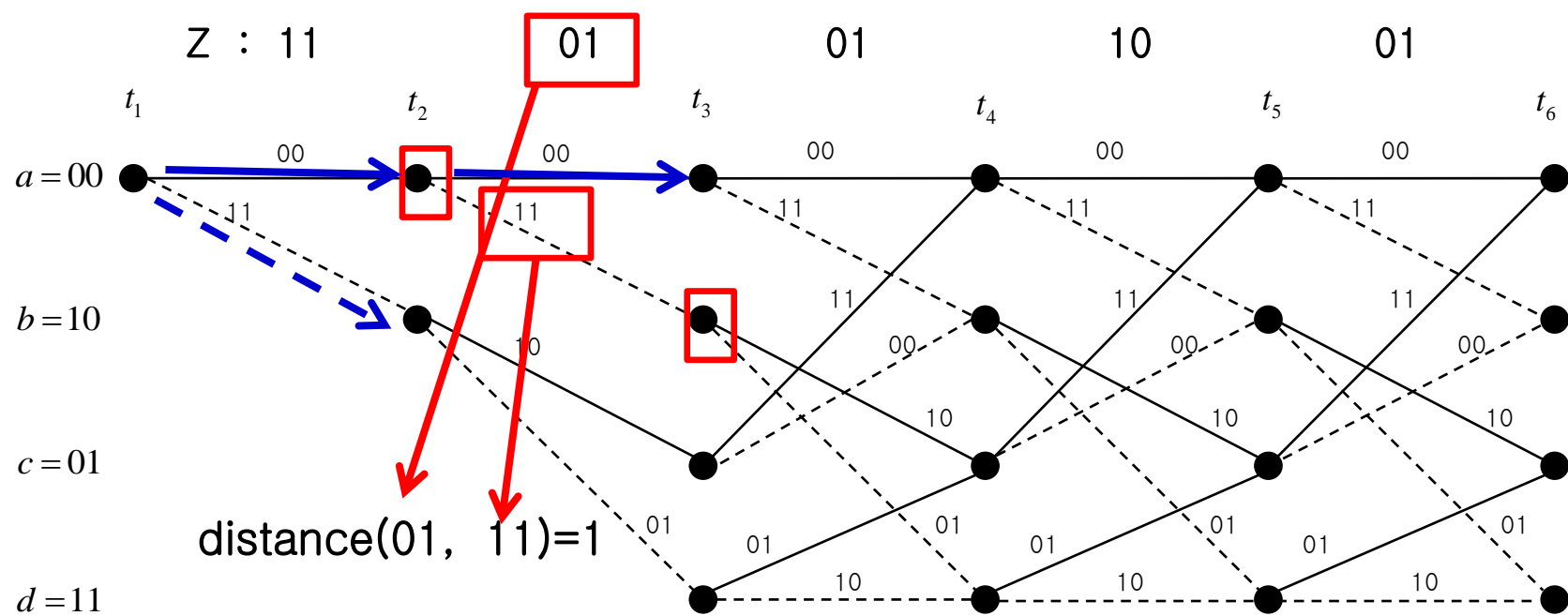Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0				
d3	0					
d4	0					
output1	None	0	00			
output2	None	1				
output3	None					
output4	None					

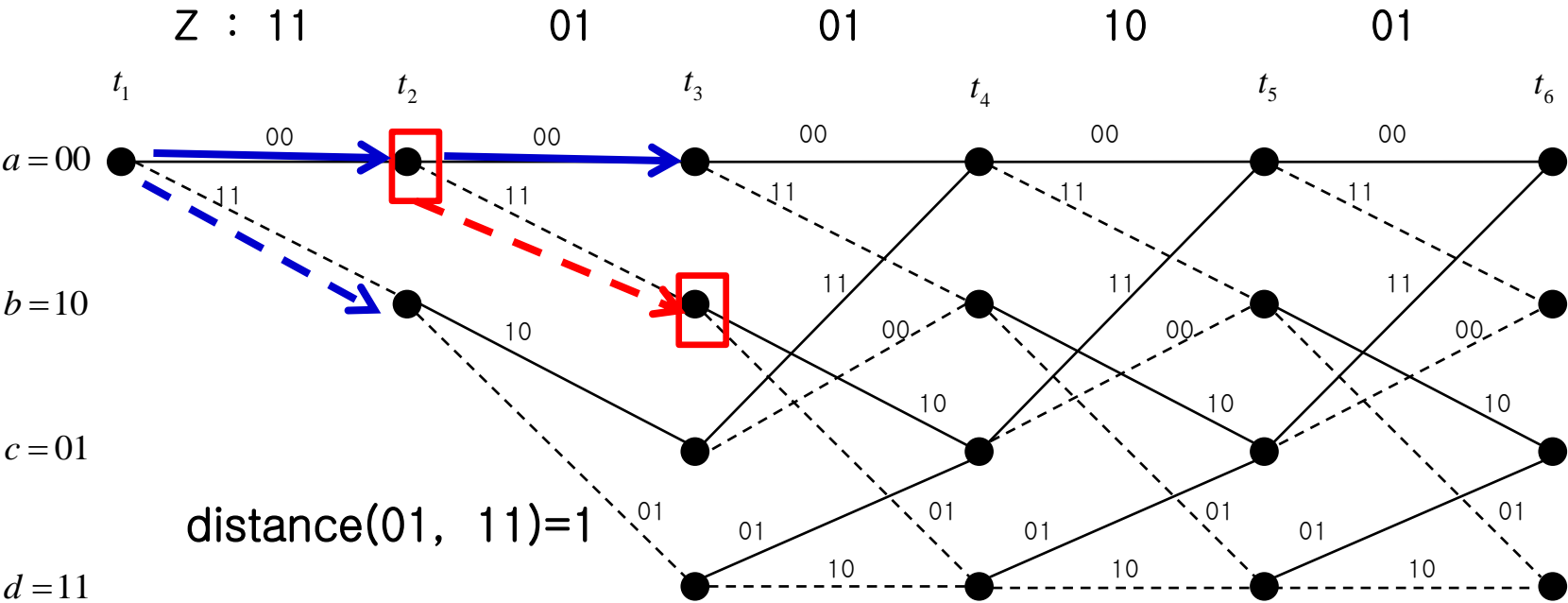Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0				
d3	0					
d4	0					
output1	None	0	00			
output2	None	1				
output3	None					
output4	None					

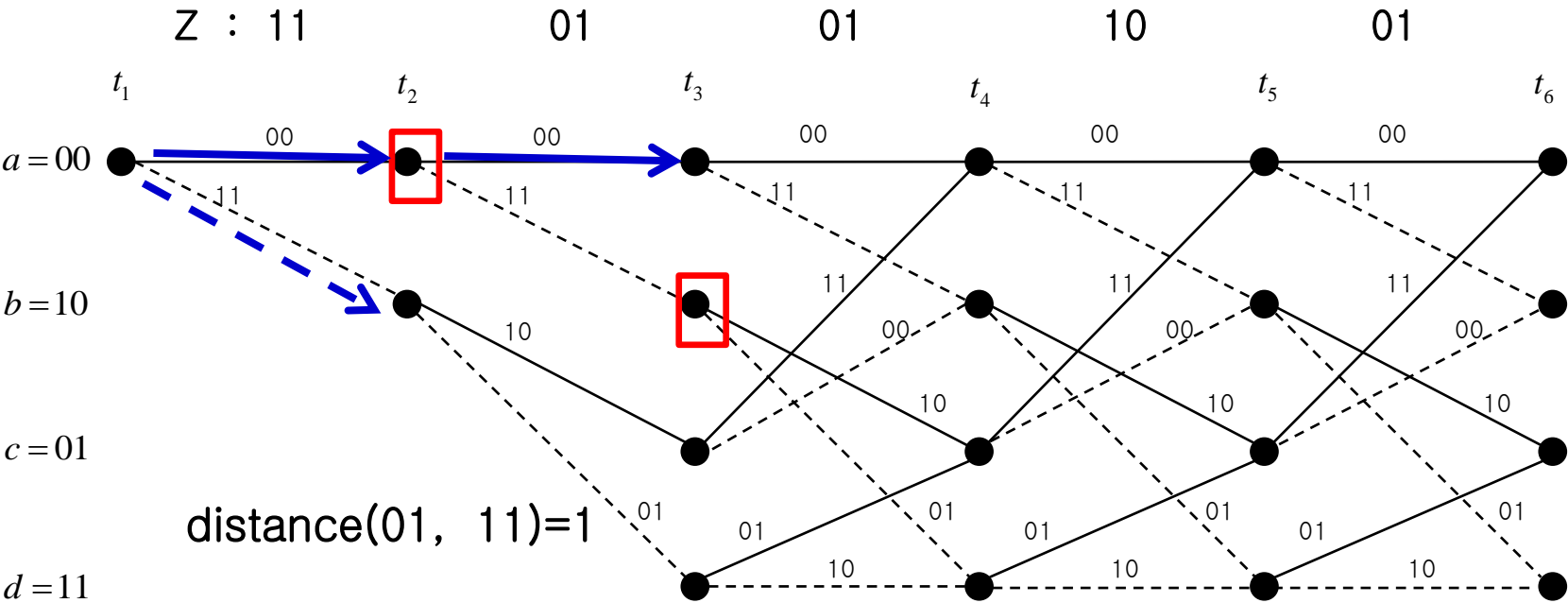Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0				
d3	0					
d4	0					
output1	None	0	00			
output2	None	1				
output3	None					
output4	None					

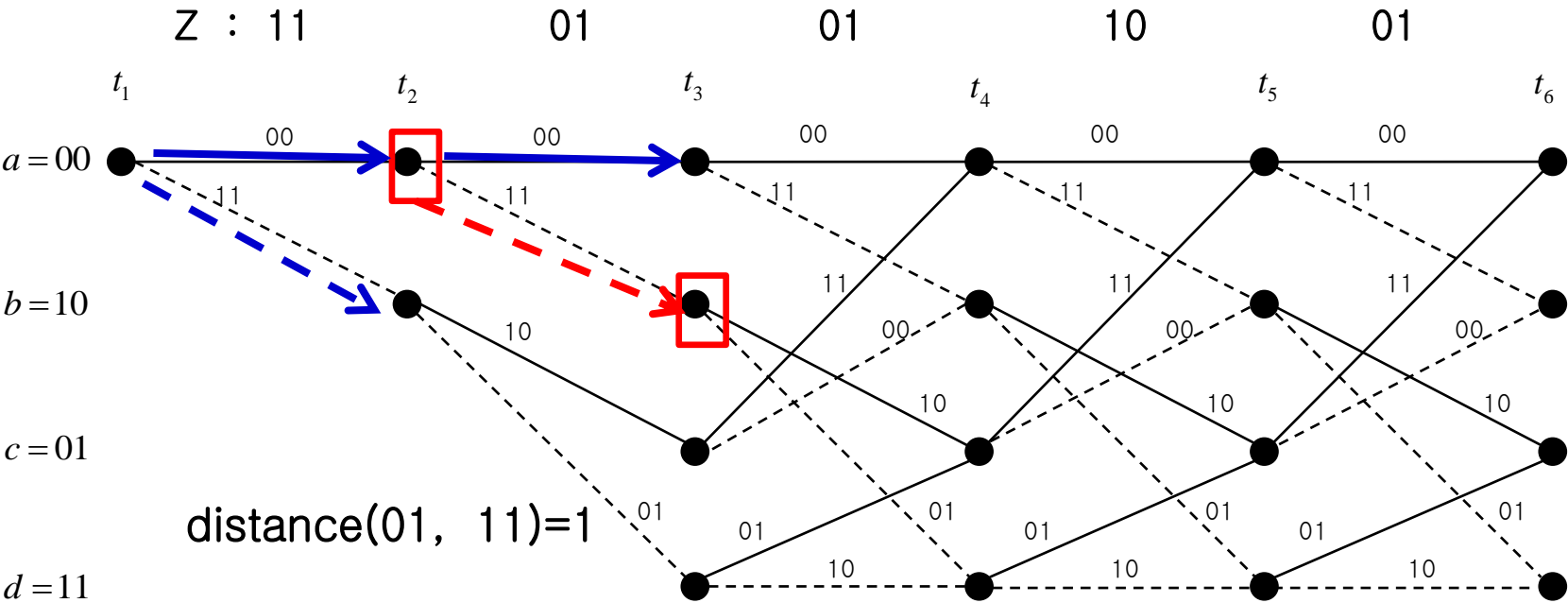Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0				
d3	0					
d4	0					
output1	None	0	00			
output2	None	1				
output3	None					
output4	None					

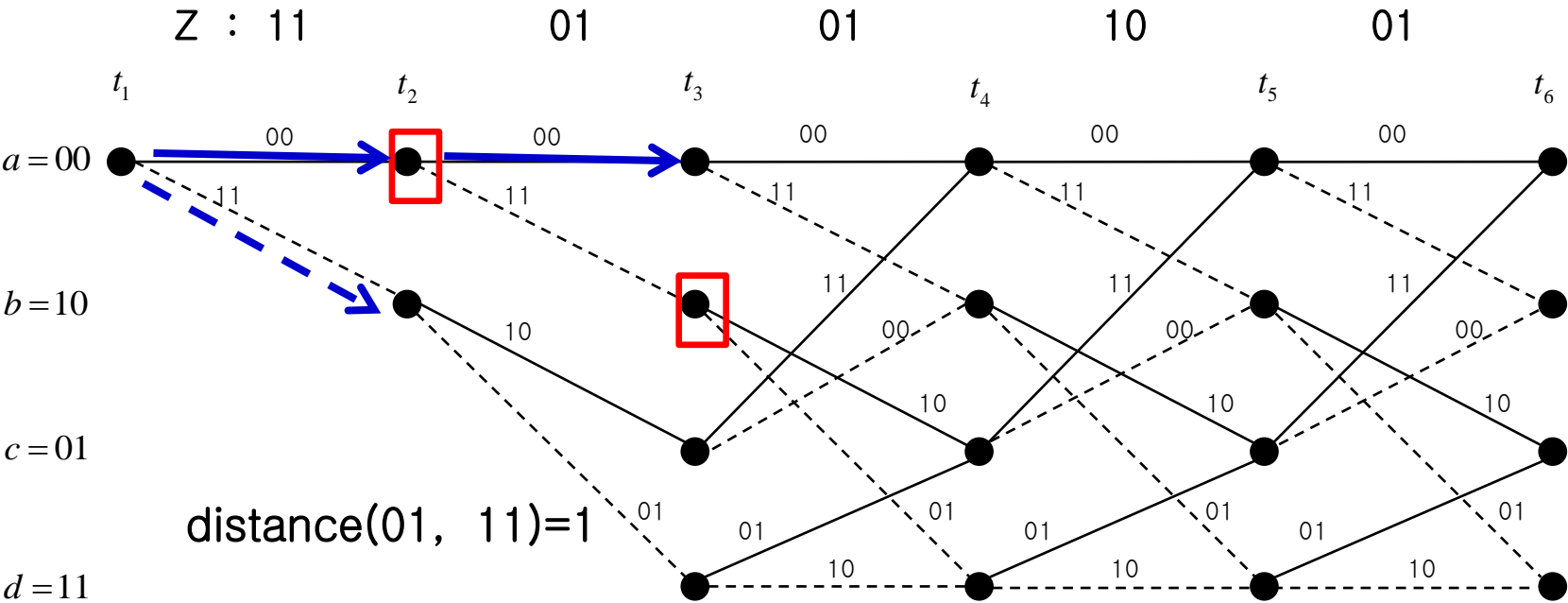Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0				
d3	0					
d4	0					
output1	None	0	00			
output2	None	1				
output3	None					
output4	None					

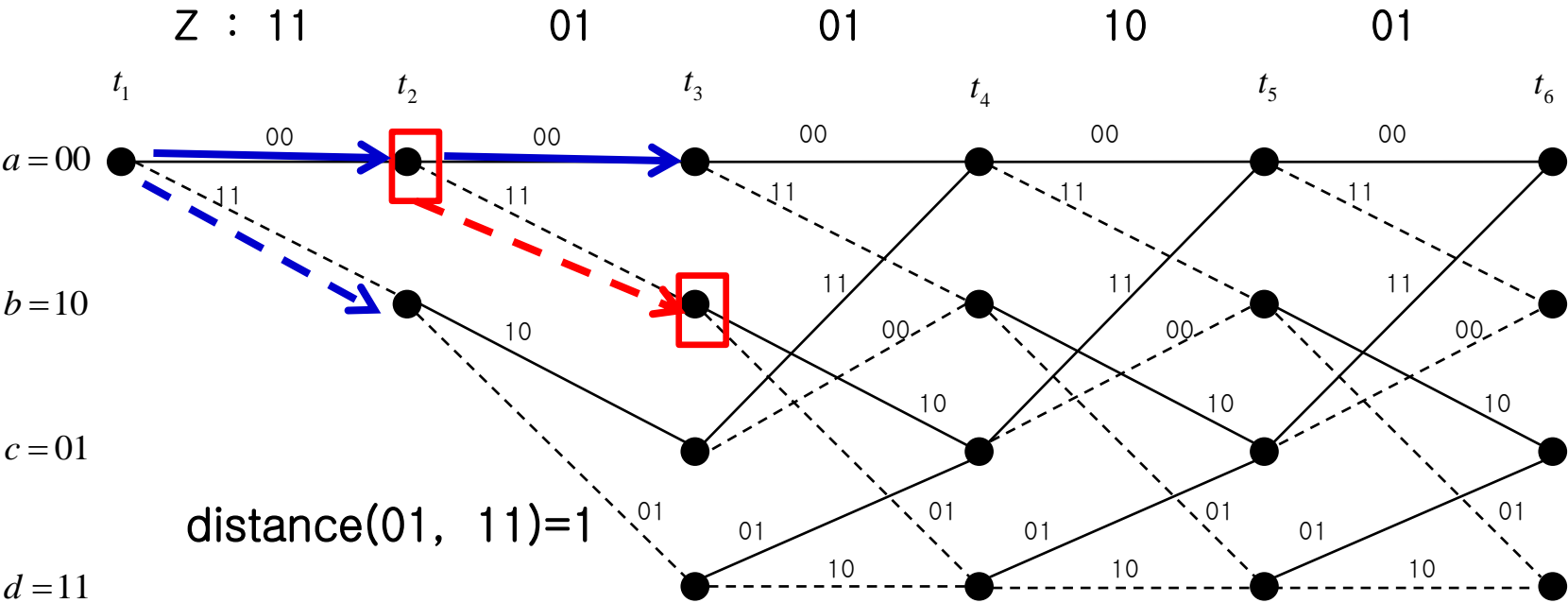Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0				
d3	0					
d4	0					
output1	None	0	00			
output2	None	1				
output3	None					
output4	None					

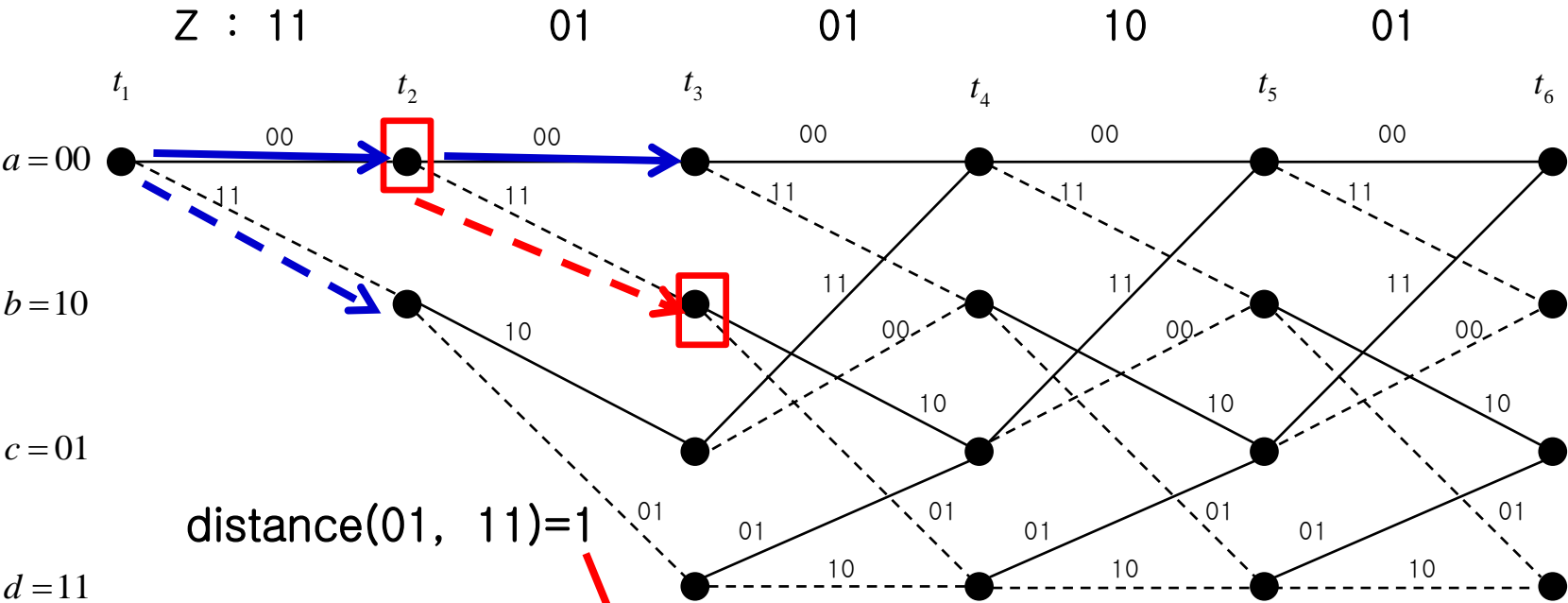Z= decoder input, received (demodulated) sequence.



	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	2+1=3			
d3	0					
d4	0					
output1	None	0	00			
output2	None	1				
output3	None					
output4	None					

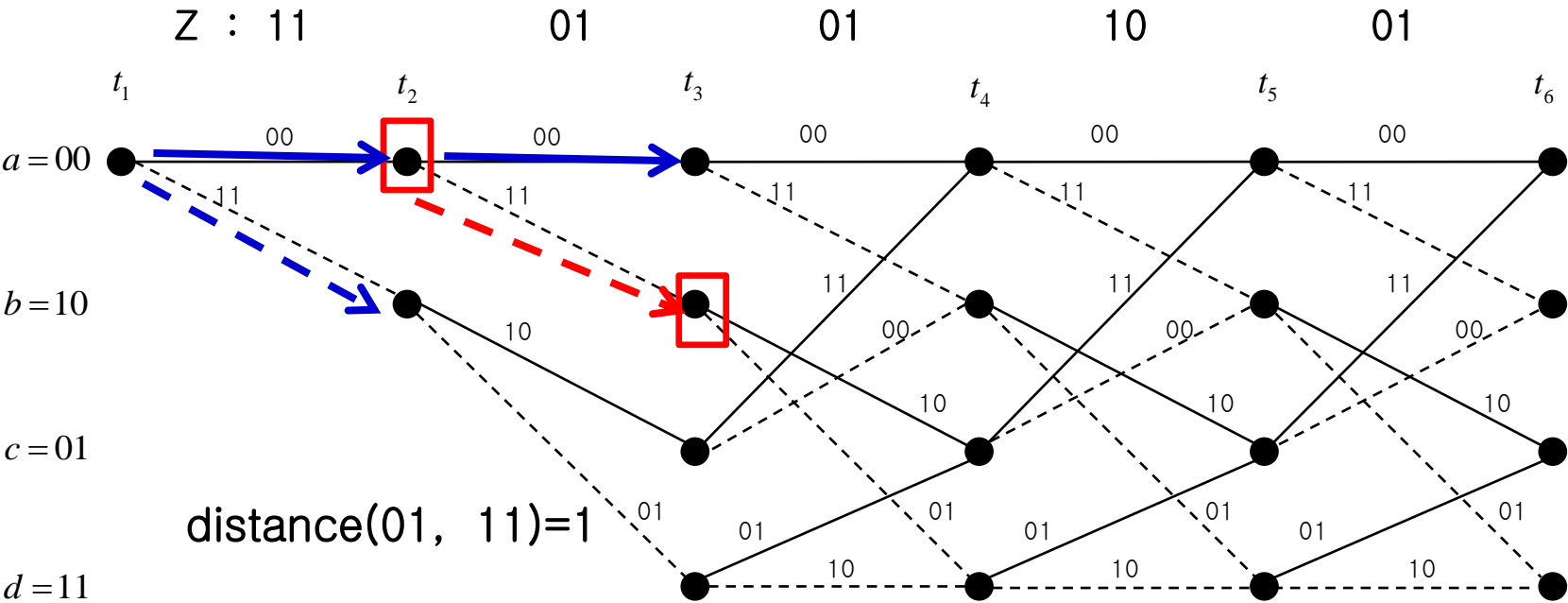
Z= decoder input, received (demodulated) sequence.



	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0					
d4	0					
output1	None	0	00			
output2	None	1	01 (Dashed line = 1)			
output3	None					
output4	None					




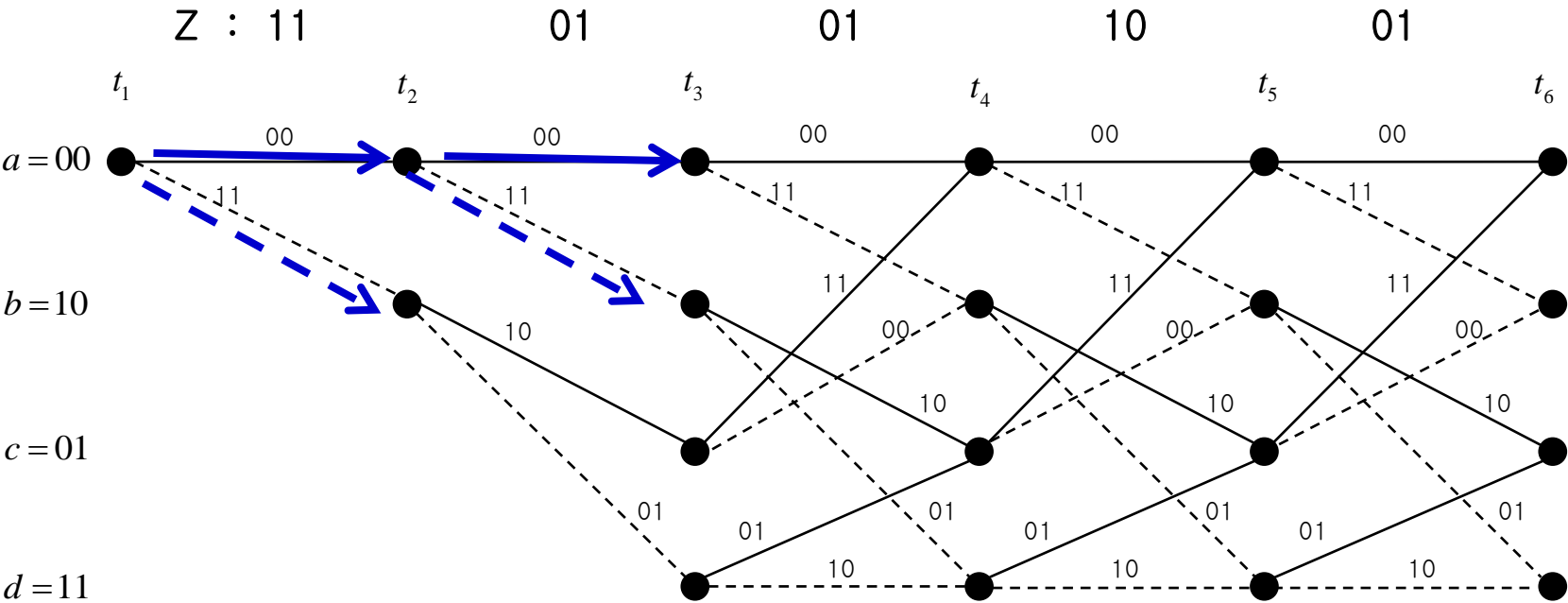Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0					
d4	0					
output1	None	0	00			
output2	None	1	01			
output3	None					
output4	None					

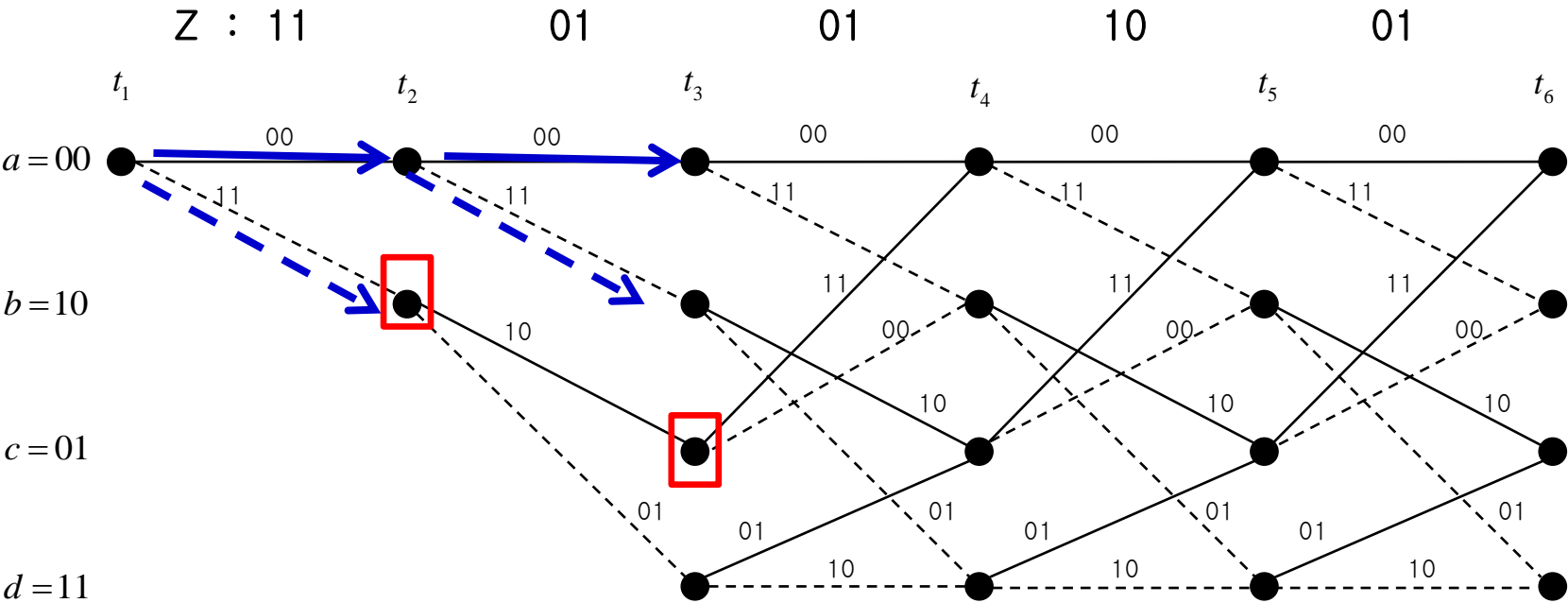Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0					
d4	0					
output1	None	0	00			
output2	None	1	01			
output3	None					
output4	None					

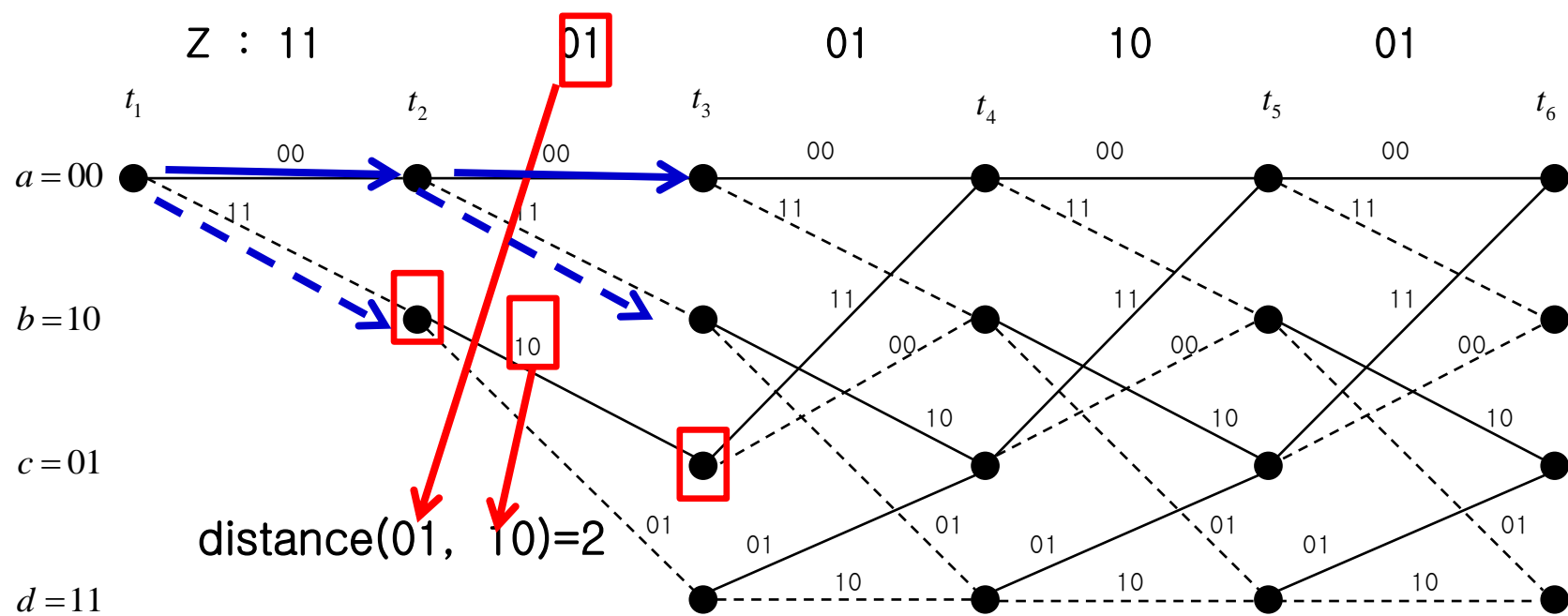Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0					
d4	0					
output1	None	0	00			
output2	None	1	01			
output3	None					
output4	None					

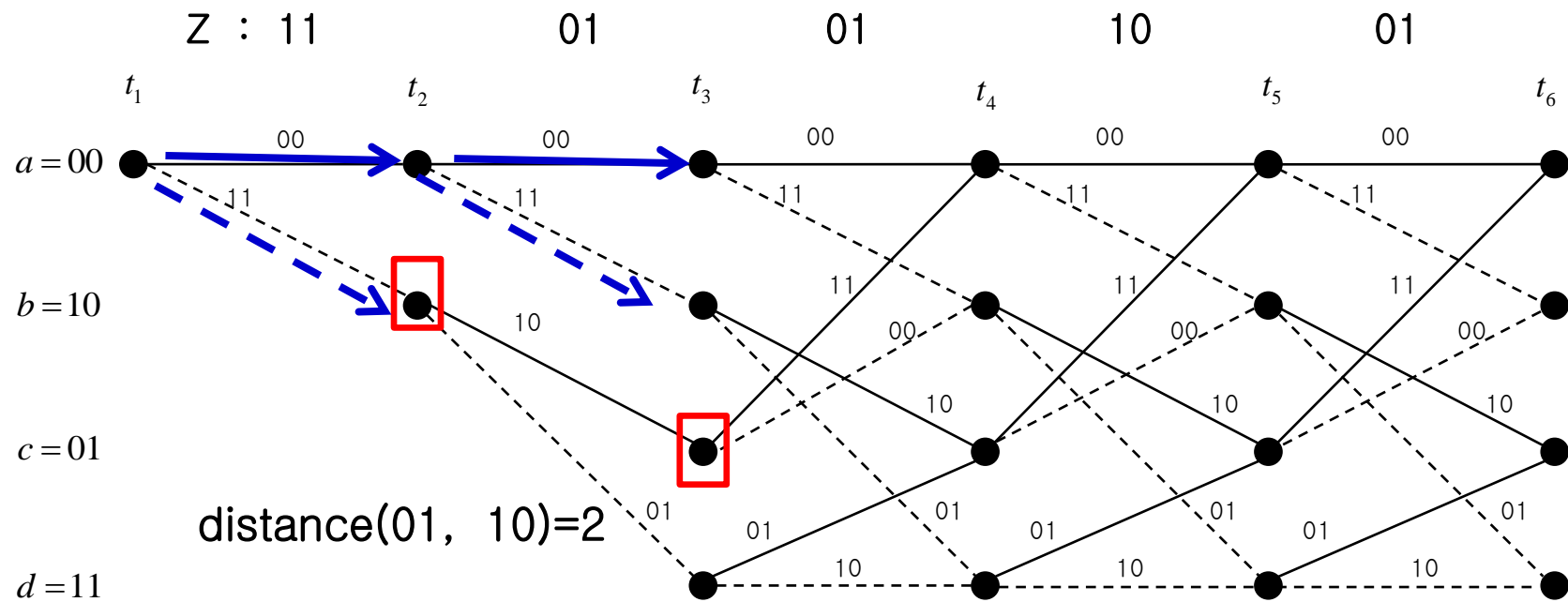Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0					
d4	0					
output1	None	0	00			
output2	None	1	01			
output3	None					
output4	None					

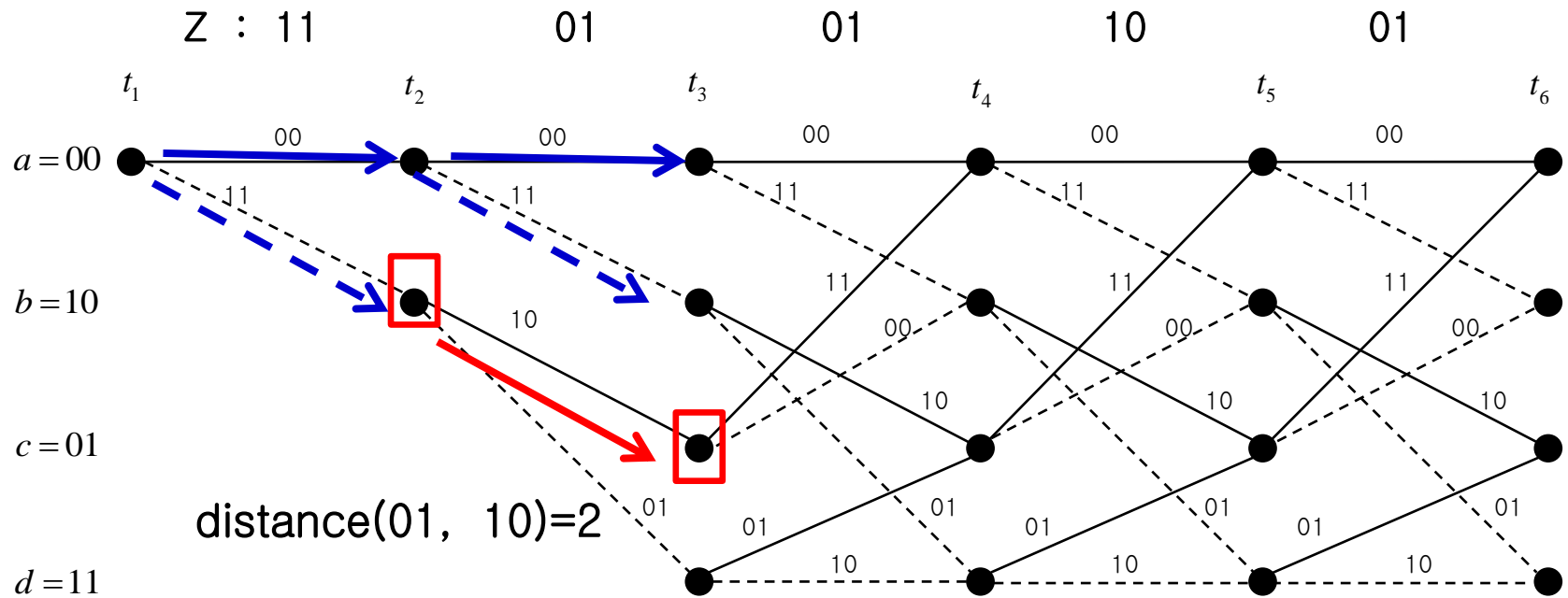Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0					
d4	0					
output1	None	0	00			
output2	None	1	01			
output3	None					
output4	None					

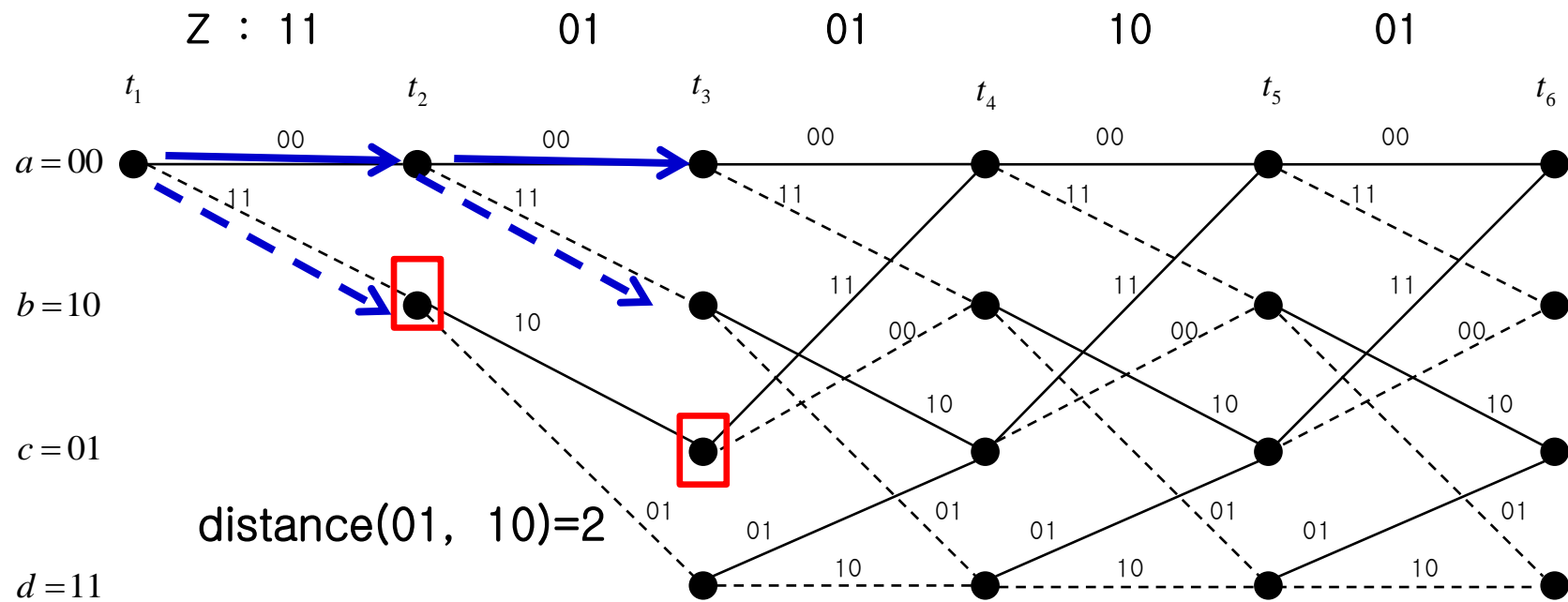Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0					
d4	0					
output1	None	0	00			
output2	None	1	01			
output3	None					
output4	None					

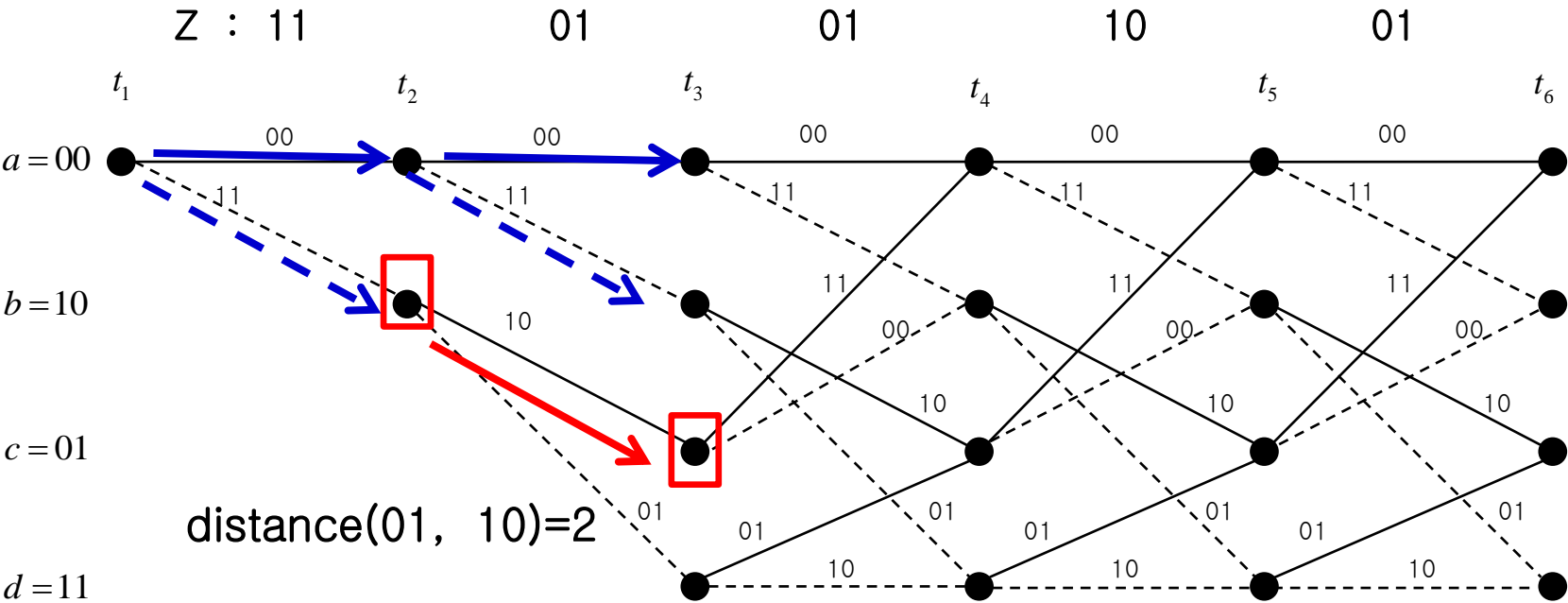Z= decoder input, received (demodulated) sequence.



	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0					
d4	0					
output1	None	0	00			
output2	None	1	01			
output3	None					
output4	None					

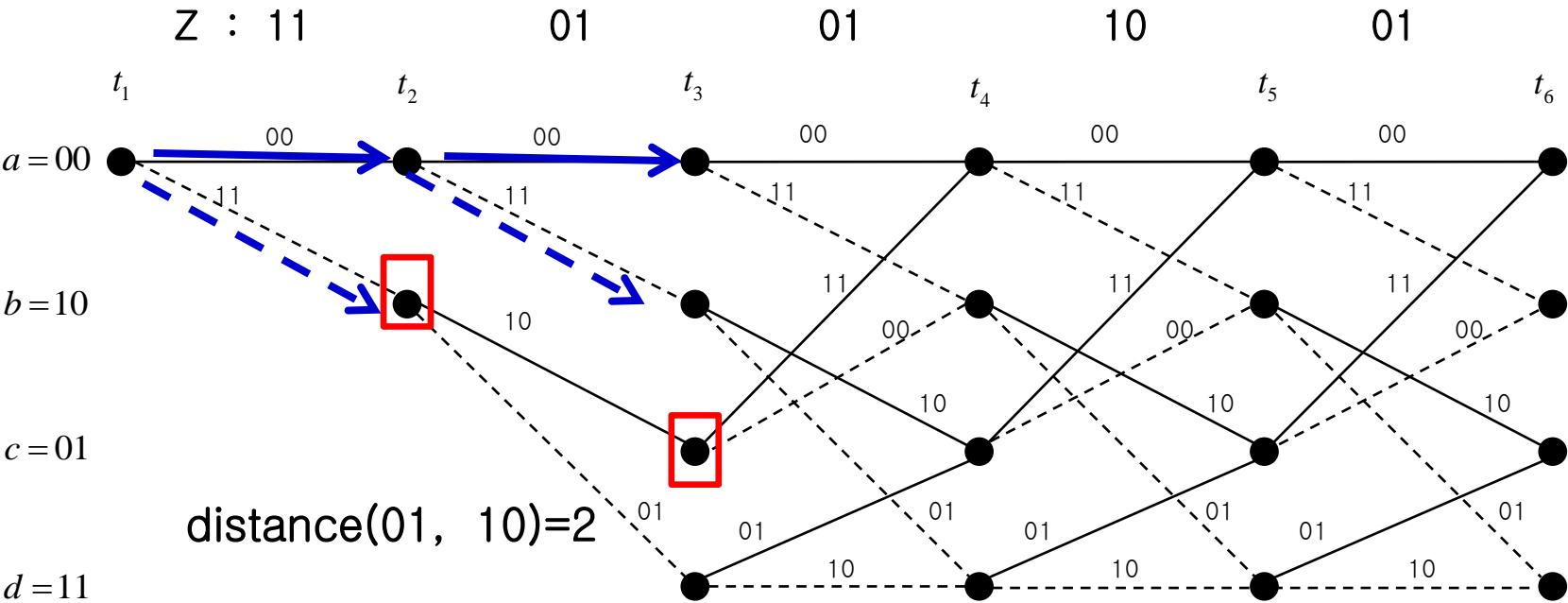
Z= decoder input, received (demodulated) sequence.



	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0					
d4	0					
output1	None	0	00			
output2	None	1	01			
output3	None					
output4	None					




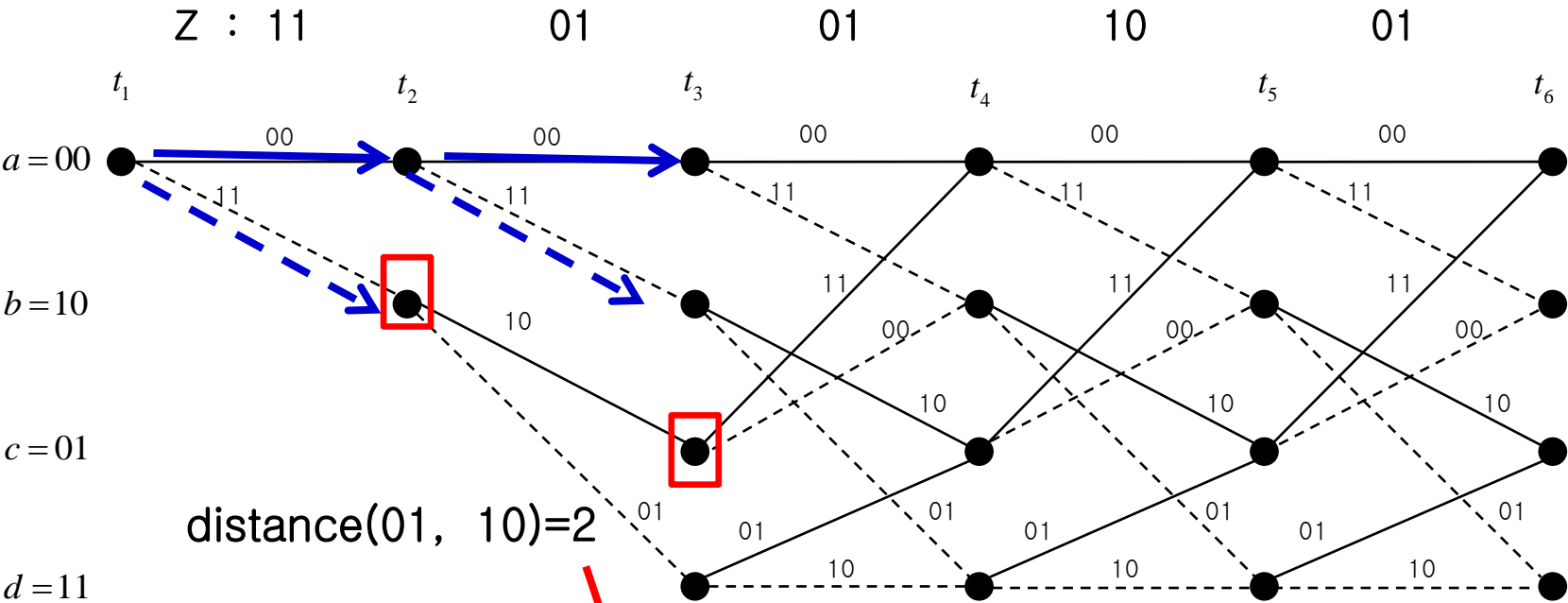Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0		0+2=2			
d4	0					
output1	None	0	00			
output2	None	1	01			
output3	None					
output4	None					

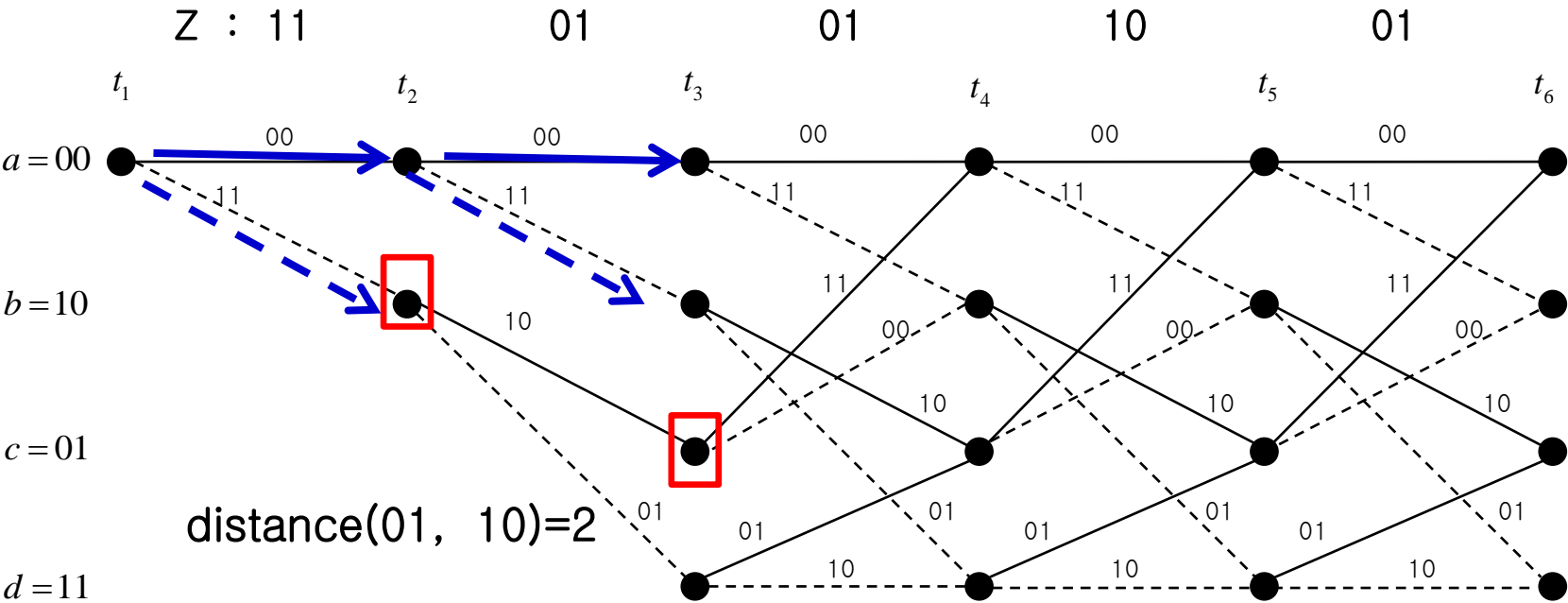Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0		2			
d4	0					
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None					

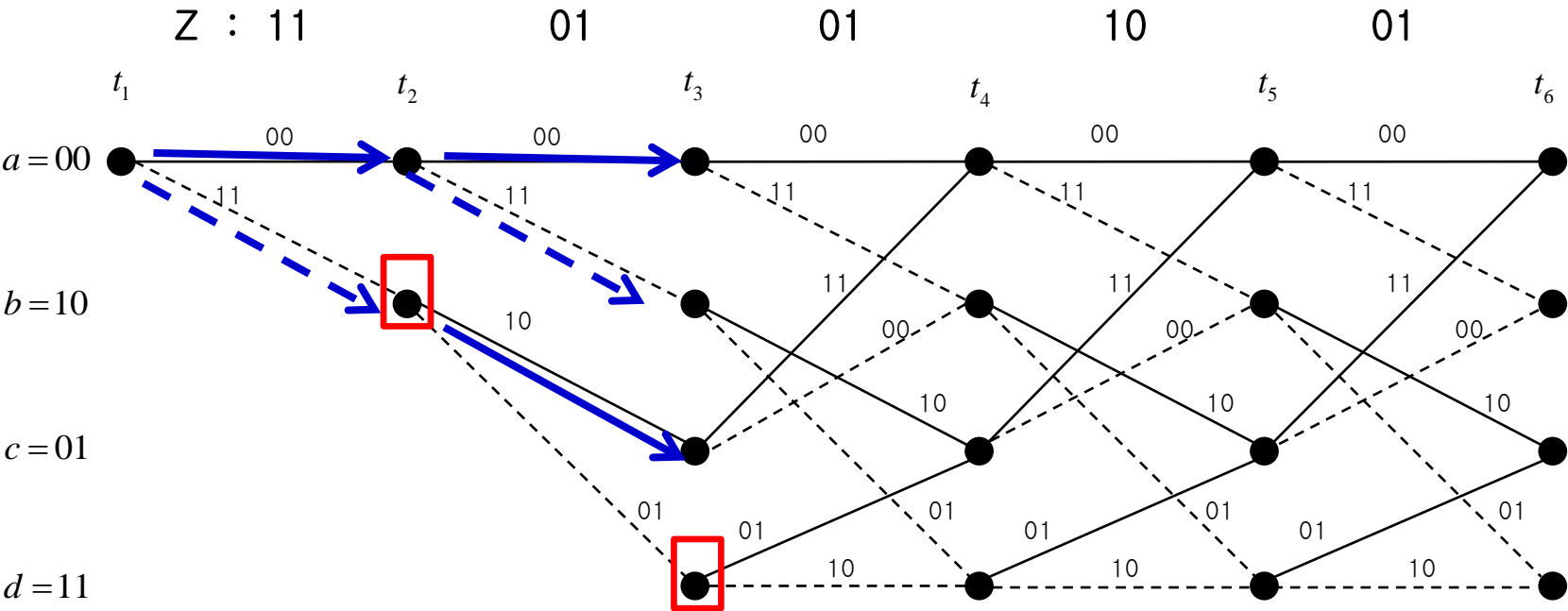Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0		2			
d4	0					
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None					

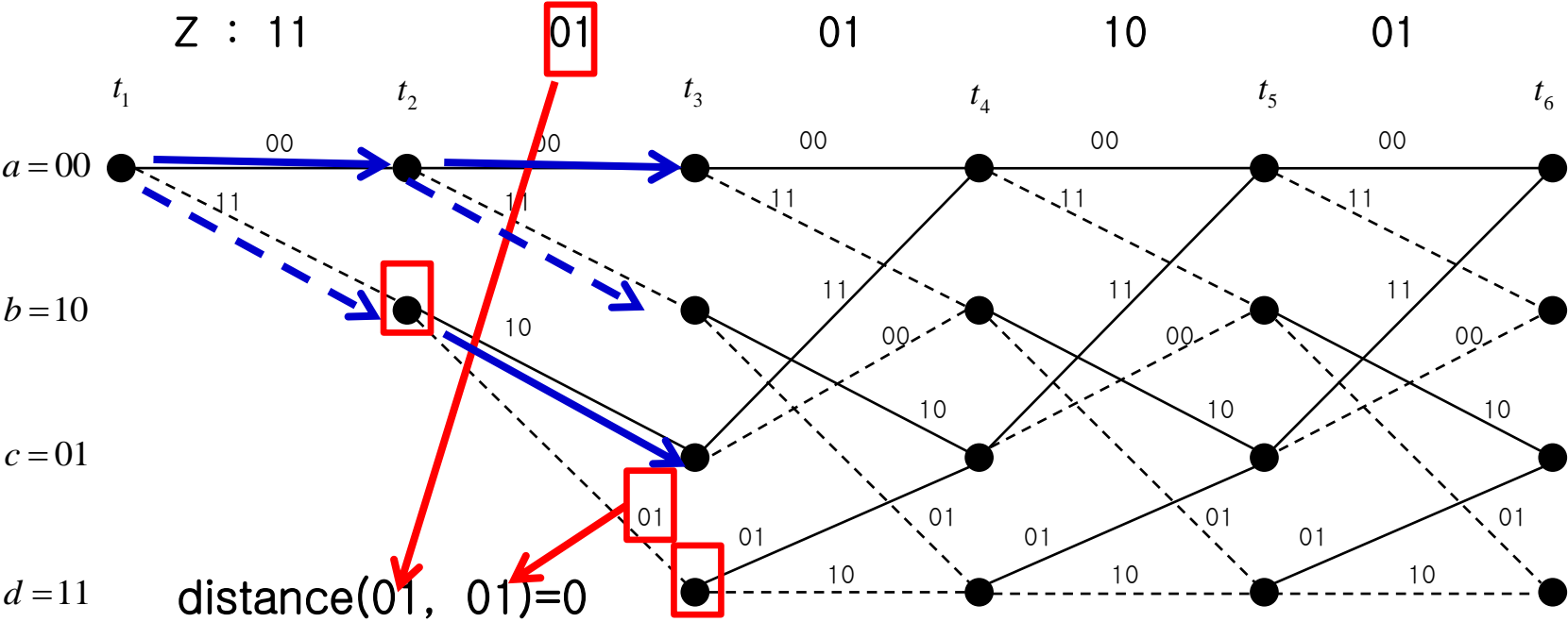Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0		2			
d4	0					
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None					

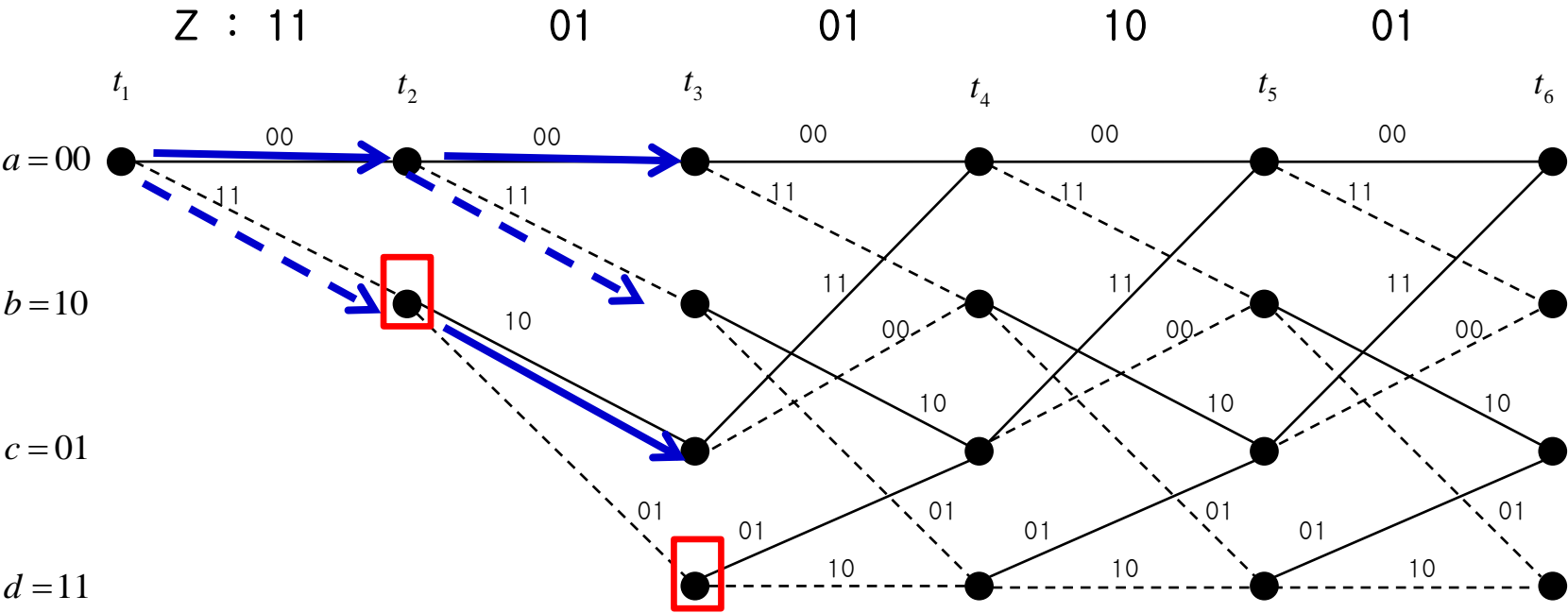Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0		2			
d4	0					
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None					

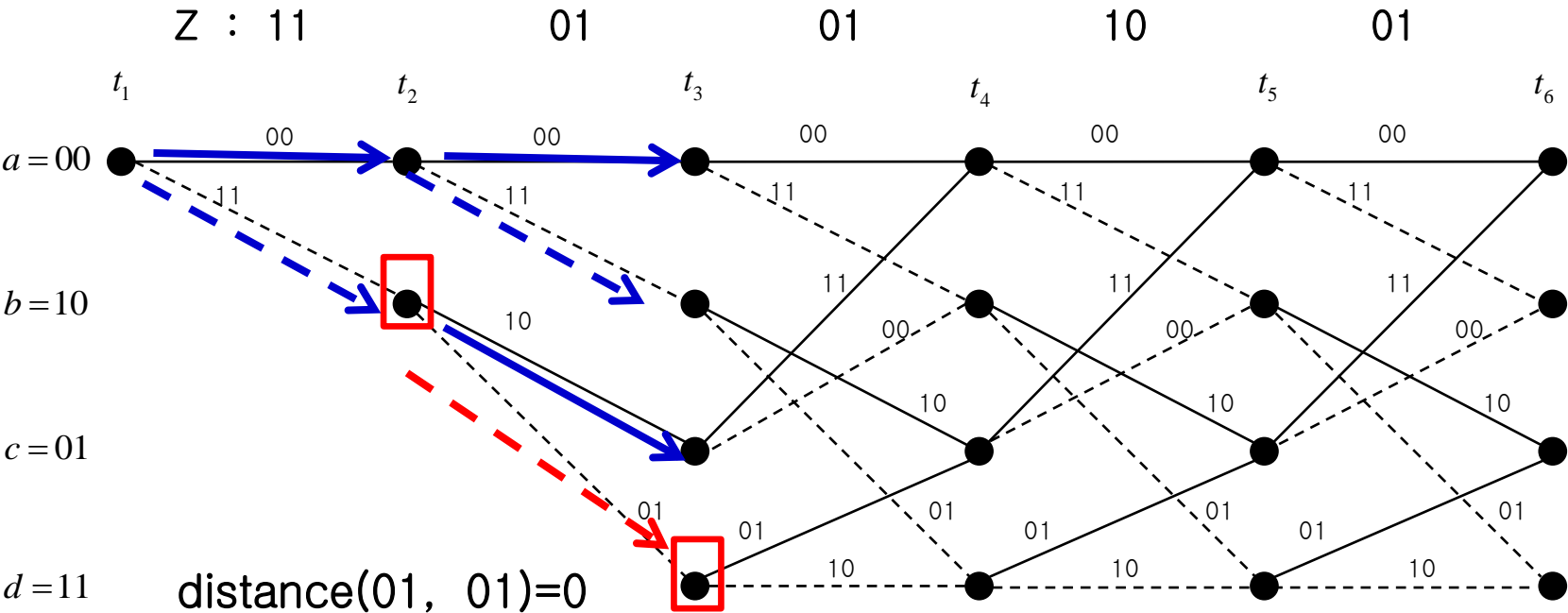Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0		2			
d4	0					
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None					

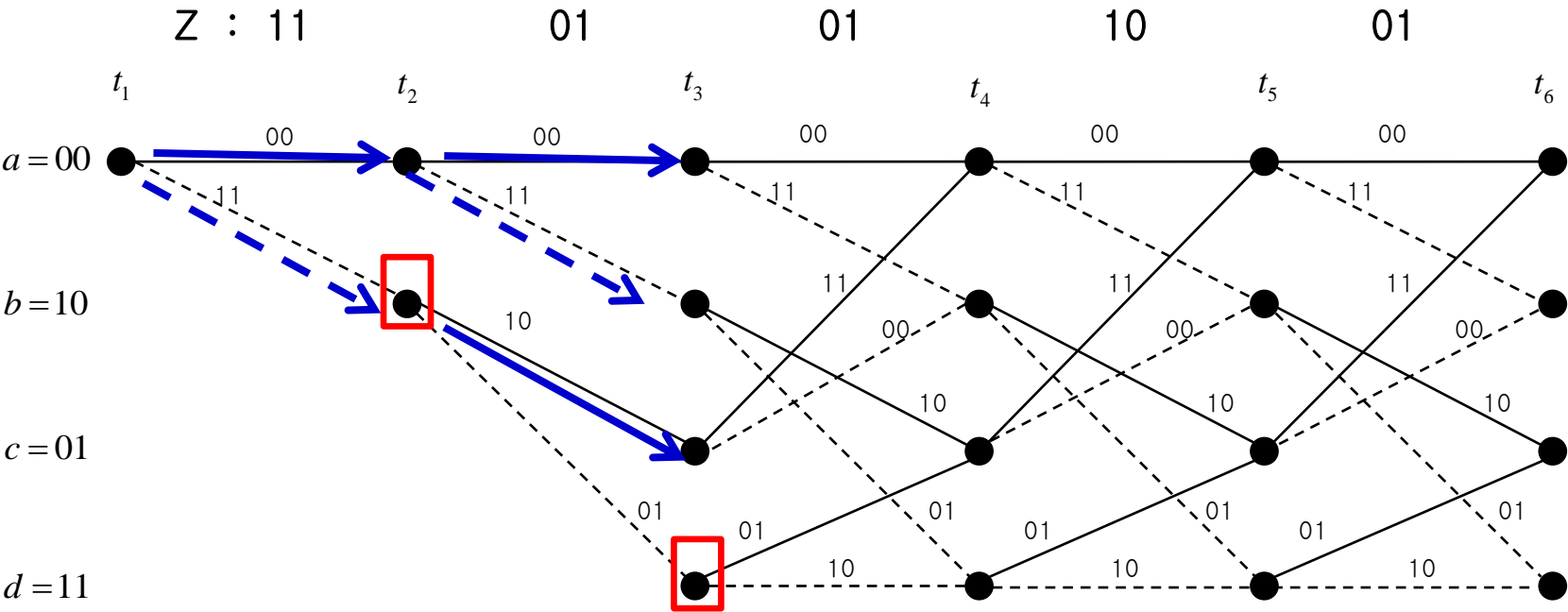Z= decoder input, received (demodulated) sequence.



	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0		2			
d4	0					
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None					

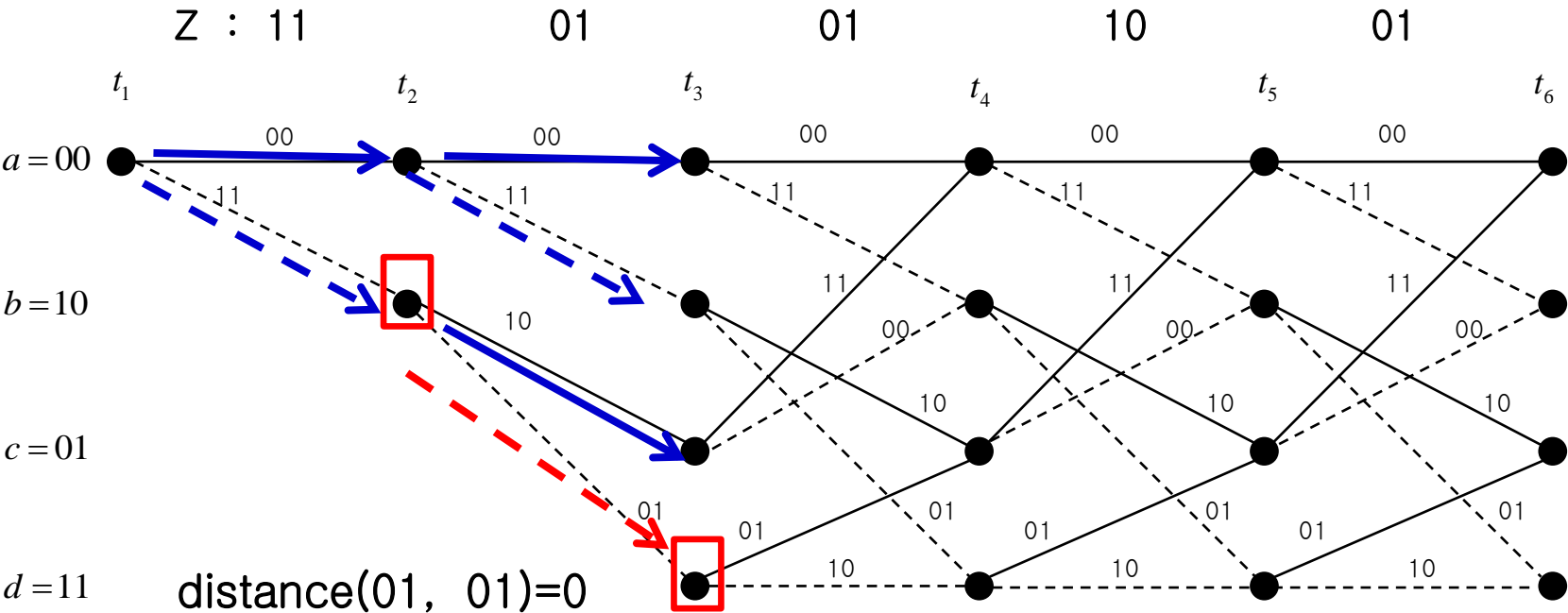
Z= decoder input, received (demodulated) sequence.



	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0		2			
d4	0					
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None					




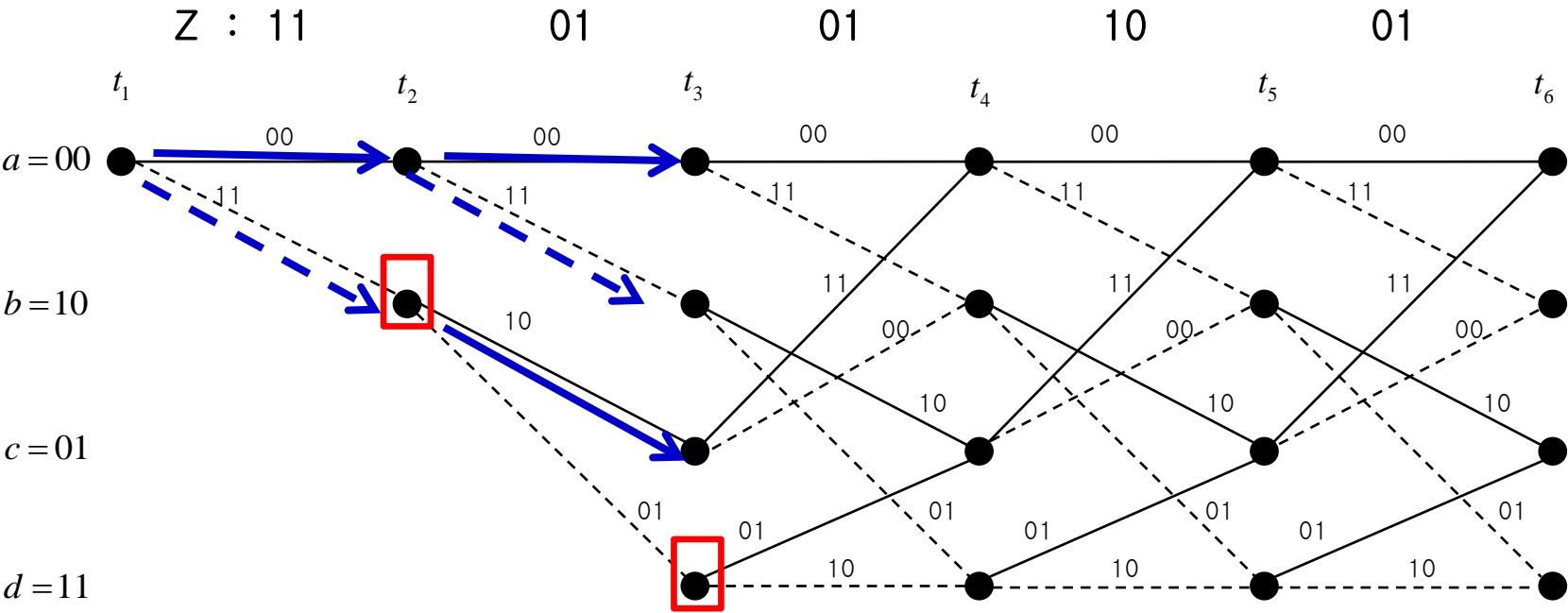Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0		2			
d4	0					
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None					

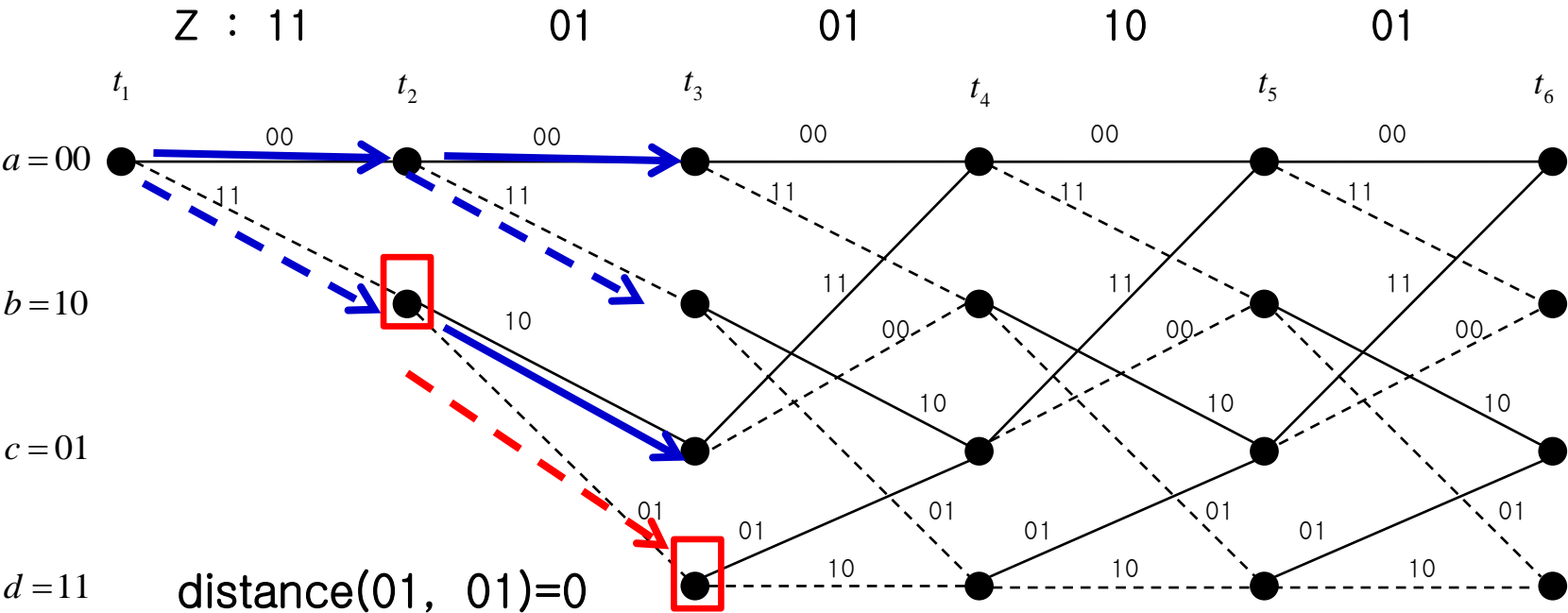Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0		2			
d4	0					
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None					

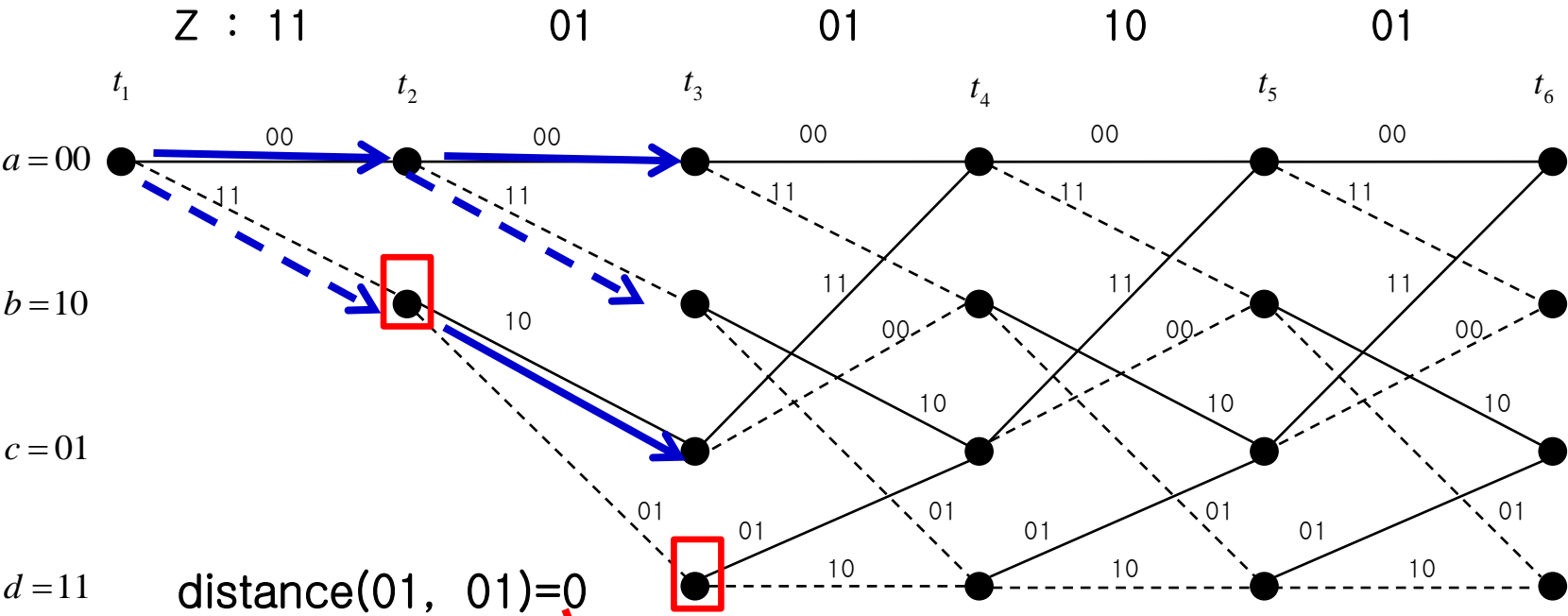Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0		2			
d4	0		0+0=0			
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None					

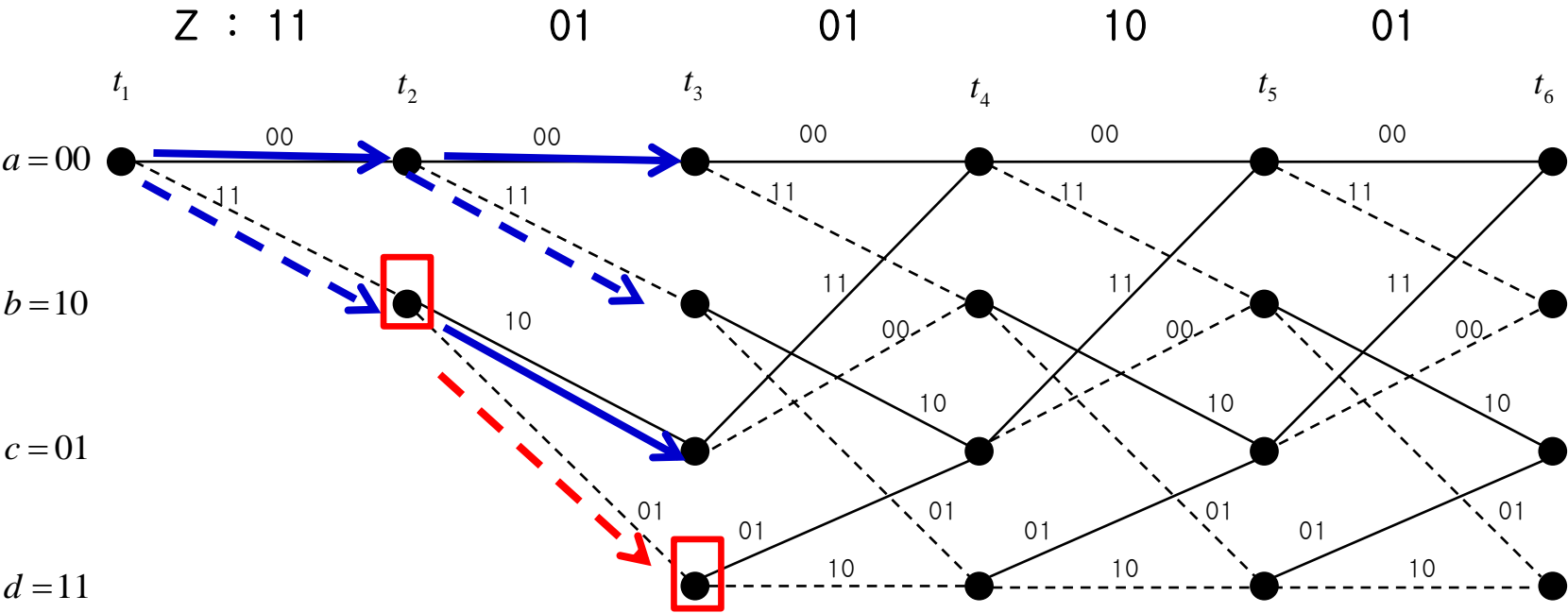Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0		2			
d4	0		0			
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None		11			

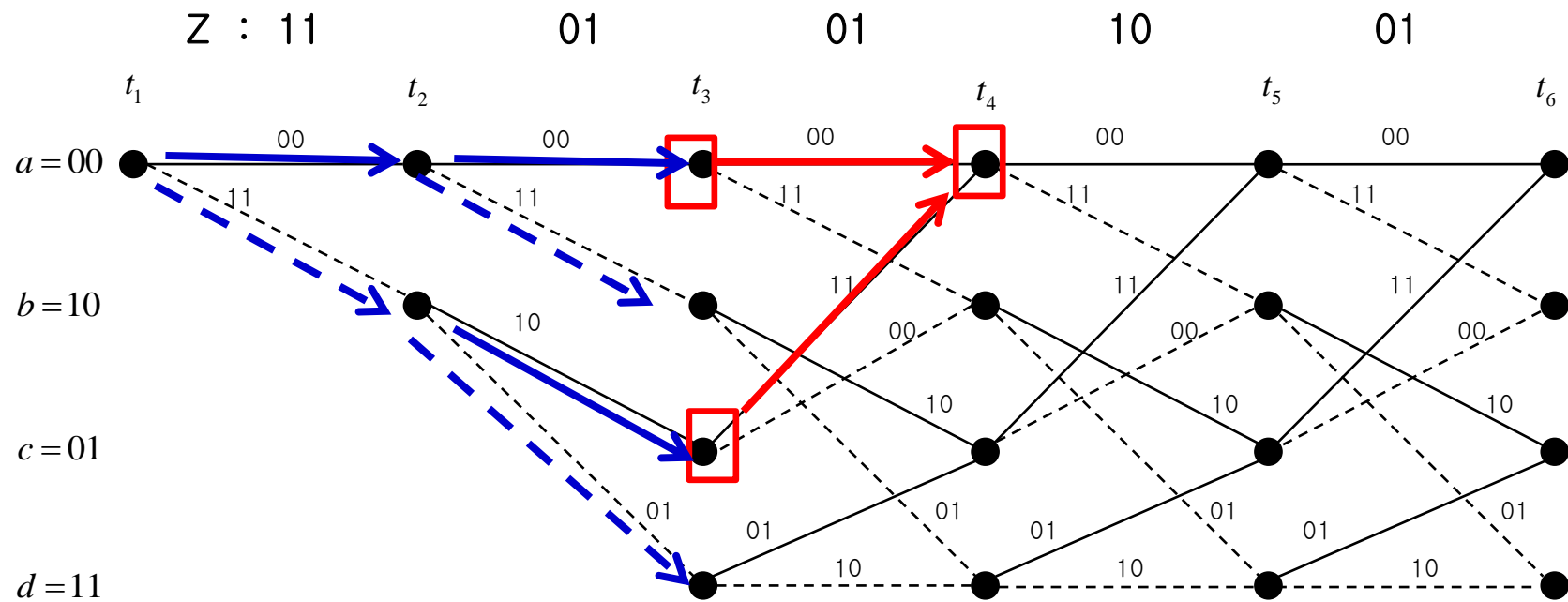Z= decoder input, received (demodulated) sequence.




`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0		2			
d4	0		0			
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None		11			

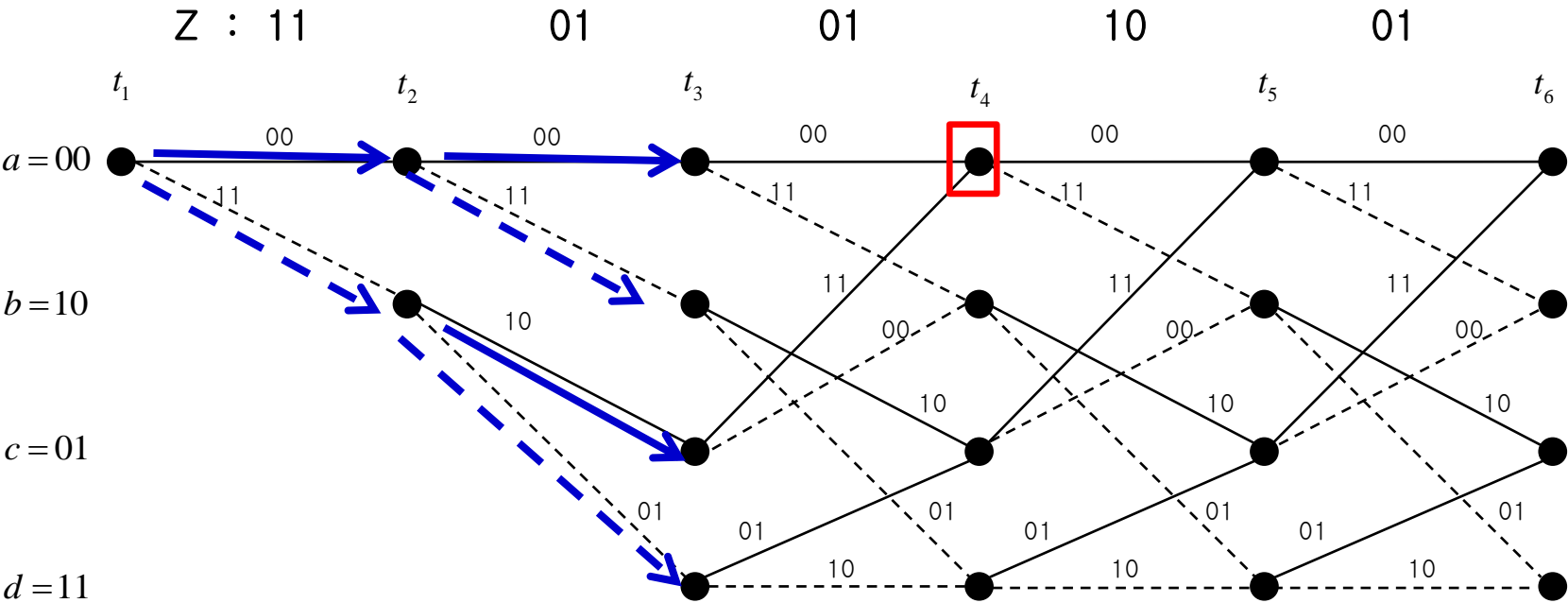Z= decoder input, received (demodulated) sequence.




`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0		2			
d4	0		0			
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None		11			

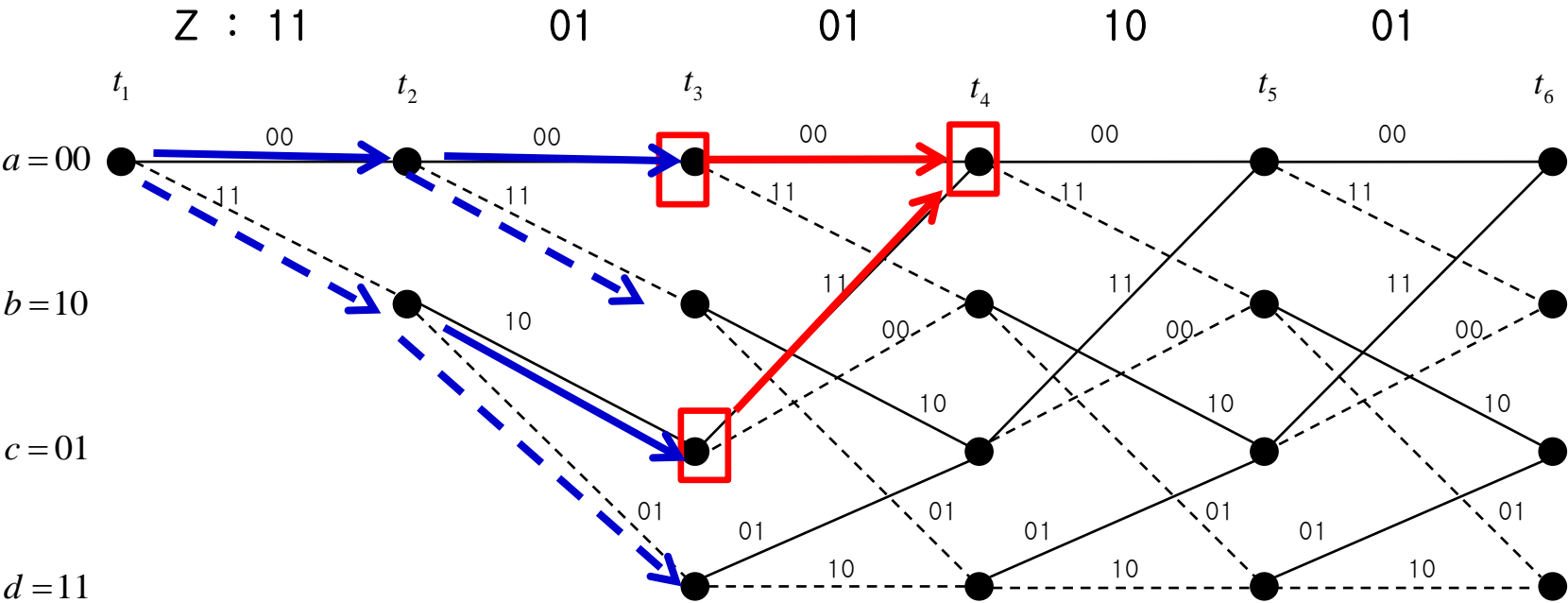Z= decoder input, received (demodulated) sequence.



`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0		2			
d4	0		0			
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None		11			

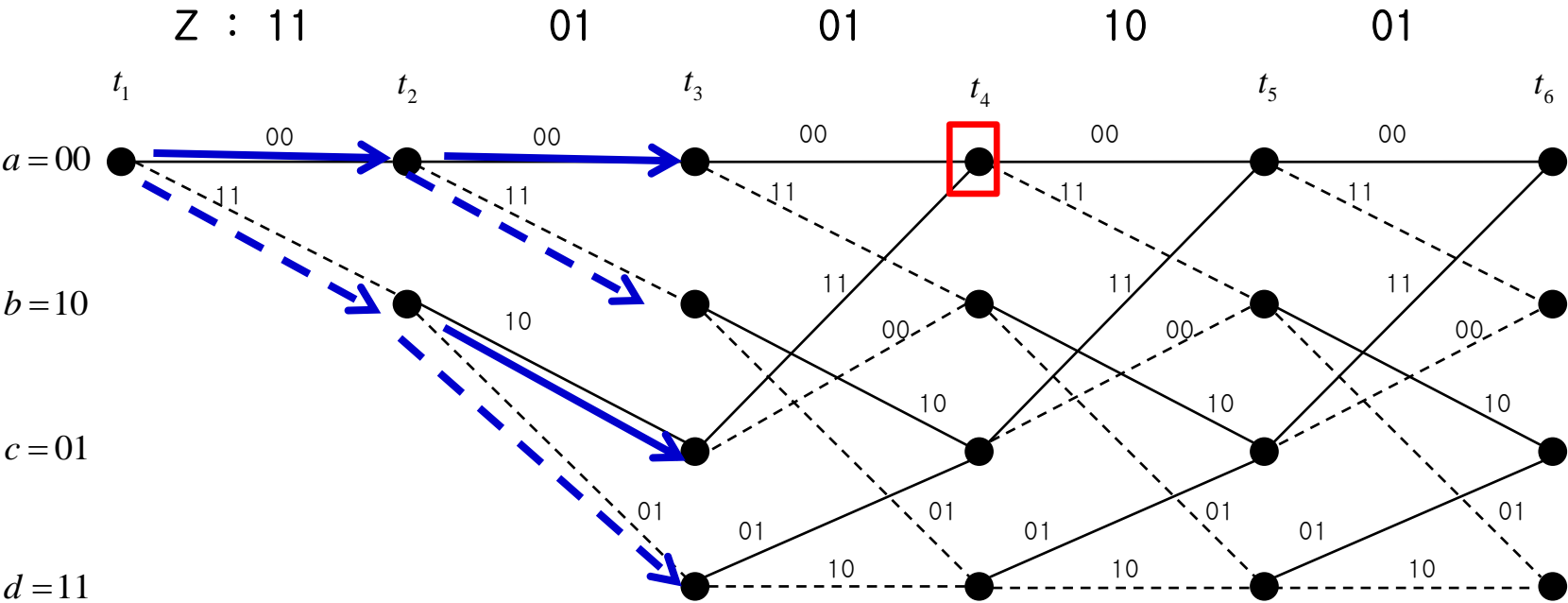
Z= decoder input, received (demodulated) sequence.



`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0		2			
d4	0		0			
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None		11			




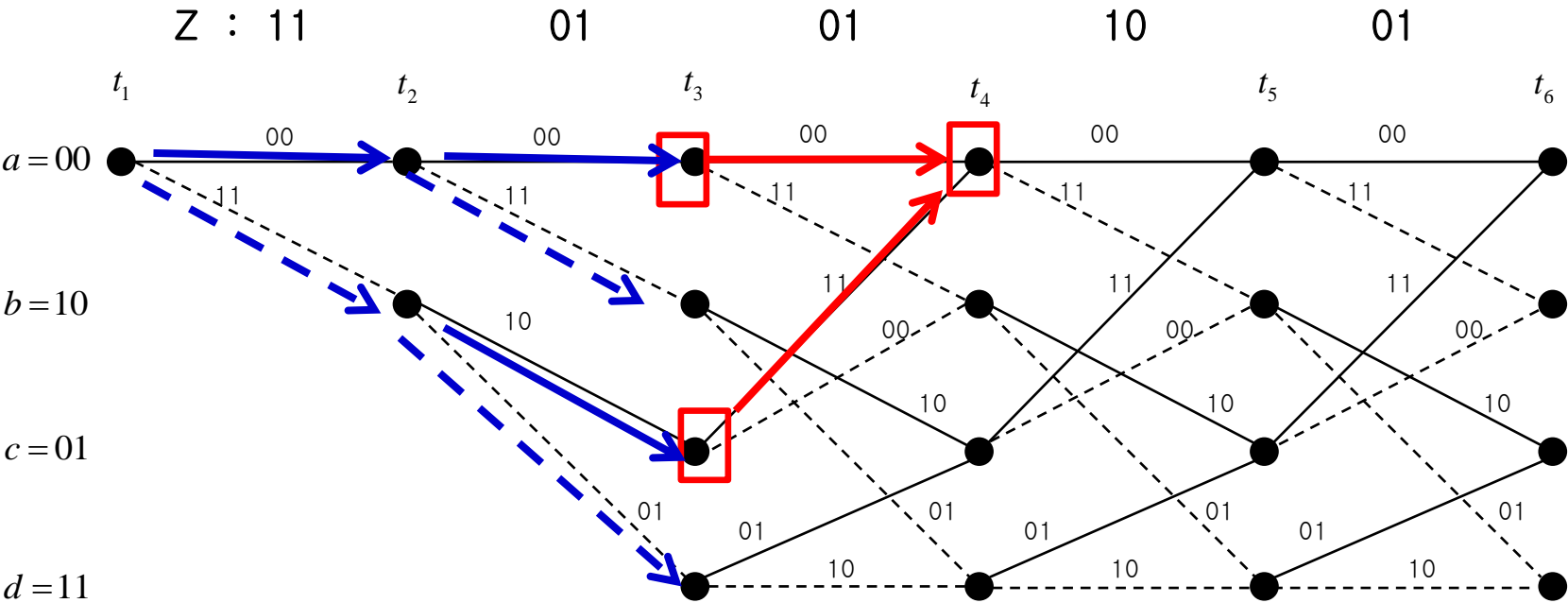Z= decoder input, received (demodulated) sequence.




`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0		2			
d4	0		0			
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None		11			

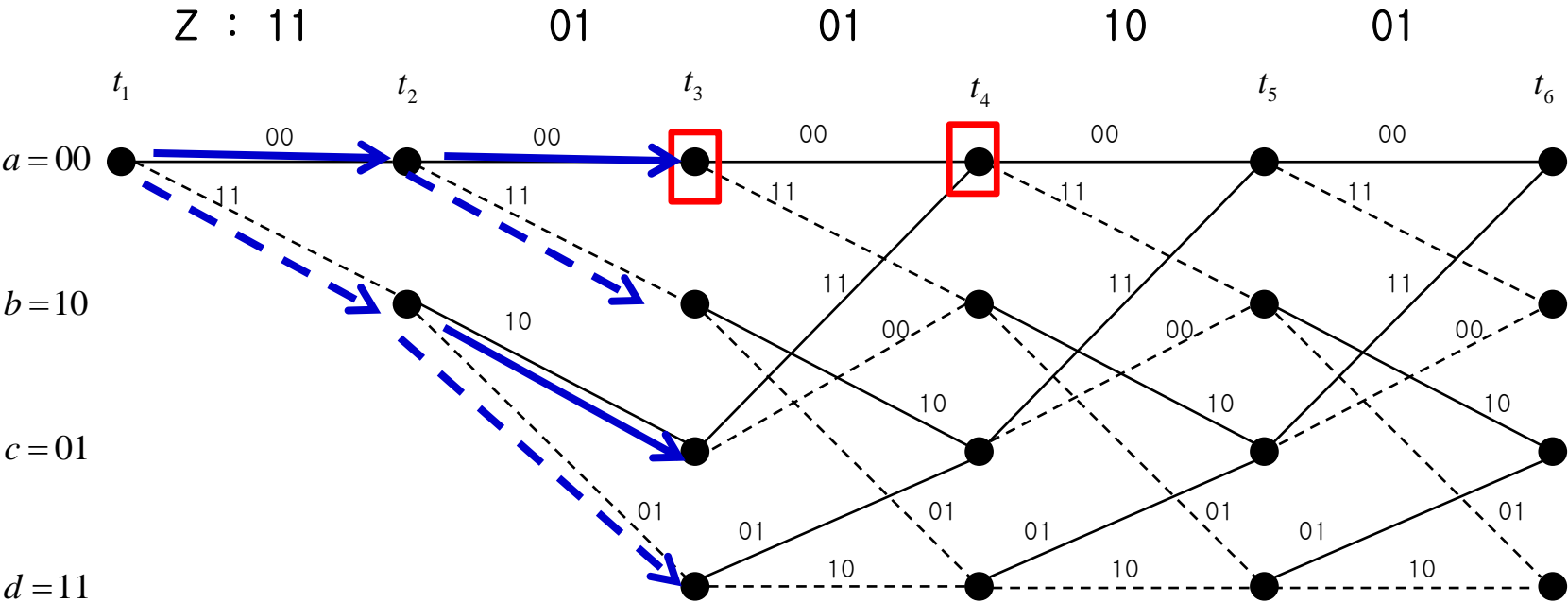Z= decoder input, received (demodulated) sequence.




	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0		2			
d4	0		0			
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None		11			

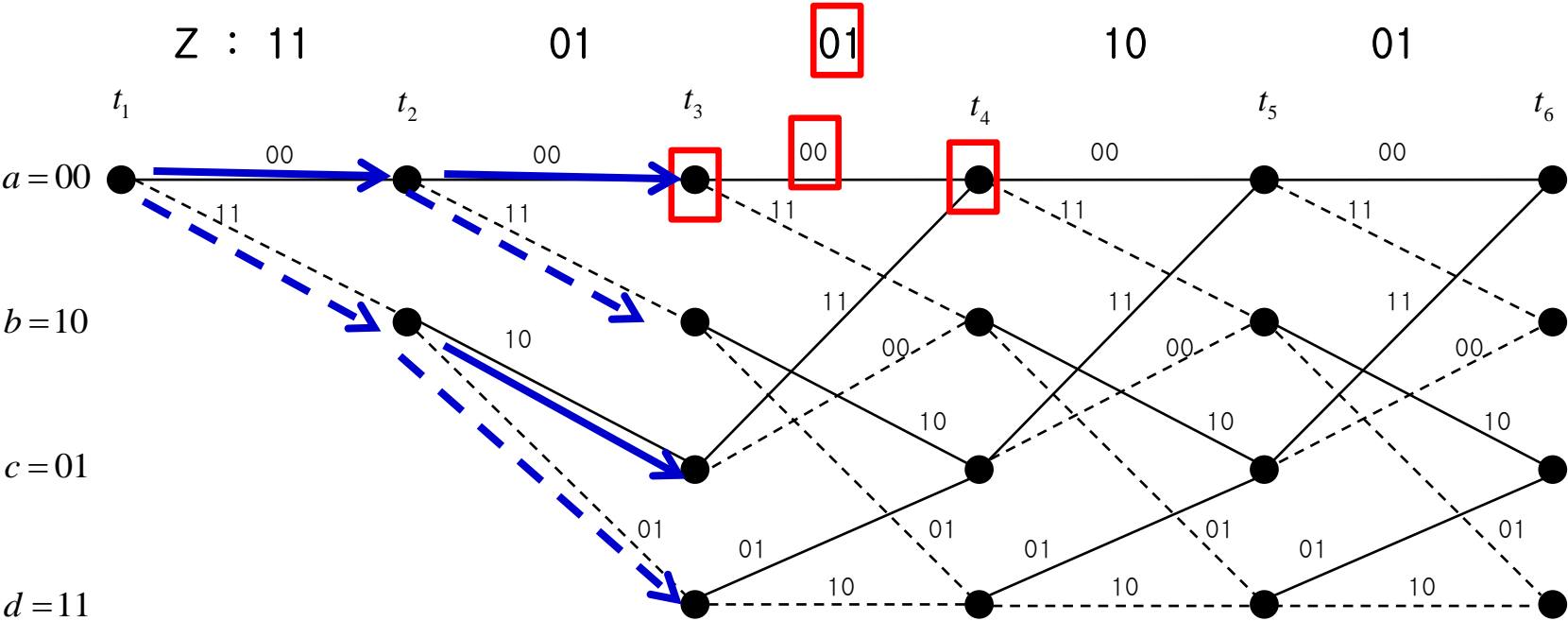Z= decoder input, received (demodulated) sequence.




`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0		2			
d4	0		0			
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None		11			

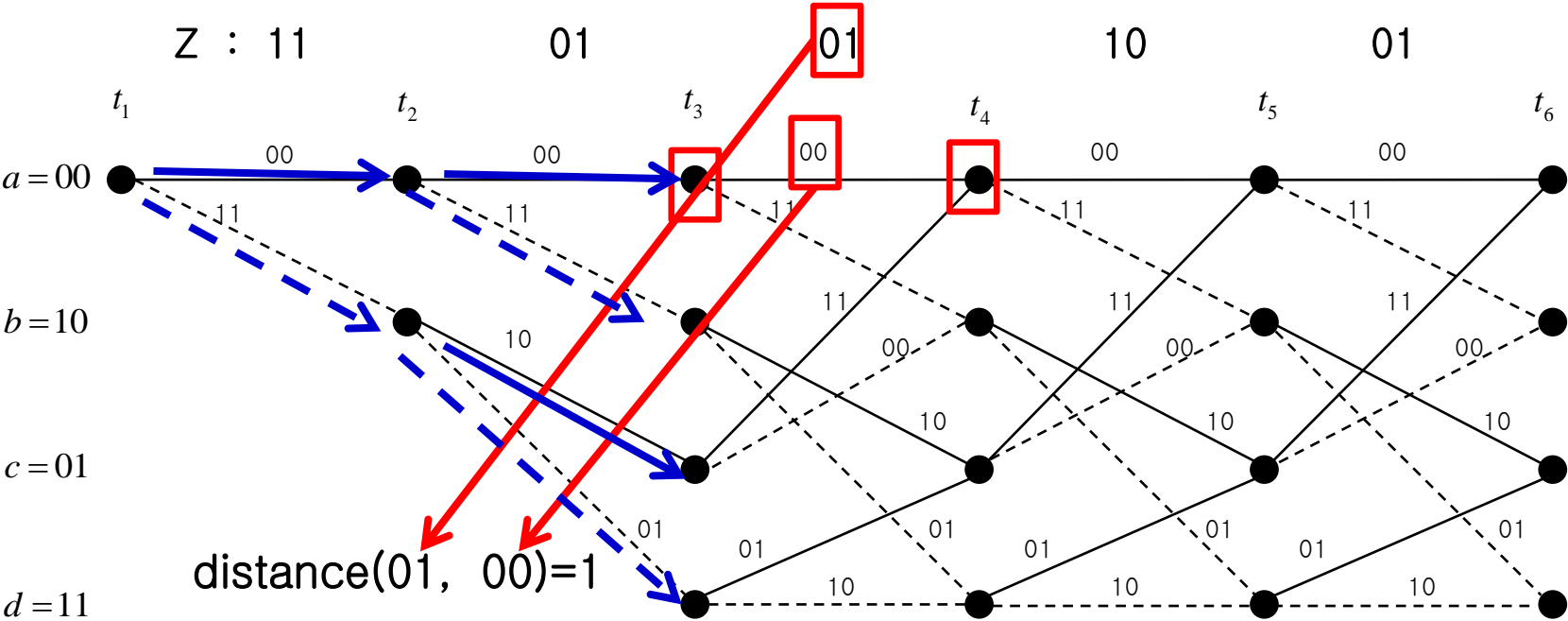Z= decoder input, received (demodulated) sequence.




`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3			
d2	0	0	3			
d3	0		2			
d4	0		0			
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None		11			

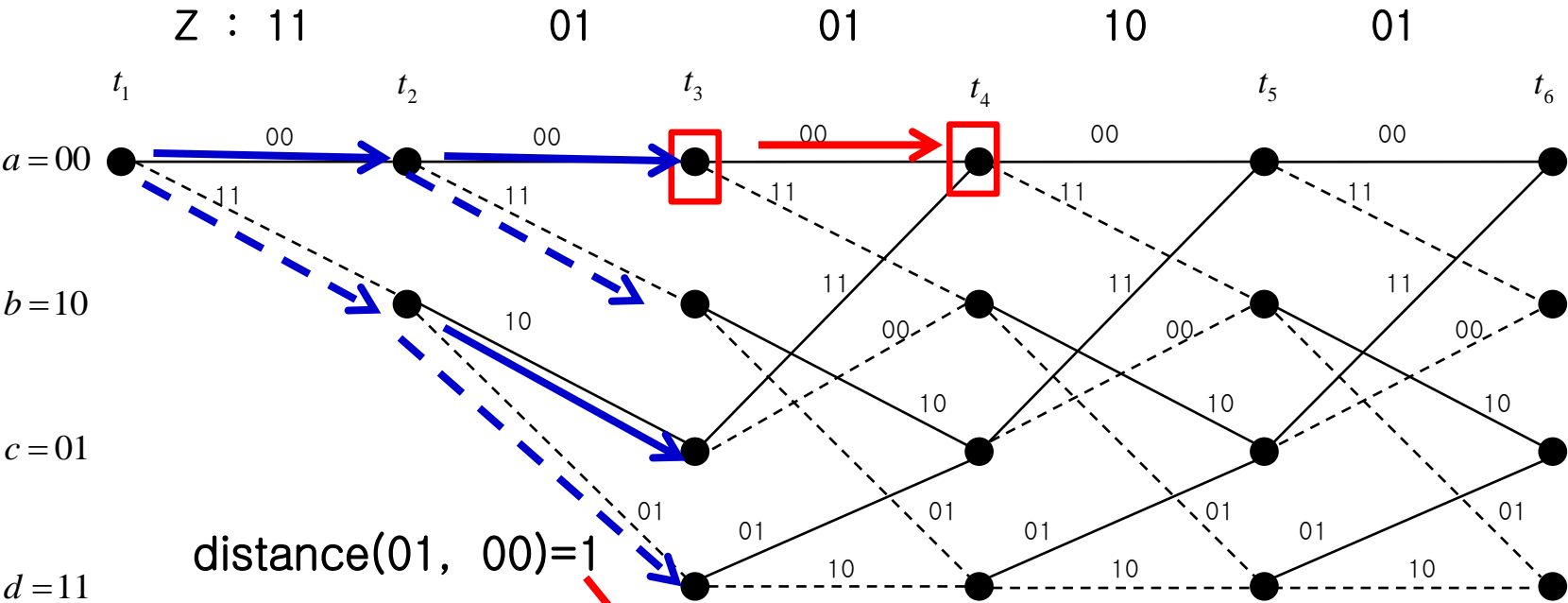Z= decoder input, received (demodulated) sequence.




	t <sub>1</sub> =0	t <sub>1</sub> ->t <sub>2</sub>	t <sub>2</sub> ->t <sub>3</sub>	t <sub>3</sub> ->t <sub>4</sub>	t <sub>4</sub> ->t <sub>5</sub>	t <sub>5</sub> ->t <sub>6</sub>
d1	0	2	3+1	4		
d2	0	0	3			
d3	0		2			
d4	0		0			
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None		11			

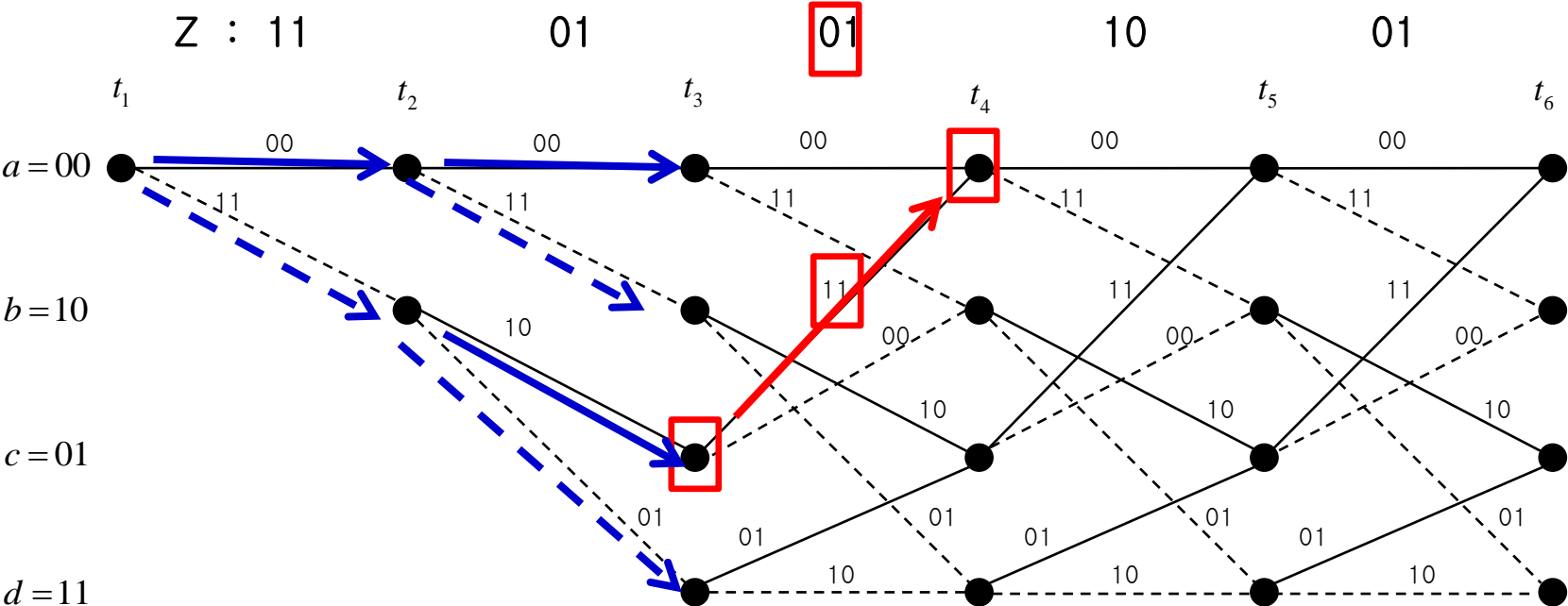Z= decoder input, received (demodulated) sequence.




`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3	4		
d2	0	0	3			
d3	0		2			
d4	0		0			
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None		11			

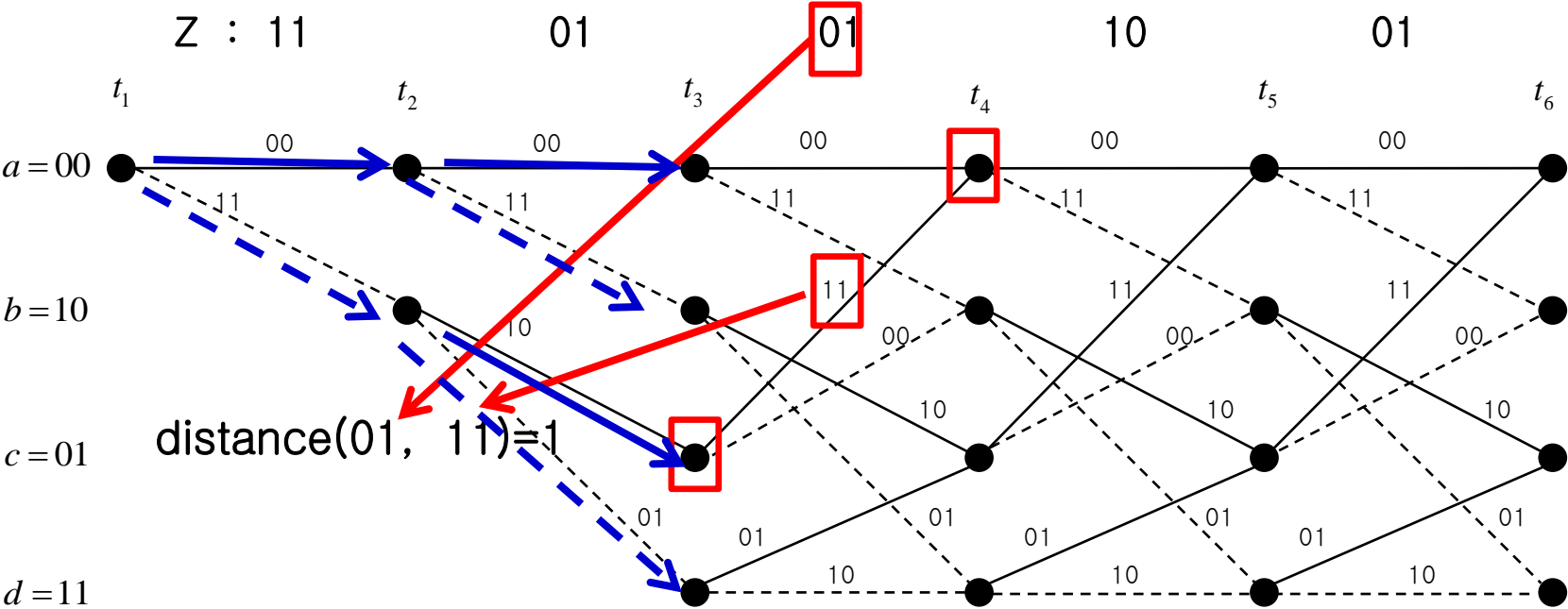Z= decoder input, received (demodulated) sequence.



`	t <sub>1</sub> =0	t <sub>1</sub> ->t <sub>2</sub>	t <sub>2</sub> ->t <sub>3</sub>	t <sub>3</sub> ->t <sub>4</sub>	t <sub>4</sub> ->t <sub>5</sub>	t <sub>5</sub> ->t <sub>6</sub>
d1	0	2	3	4		
d2	0	0	3			
d3	0		2			
d4	0		0			
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None		11			

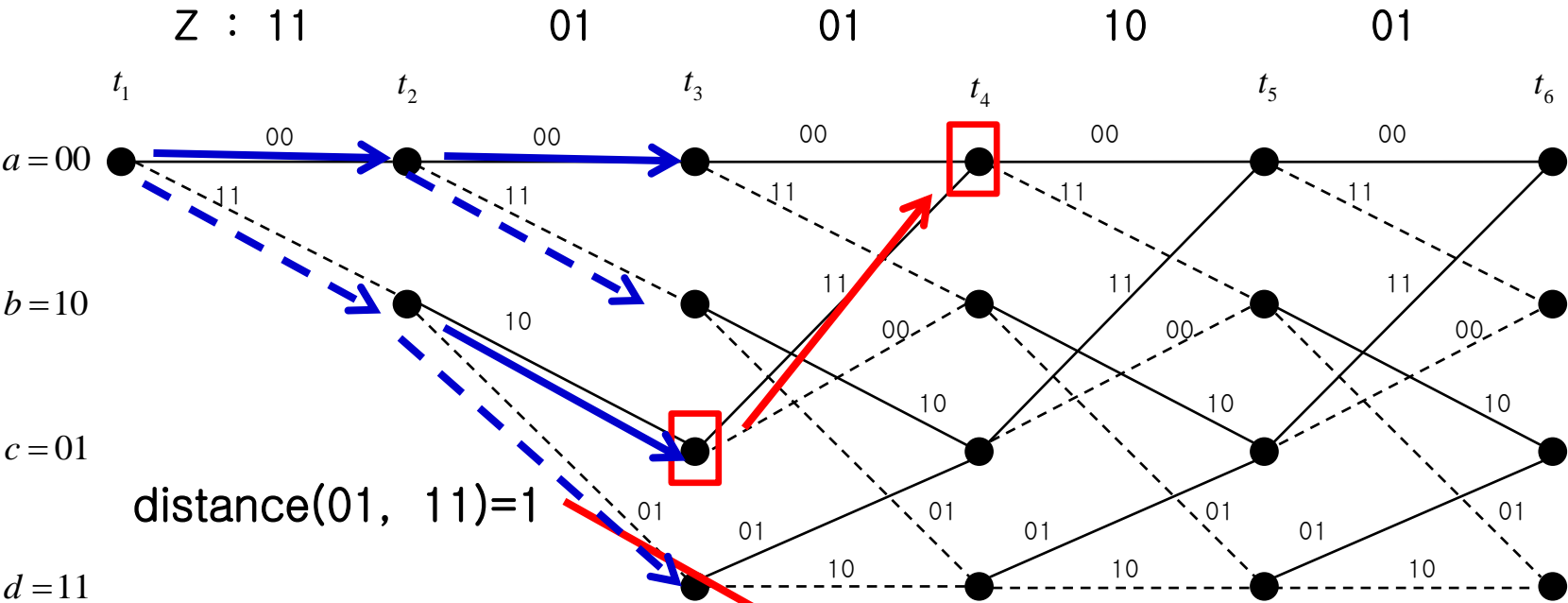
Z= decoder input, received (demodulated) sequence.



`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3	(4, 2+1=3)		
d2	0	0	3			
d3	0		2			
d4	0		0			
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None		11			




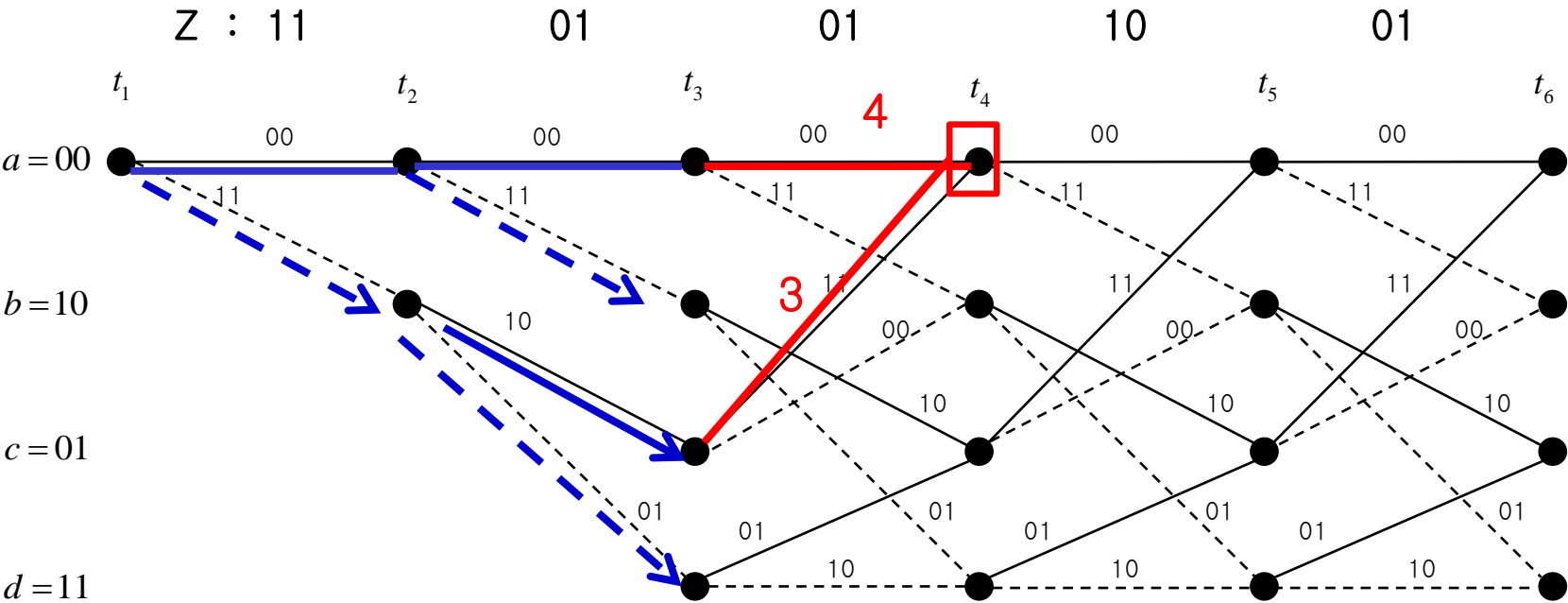Z= decoder input, received (demodulated) sequence.




`	t <sub>1</sub> =0	t <sub>1</sub> ->t <sub>2</sub>	t <sub>2</sub> ->t <sub>3</sub>	t <sub>3</sub> ->t <sub>4</sub>	t <sub>4</sub> ->t <sub>5</sub>	t <sub>5</sub> ->t <sub>6</sub>
d1	0	2	3	(4, 3)		
d2	0	0	3			
d3	0		2			
d4	0		0			
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None		11			

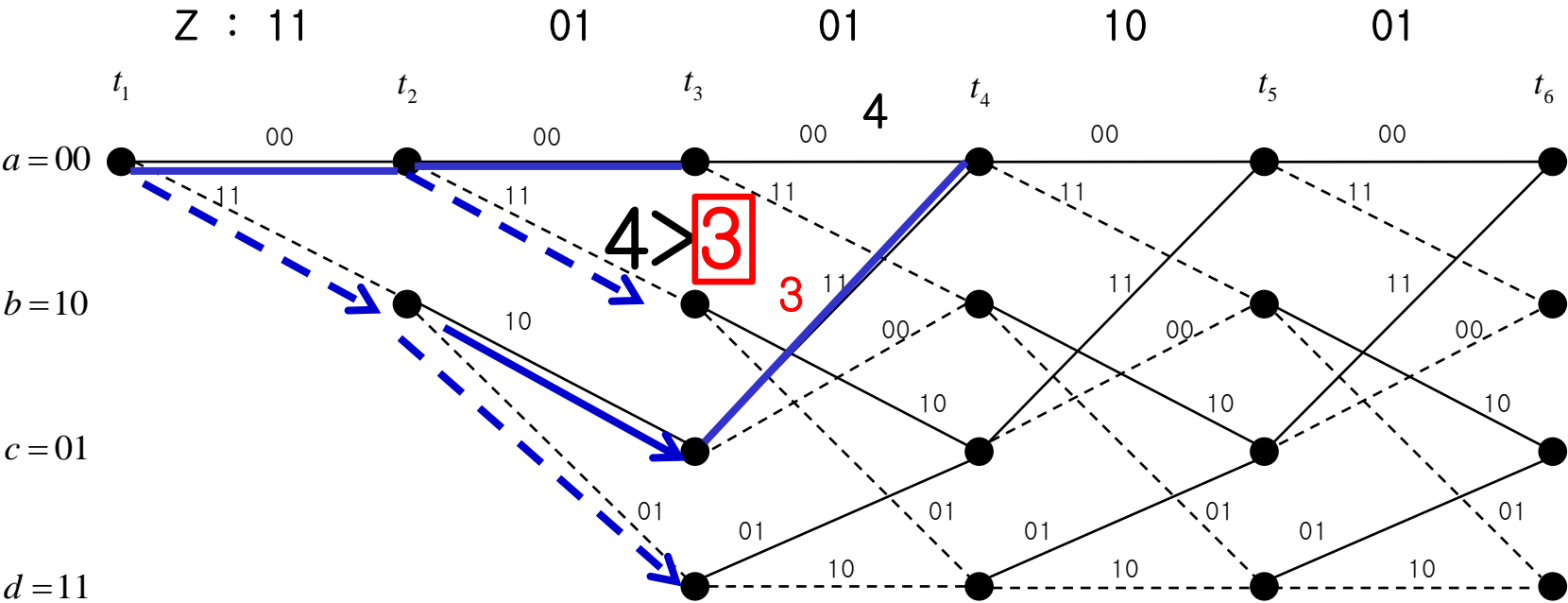Z= decoder input, received (demodulated) sequence.




`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3	3		
d2	0	0	3			
d3	0		2			
d4	0		0			
output1	None	0	00			
output2	None	1	01			
output3	None		10			
output4	None		11			

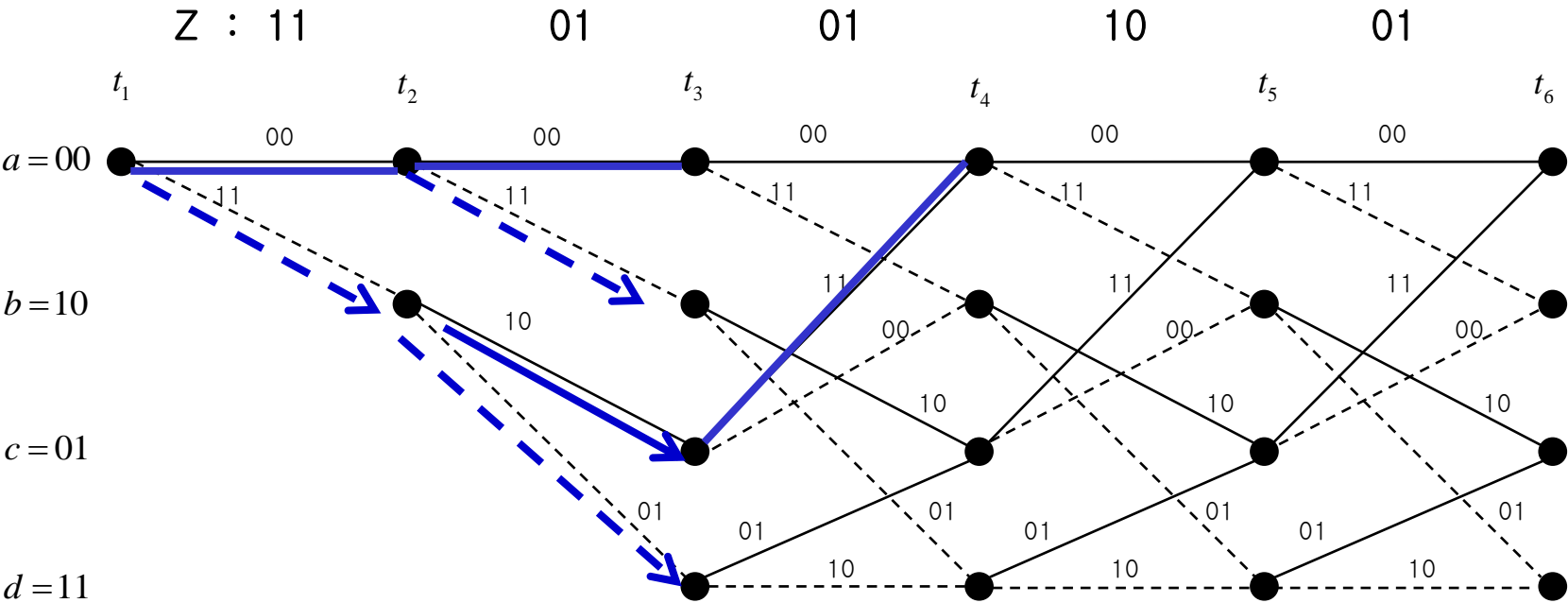Z= decoder input, received (demodulated) sequence.




`	t <sub>1</sub> =0	t <sub>1</sub> ->t <sub>2</sub>	t <sub>2</sub> ->t <sub>3</sub>	t <sub>3</sub> ->t <sub>4</sub>	t <sub>4</sub> ->t <sub>5</sub>	t <sub>5</sub> ->t <sub>6</sub>
d1	0	2	3	3		
d2	0	0	3			
d3	0		2			
d4	0		0			
output1	None	0	00	100		
output2	None	1	01			
output3	None		10			
output4	None		11			

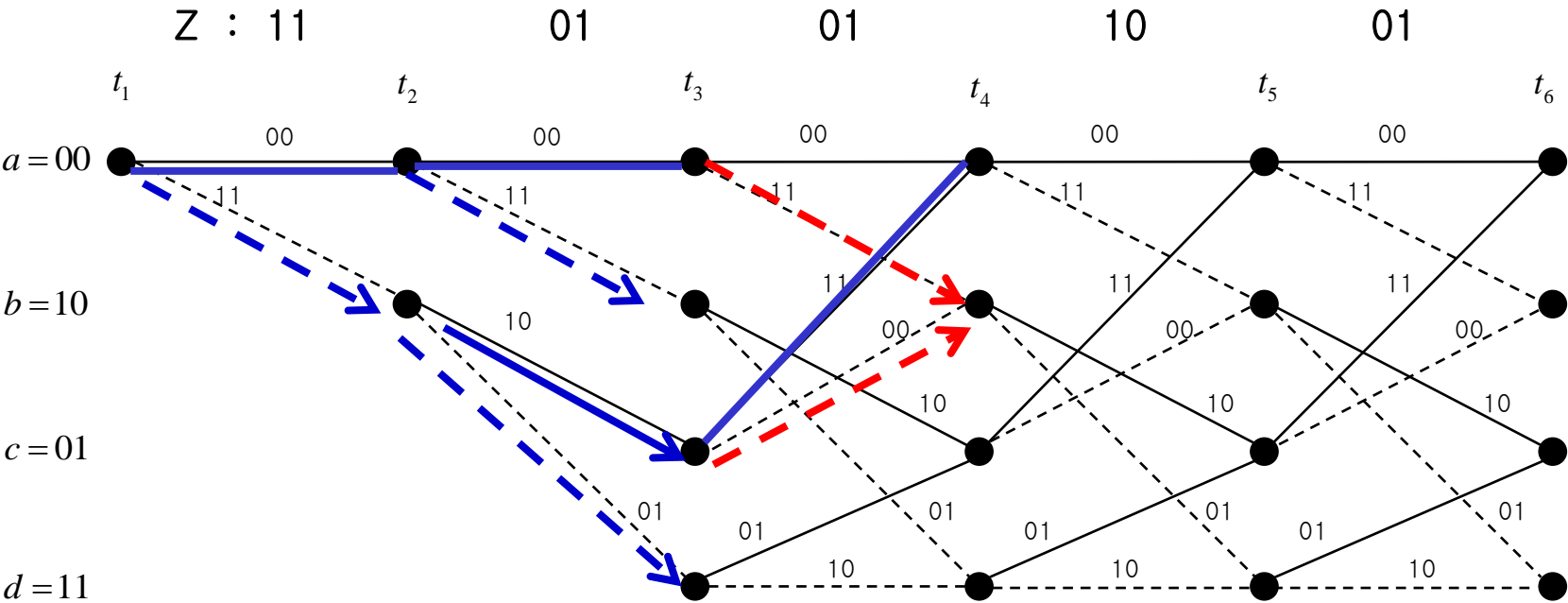Z= decoder input, received (demodulated) sequence.




`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3	3		
d2	0	0	3			
d3	0		2			
d4	0		0			
output1	None	0	00	100		
output2	None	1	01			
output3	None		10			
output4	None		11			

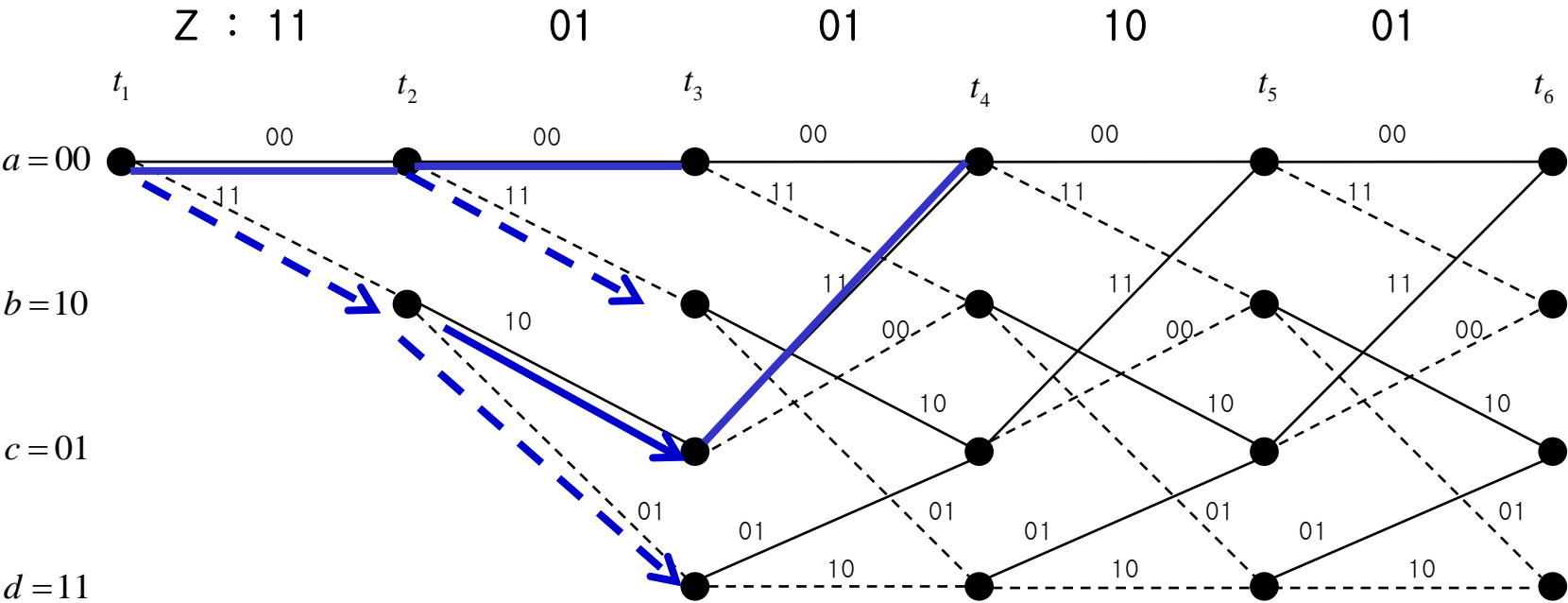Z= decoder input, received (demodulated) sequence.




`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3	3		
d2	0	0	3			
d3	0		2			
d4	0		0			
output1	None	0	00	100		
output2	None	1	01			
output3	None		10			
output4	None		11			

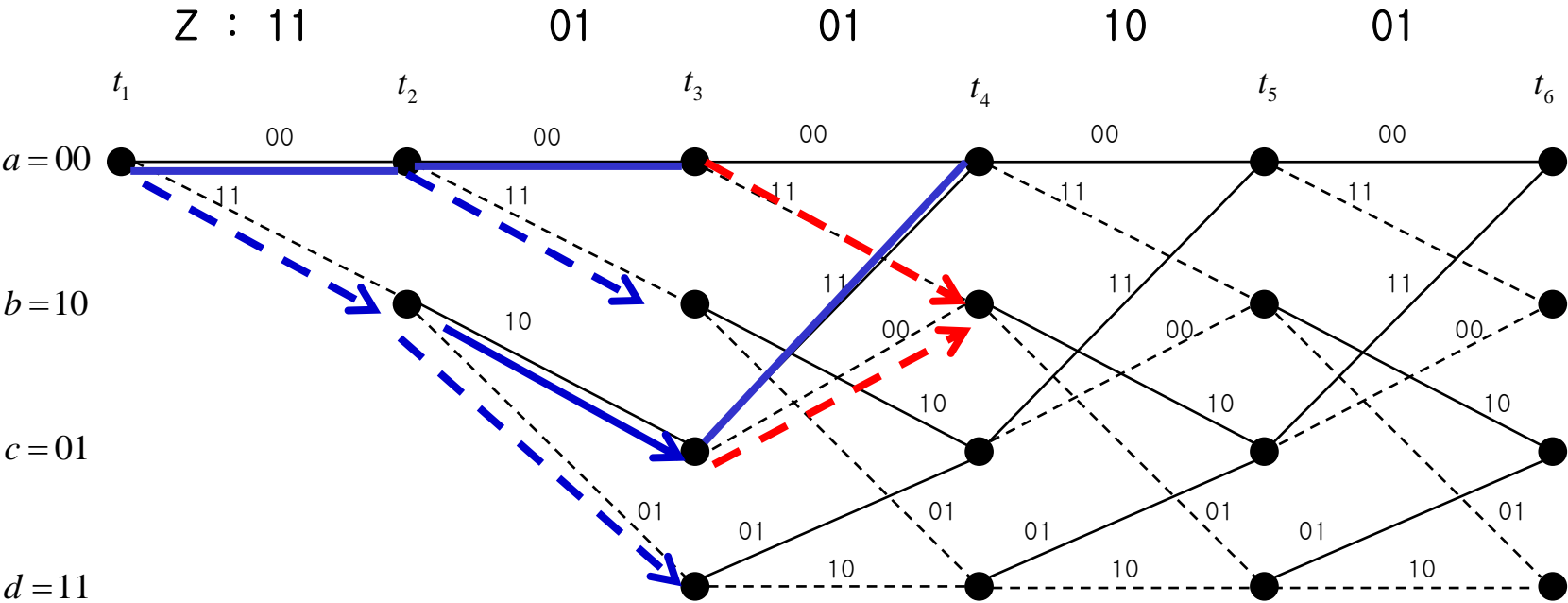Z= decoder input, received (demodulated) sequence.




`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3	3		
d2	0	0	3			
d3	0		2			
d4	0		0			
output1	None	0	00	100		
output2	None	1	01			
output3	None		10			
output4	None		11			

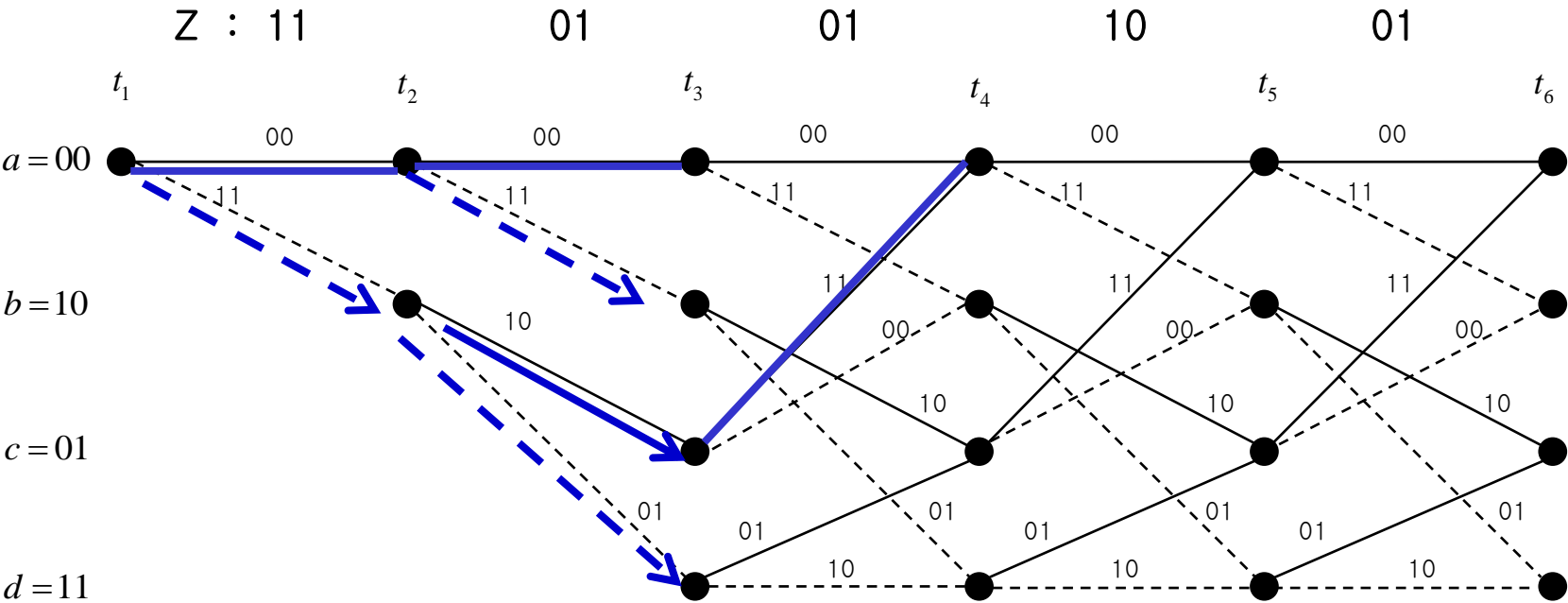Z= decoder input, received (demodulated) sequence.



`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3	3		
d2	0	0	3			
d3	0		2			
d4	0		0			
output1	None	0	00	100		
output2	None	1	01			
output3	None		10			
output4	None		11			

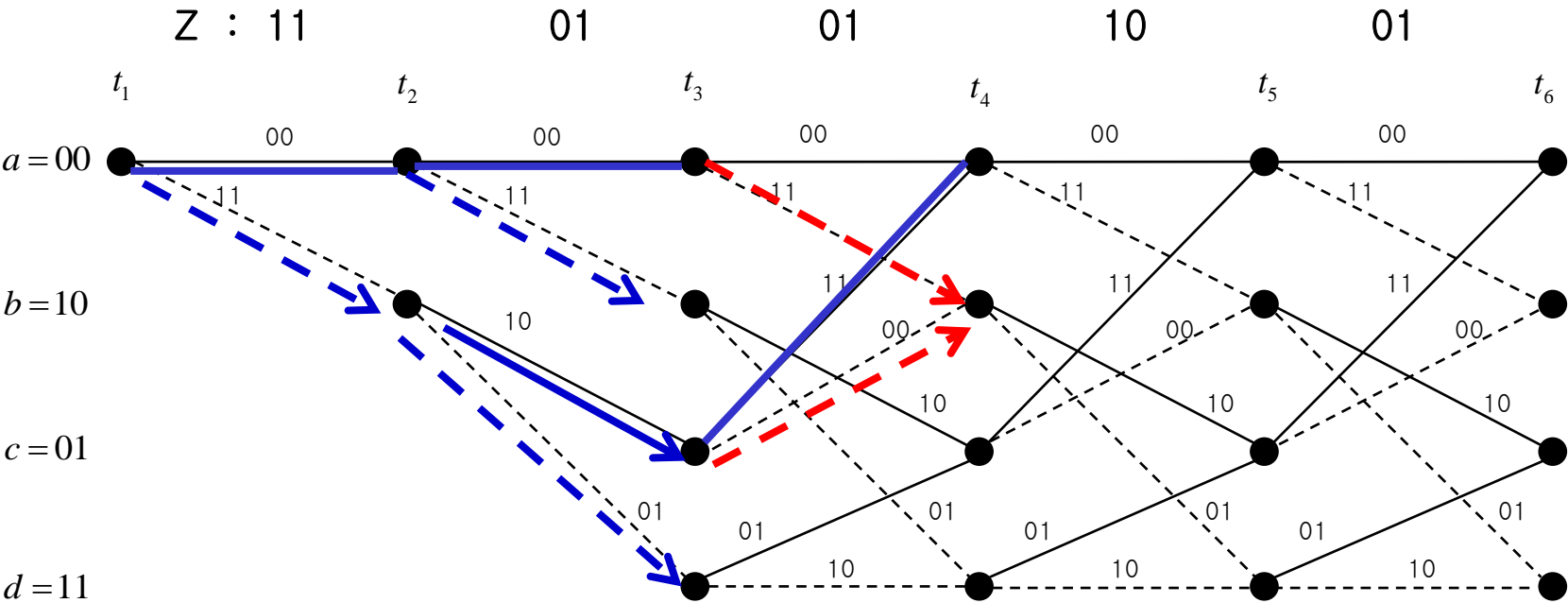
Z= decoder input, received (demodulated) sequence.



`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3	3		
d2	0	0	3			
d3	0		2			
d4	0		0			
output1	None	0	00	100		
output2	None	1	01			
output3	None		10			
output4	None		11			




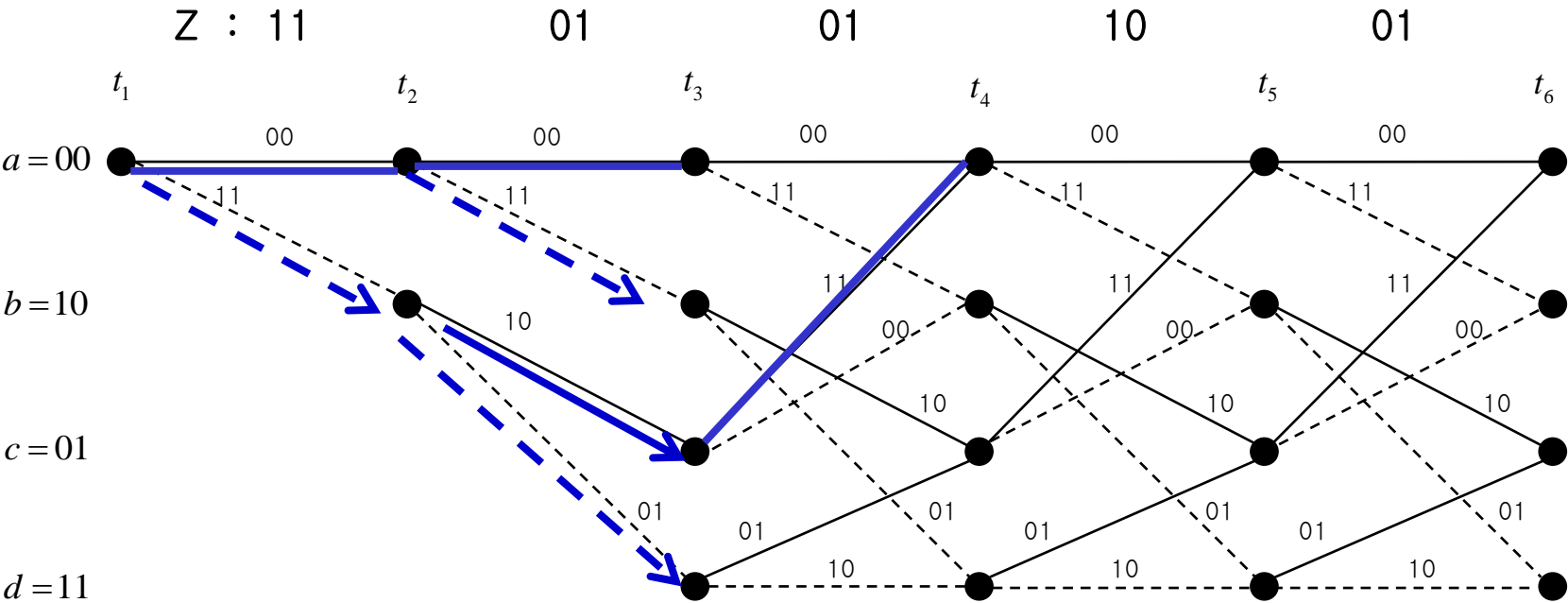Z= decoder input, received (demodulated) sequence.




`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3	3		
d2	0	0	3			
d3	0		2			
d4	0		0			
output1	None	0	00	100		
output2	None	1	01			
output3	None		10			
output4	None		11			

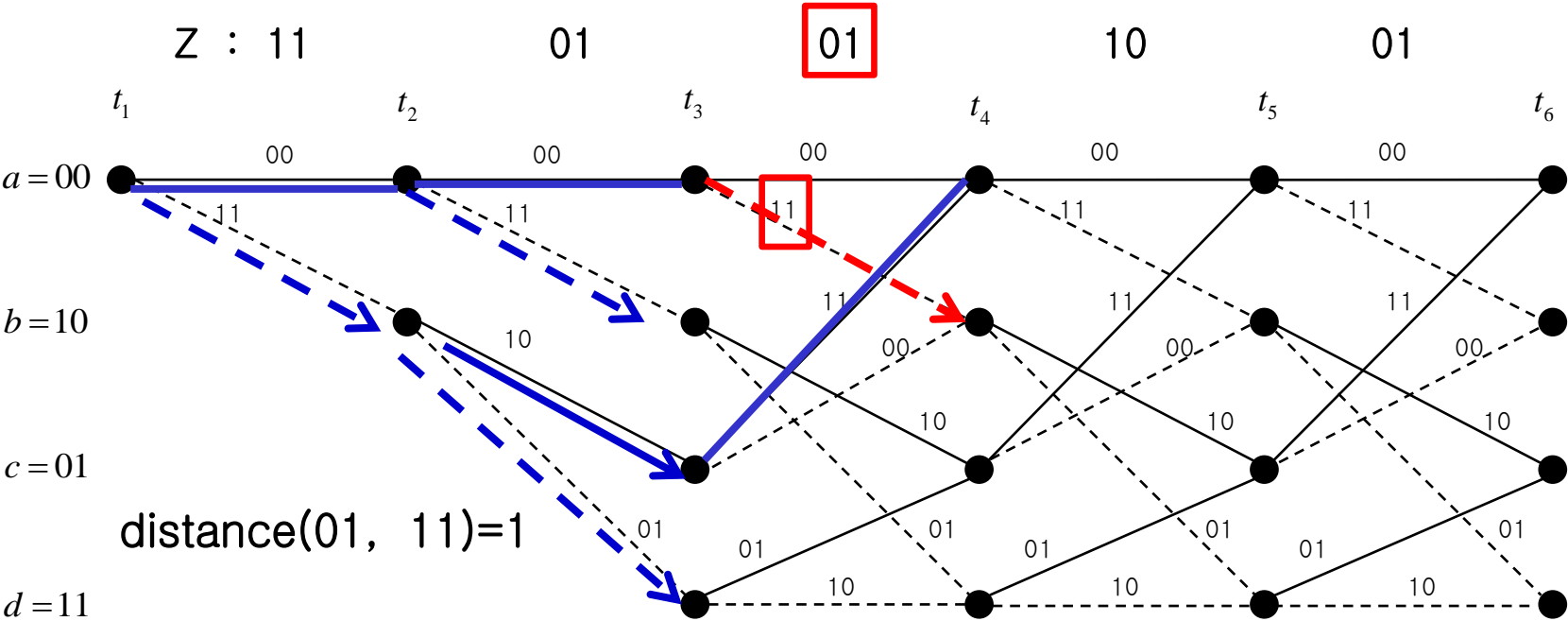Z= decoder input, received (demodulated) sequence.




`	t <sub>1</sub> =0	t <sub>1</sub> ->t <sub>2</sub>	t <sub>2</sub> ->t <sub>3</sub>	t <sub>3</sub> ->t <sub>4</sub>	t <sub>4</sub> ->t <sub>5</sub>	t <sub>5</sub> ->t <sub>6</sub>
d1	0	2	3	3		
d2	0	0	3			
d3	0		2			
d4	0		0			
output1	None	0	00	100		
output2	None	1	01			
output3	None		10			
output4	None		11			

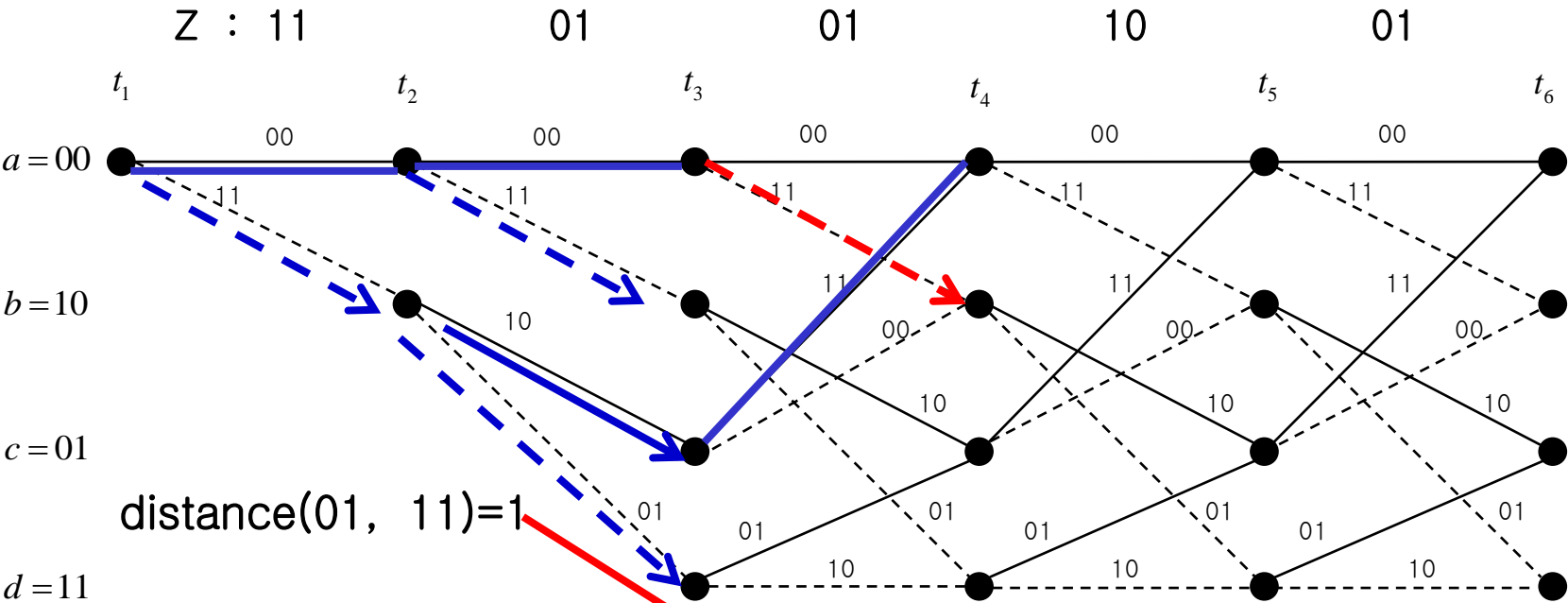Z= decoder input, received (demodulated) sequence.




`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3	3		
d2	0	0	3	3+1=4		
d3	0		2			
d4	0		0			
output1	None	0	00	100		
output2	None	1	01			
output3	None		10			
output4	None		11			

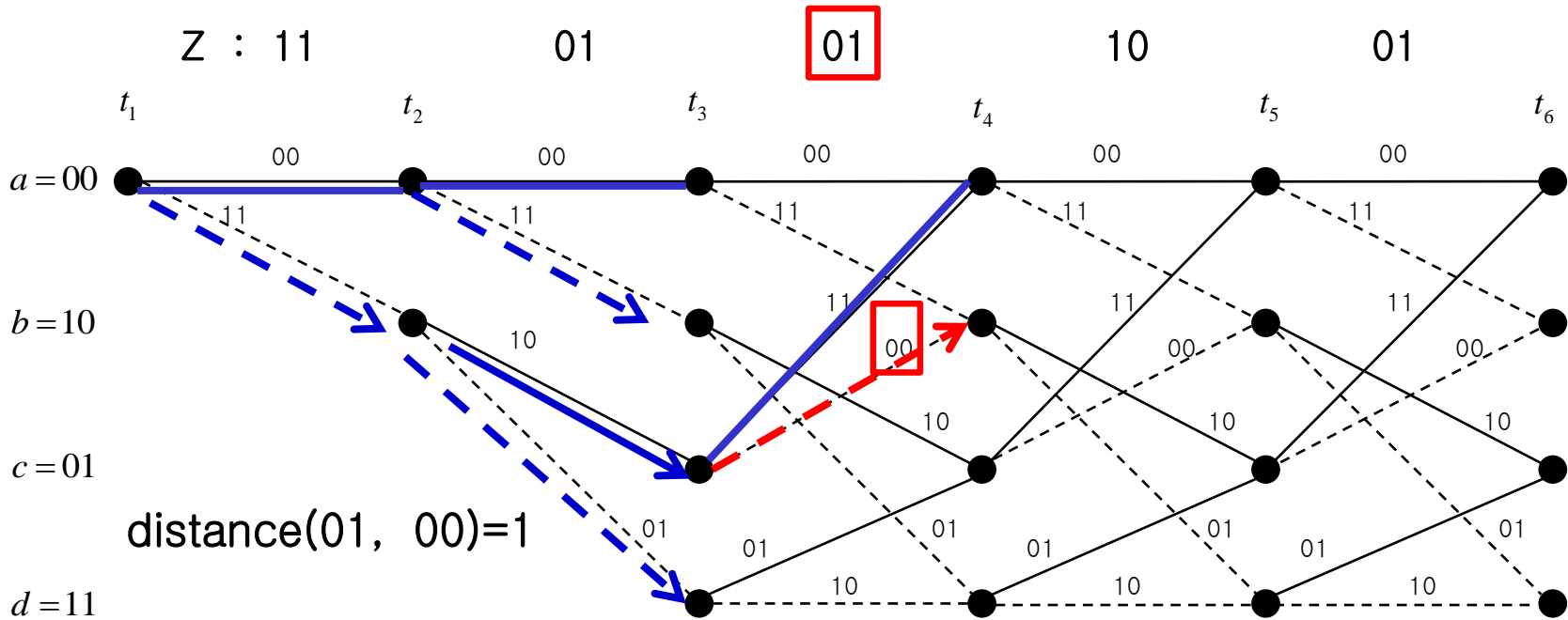Z= decoder input, received (demodulated) sequence.




`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3	3		
d2	0	0	3	(4,		
d3	0		2			
d4	0		0			
output1	None	0	00	100		
output2	None	1	01			
output3	None		10			
output4	None		11			

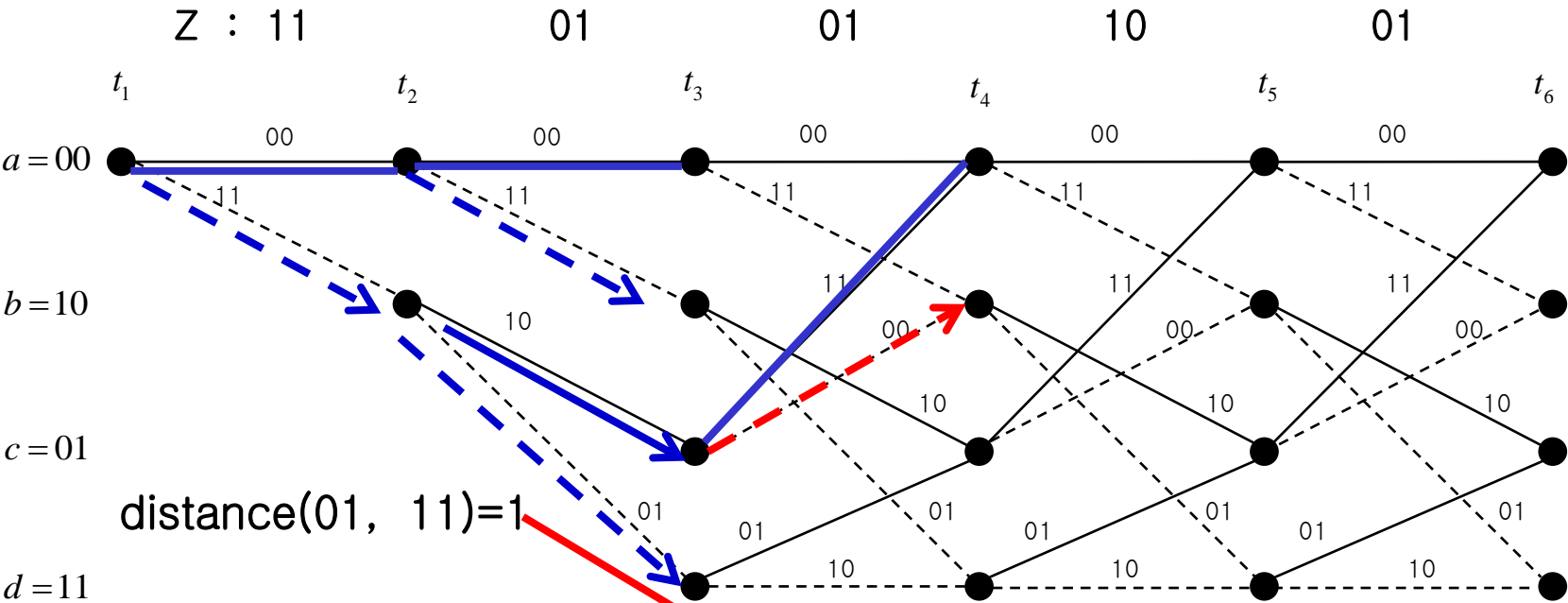Z= decoder input, received (demodulated) sequence.




`	t <sub>1</sub> =0	t <sub>1</sub> ->t <sub>2</sub>	t <sub>2</sub> ->t <sub>3</sub>	t <sub>3</sub> ->t <sub>4</sub>	t <sub>4</sub> ->t <sub>5</sub>	t <sub>5</sub> ->t <sub>6</sub>
d1	0	2	3	3		
d2	0	0	3	(4, 2+1=3)		
d3	0		2			
d4	0		0			
output1	None	0	00	100		
output2	None	1	01			
output3	None		10			
output4	None		11			

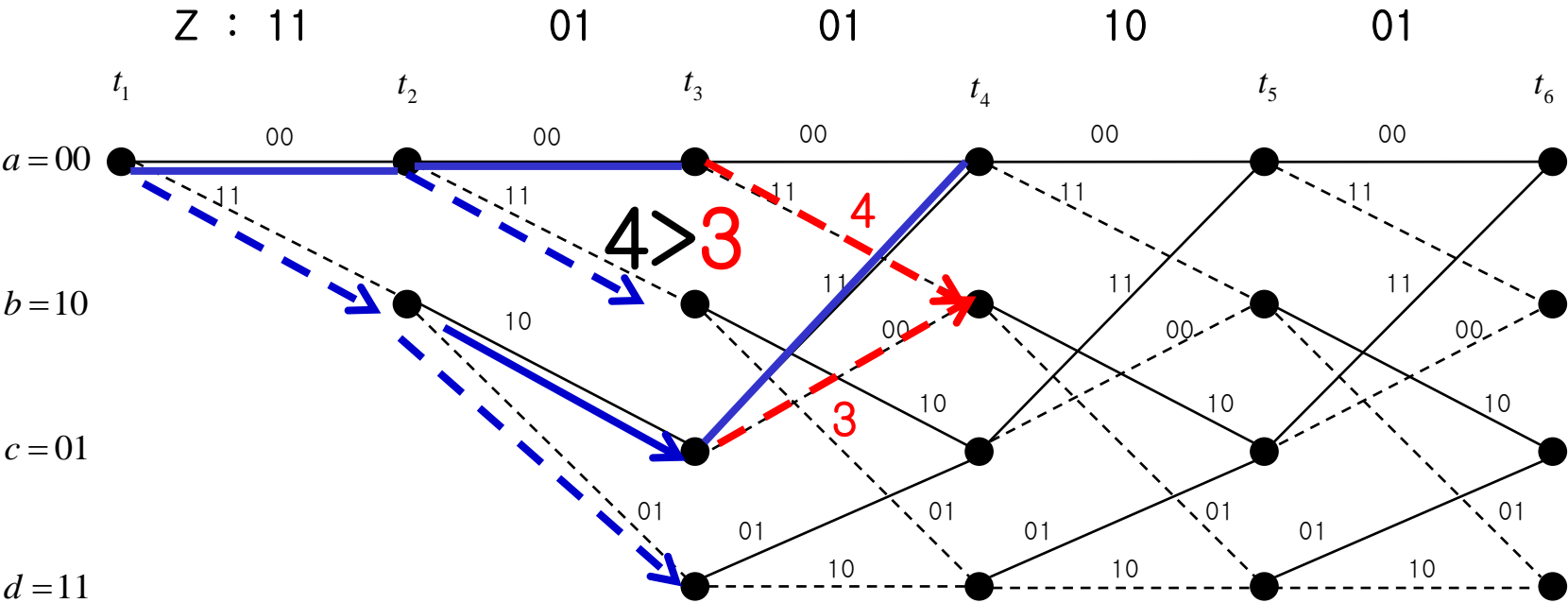Z= decoder input, received (demodulated) sequence.




`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3	3		
d2	0	0	3	(4,3)		
d3	0		2			
d4	0		0			
output1	None	0	00	100		
output2	None	1	01			
output3	None		10			
output4	None		11			

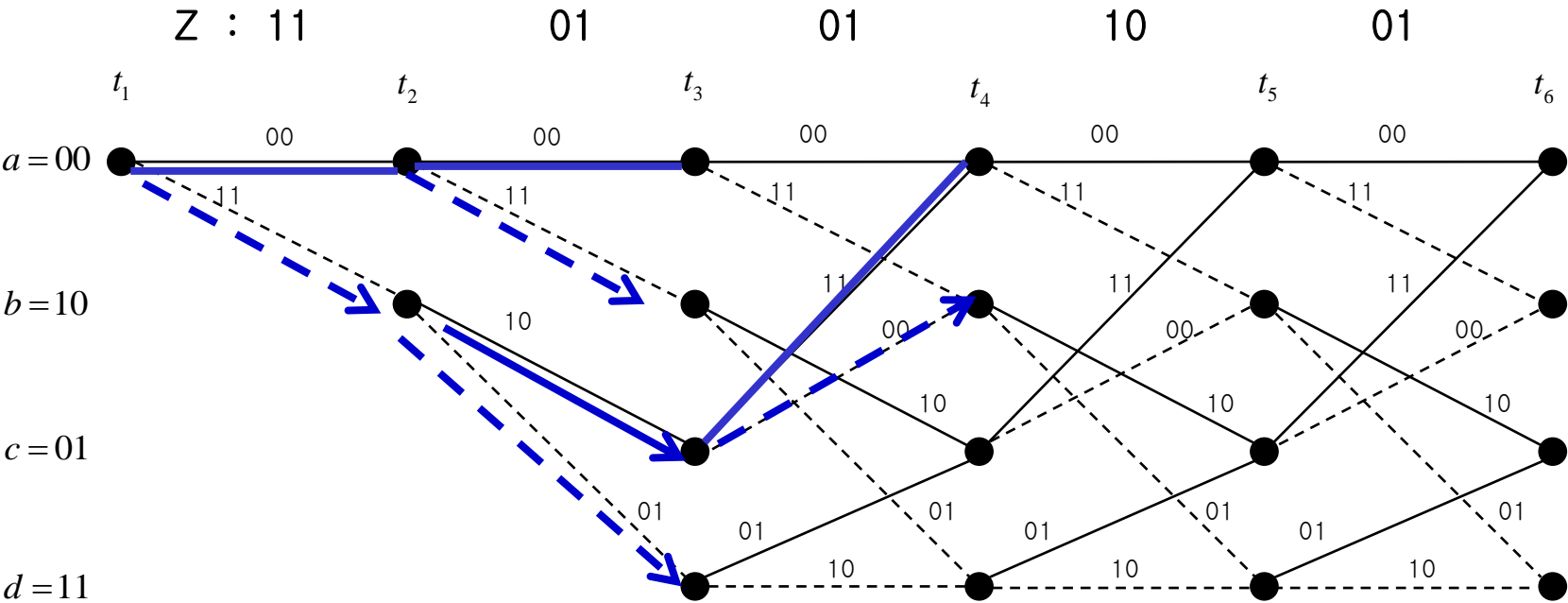Z= decoder input, received (demodulated) sequence.



`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3	3		
d2	0	0	3	3		
d3	0		2			
d4	0		0			
output1	None	0	00	100		
output2	None	1	01			
output3	None		10			
output4	None		11			

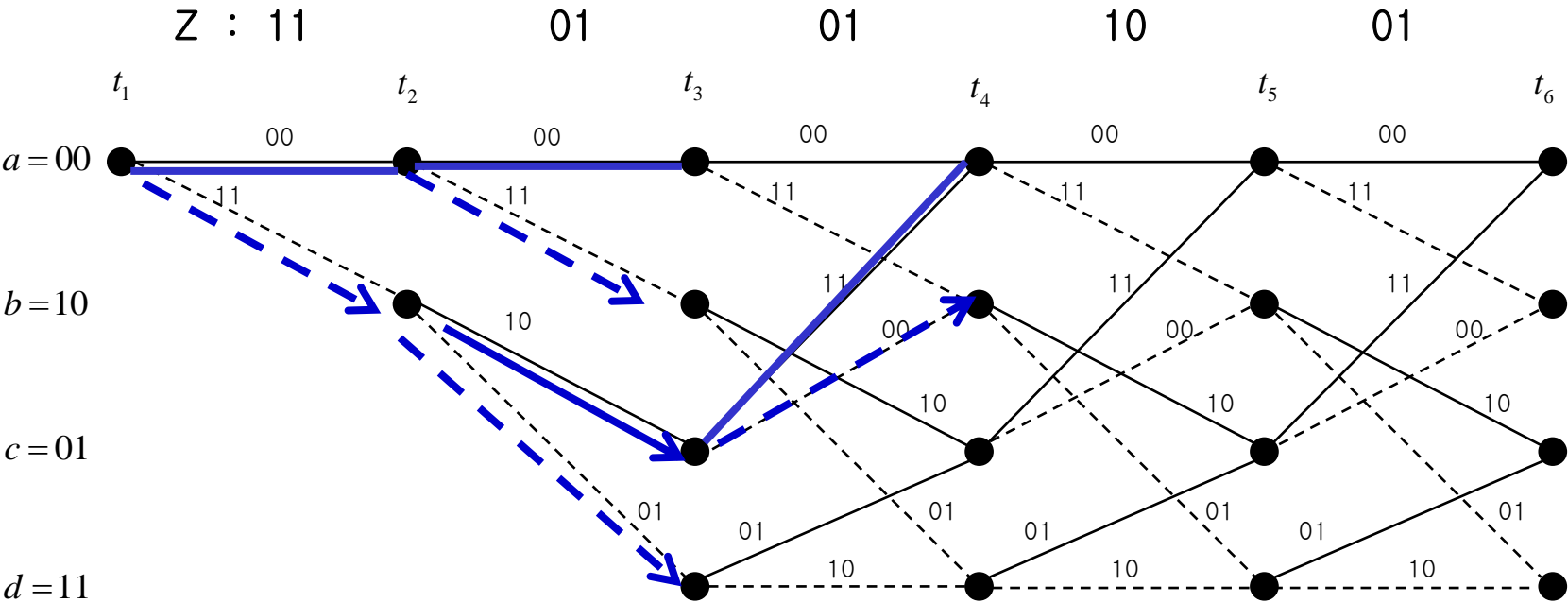
Z= decoder input, received (demodulated) sequence.



`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3	3		
d2	0	0	3	3		
d3	0		2			
d4	0		0			
output1	None	0	00	100		
output2	None	1	01	101		
output3	None		10			
output4	None		11			




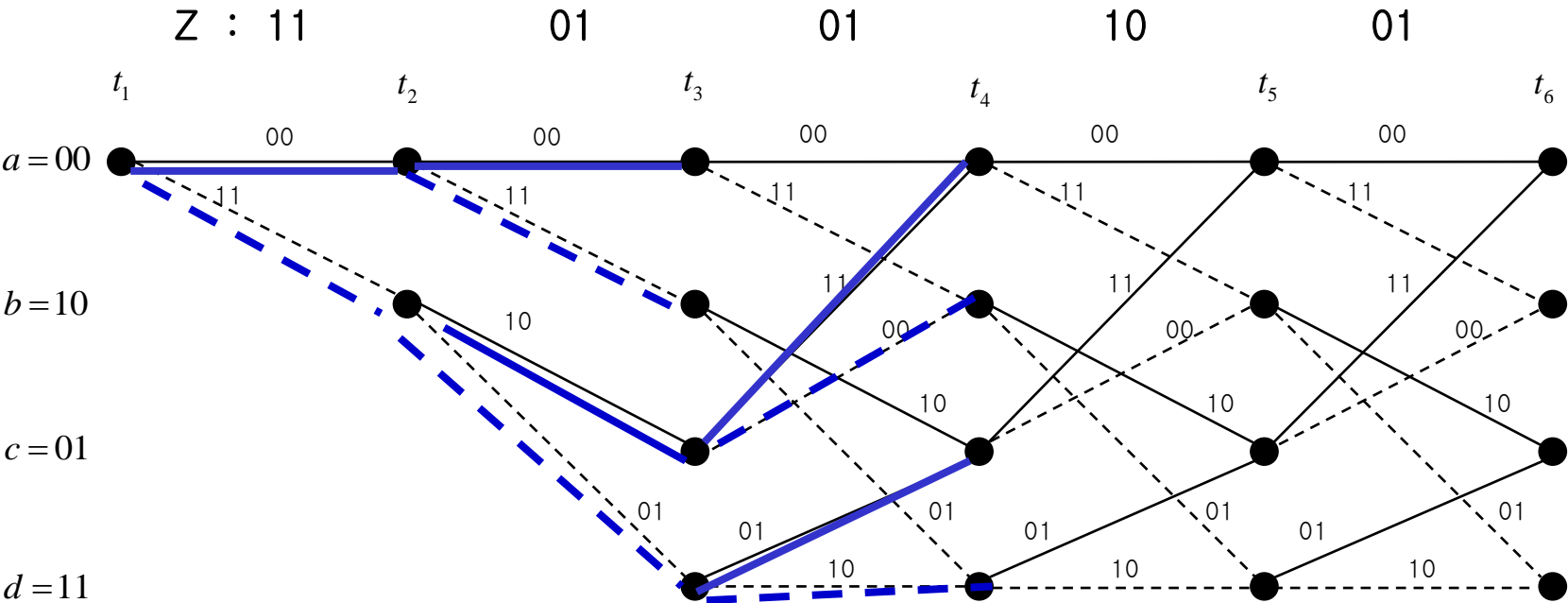Z= decoder input, received (demodulated) sequence.




`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3	3		
d2	0	0	3	3		
d3	0		2	0		
d4	0		0	2		
output1	None	0	00	100		
output2	None	1	01	101		
output3	None		10	110		
output4	None		11	111		

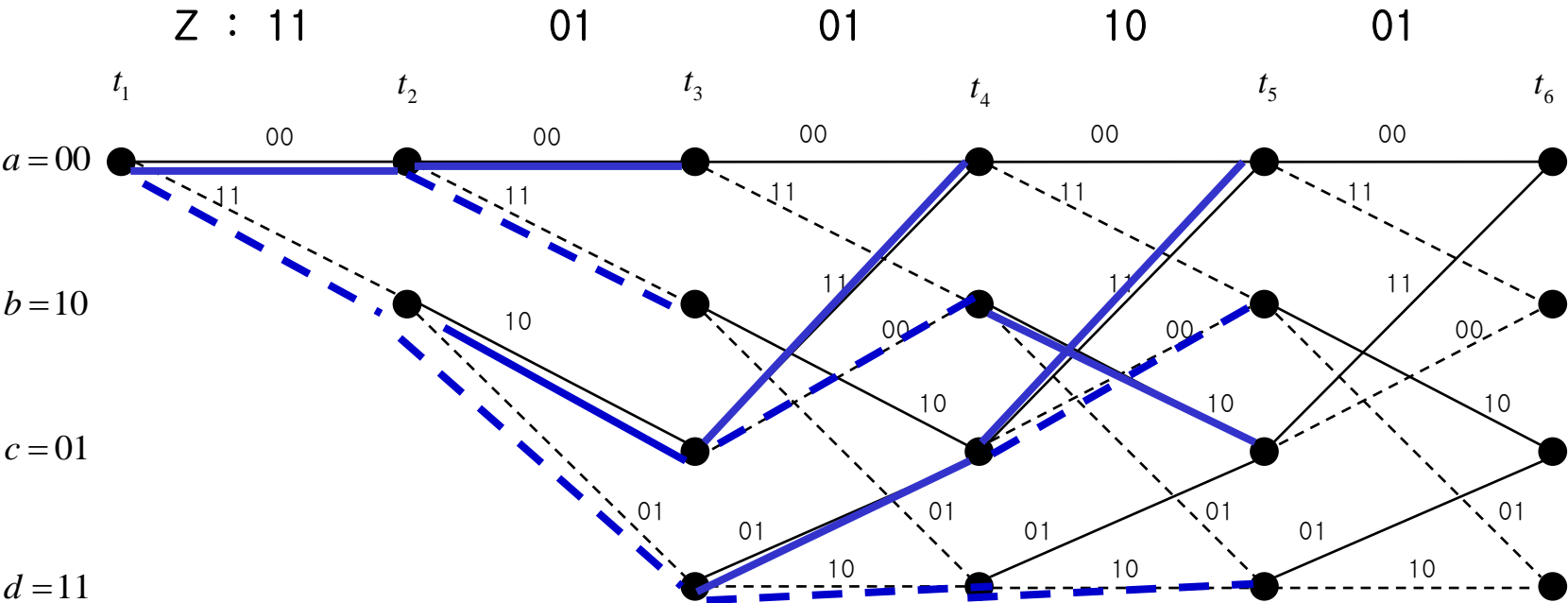Z= decoder input, received (demodulated) sequence.




`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3	3	1	
d2	0	0	3	3	1	
d3	0		2	0	3	
d4	0		0	2	2	
output1	None	0	00	100	1100	
output2	None	1	01	101	1101	
output3	None		10	110	1010	
output4	None		11	111	1111	

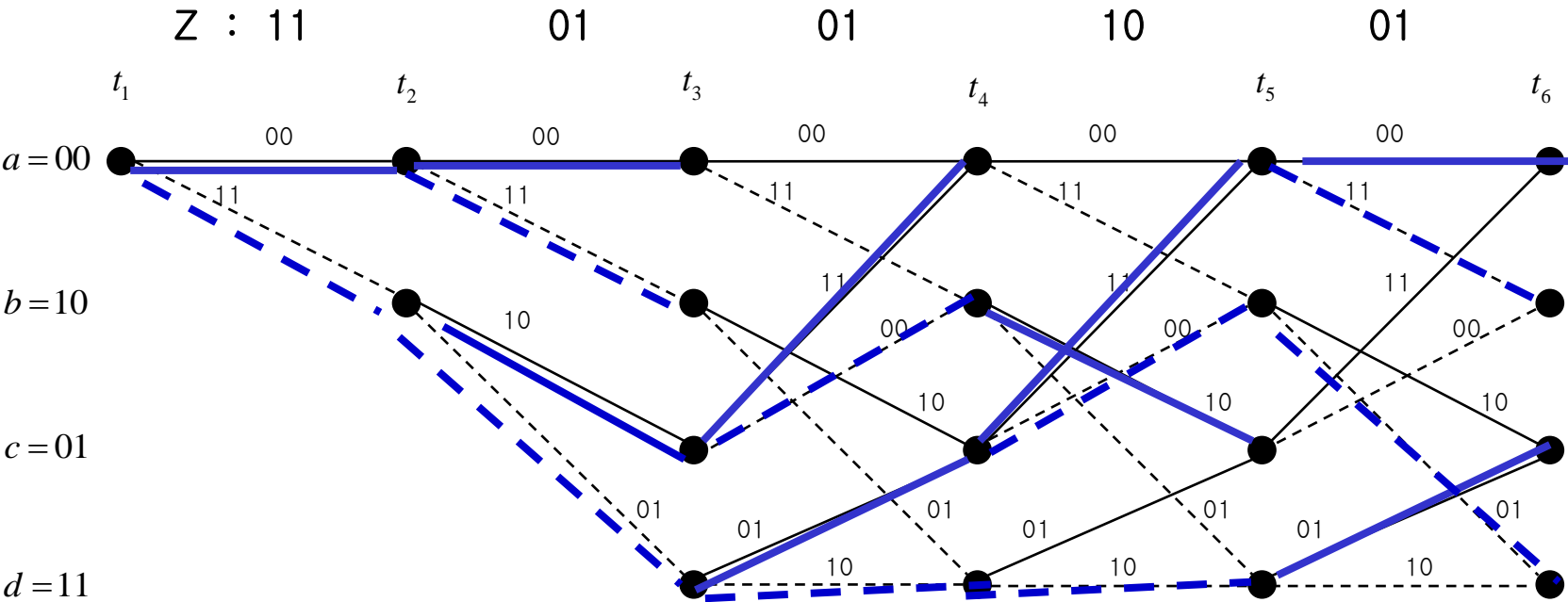Z= decoder input, received (demodulated) sequence.




`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3	3	1	2
d2	0	0	3	3	1	2
d3	0		2	0	3	2
d4	0		0	2	2	1
output1	None	0	00	100	1100	11000
output2	None	1	01	101	1101	11001
output3	None		10	110	1010	11110
output4	None		11	111	1111	11011

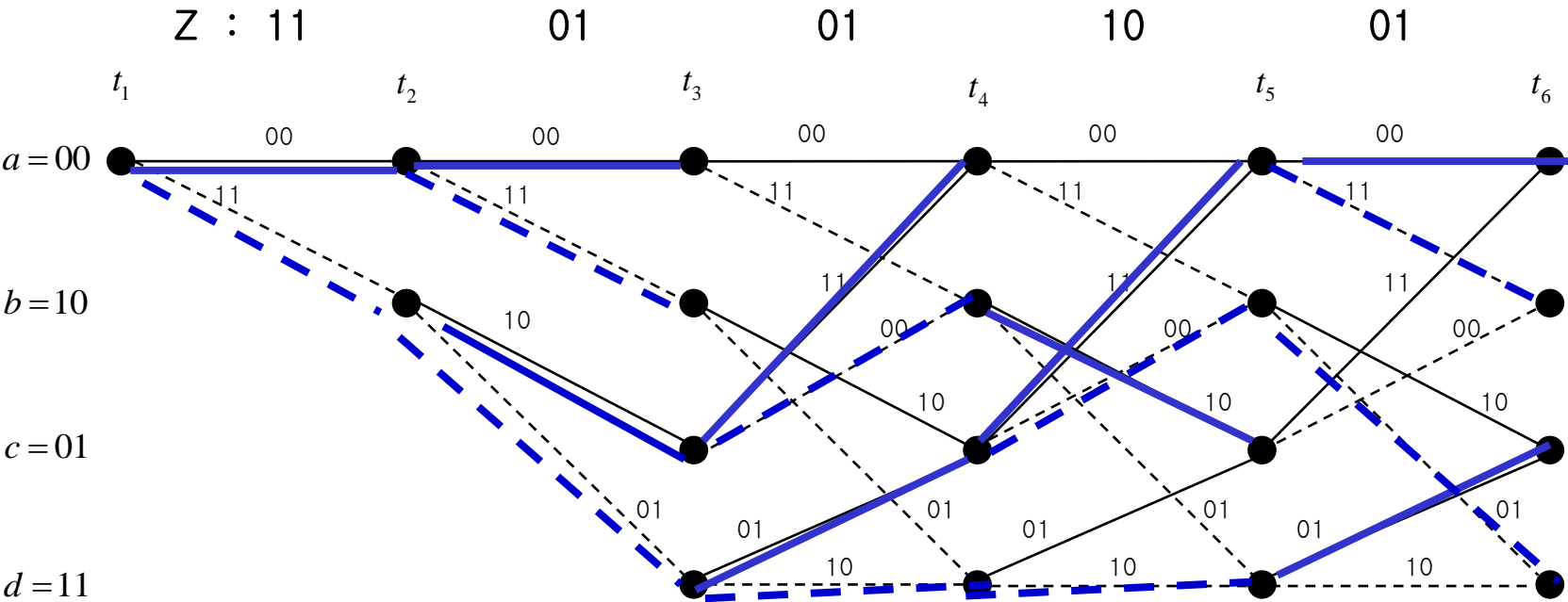Z= decoder input, received (demodulated) sequence.




`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3	3	1	2
d2	0	0	3	3	1	2
d3	0		2	0	3	2
d4	0		0	2	2	1 (Minimum)
output1	None	0	00	100	1100	11000
output2	None	1	01	101	1101	11001
output3	None		10	110	1010	11110
output4	None		11	111	1111	11011

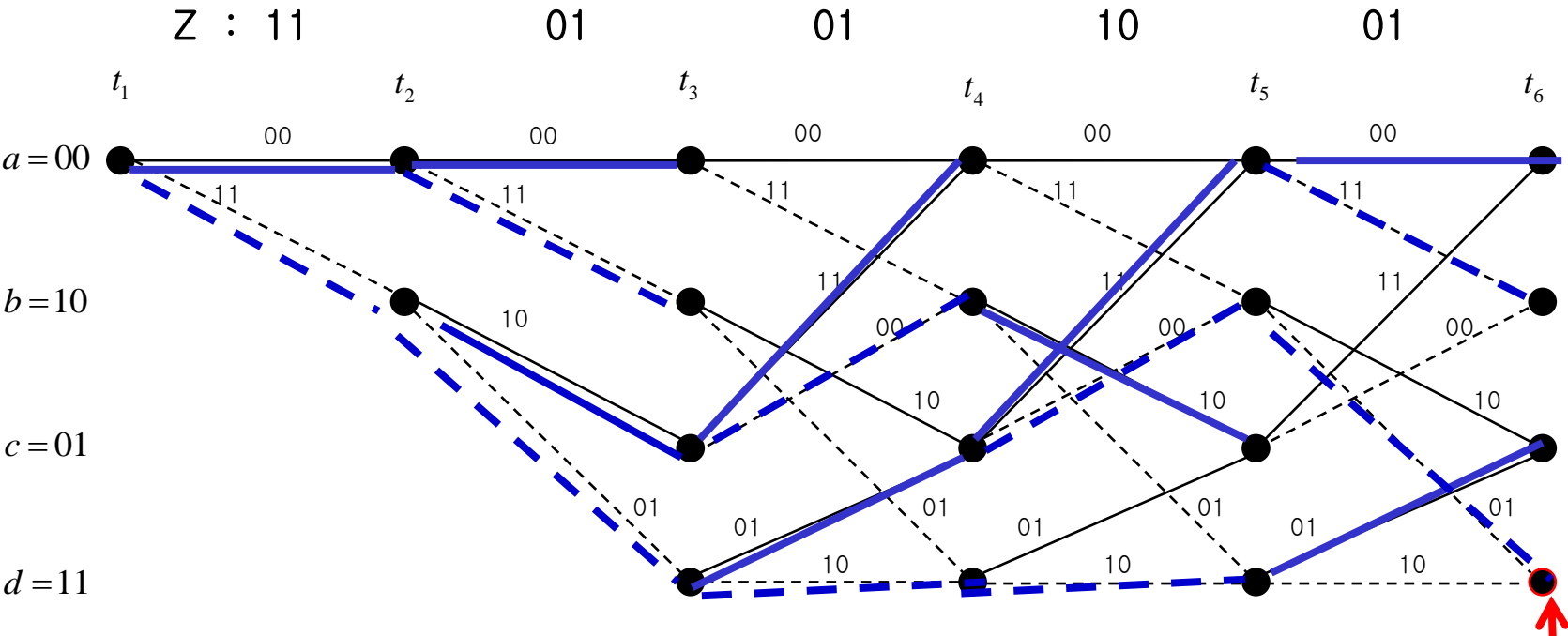Z= decoder input, received (demodulated) sequence.




`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3	3	1	2
d2	0	0	3	3	1	2
d3	0		2	0	3	2
d4	0		0	2	2	1 (Minimum)
output1	None	0	00	100	1100	11000
output2	None	1	01	101	1101	11001
output3	None		10	110	1010	11110
output4	None		11	111	1111	11011

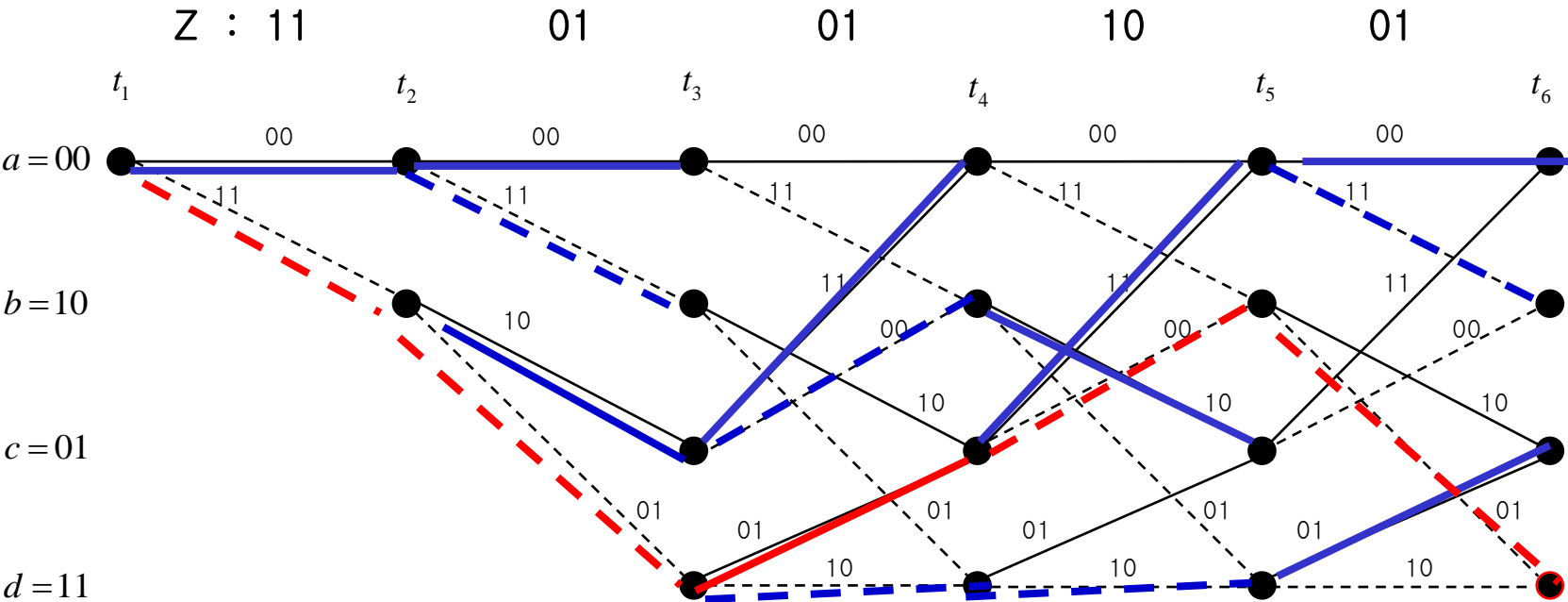Z= decoder input, received (demodulated) sequence.



`	$t_1=0$	$t_1 \rightarrow t_2$	$t_2 \rightarrow t_3$	$t_3 \rightarrow t_4$	$t_4 \rightarrow t_5$	$t_5 \rightarrow t_6$
d1	0	2	3	3	1	2
d2	0	0	3	3	1	2
d3	0		2	0	3	2
d4	0		0	2	2	1 (Minimum)
output1	None	0	00	100	1100	11000
output2	None	1	01	101	1101	11001
output3	None		10	110	1010	11110
output4	None		11	111	Decoding result = 11011	

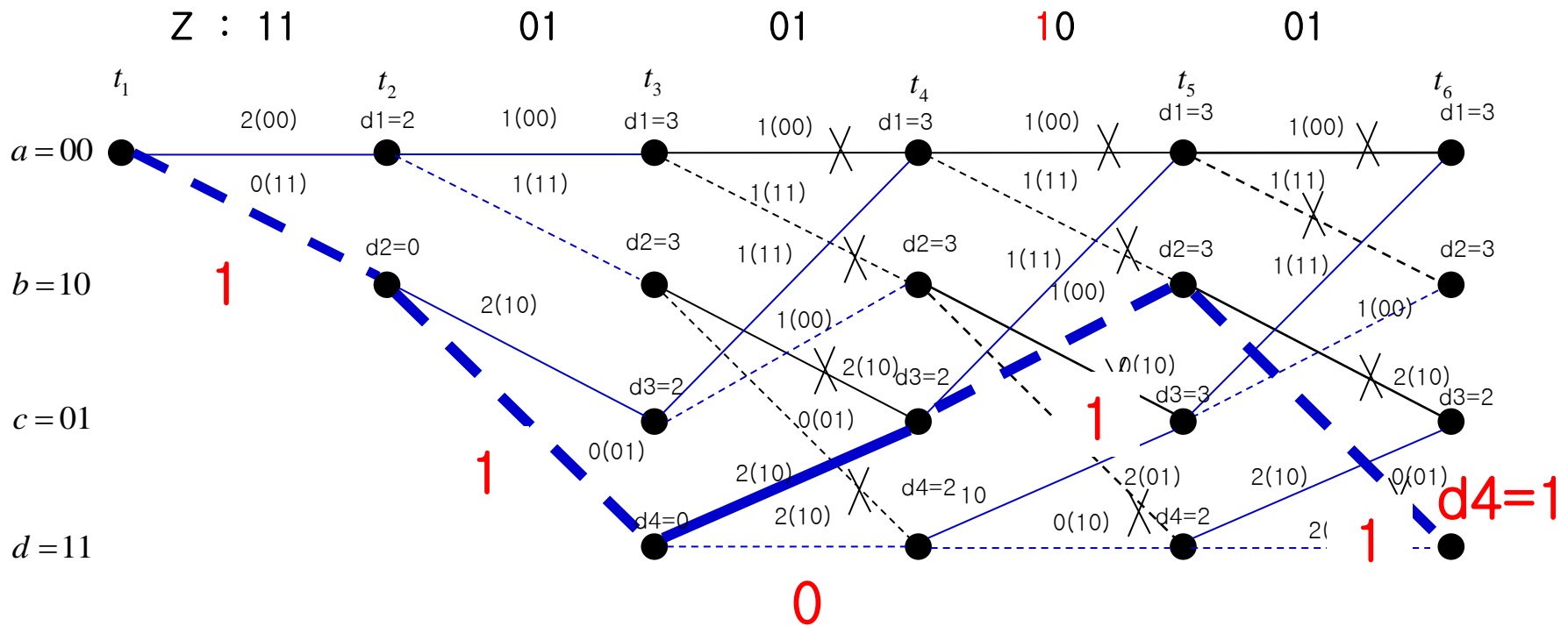

Decoder output is equal to the message  $m$  despite 1 channel bit( $z(7)$ ) error.